



Rensselaer Polytechnic Institute

Computer Hardware Design – ECSE 4770

## Lab Assignment 1 - Observing Transmission Line Effects

Rev. F

### *Objective*

- To exhibit the problems associated with driving computer busses by examining the reflections in a 50-ohm coaxial transmission line.

### *Background Information*

The [Keysight Digital oscilloscope \(model DSOX6004A\)](#) is a modern oscilloscope with its own embedded computer and has a graphical user interface. The oscilloscope has four channels, at 1GHz of bandwidth. The passive probe (N2894-60002) has a bandwidth of 700MHz, a 10M ohm impedance.

### *Related Web addresses*

Motorola

- Main site: <http://www.mot.com/>

Texas Instruments

- Main site: <http://www.ti.com>
- Digital logic data sheets: <http://www.ti.com/sc/docs/products/logic/>

Tektronix

- XYZ's of Oscilloscopes:  
[http://www.tek.com/Measurement/App\\_Notes/XYZs/03W\\_8605\\_2.pdf](http://www.tek.com/Measurement/App_Notes/XYZs/03W_8605_2.pdf)

### *Procedure*

**General Instructions:** Careful wiring is imperative in this lab since the 74S05 typically generates rise times in the 2-nanosecond range. Position the 74S05 as close as possible to one of the BNC connectors into which the 50-ohm cable will be plugged. The ground for the oscilloscope probe must be no more than a couple of inches long and should be connected directly to the ground pin of the I.C. package under observation. It is

also advisable to install bypass capacitors (0.1 $\mu$ F) between the +5 V and GND pins of each I.C. to ensure clear signals.

Note that for the report, “observe” implies including the scope output and/or measured data.

## Part 1

Set up your oscilloscope.

- Build the circuit shown in Figure 5 on the proto-board. Follow the suggestions made above. You will need to select a value for the capacitor C1, using the data sheet for the 555 timer. The output signal should be a relatively low noise periodic signal that can be used to study the different scope modes. You need not worry about the value or placement of R for this part. Attach the probe to the output (pin 3) of the 555 timer.
- Obtain and observe a stable trace of the 555. Try using the "runt" triggering modes. Try the horizontal delay mode. Describe the effects these modes have.
- Change the capacitor on pins 2/6. How does this affect the output?
- Observe the effect of changing one of the 10-Kohm resistors.

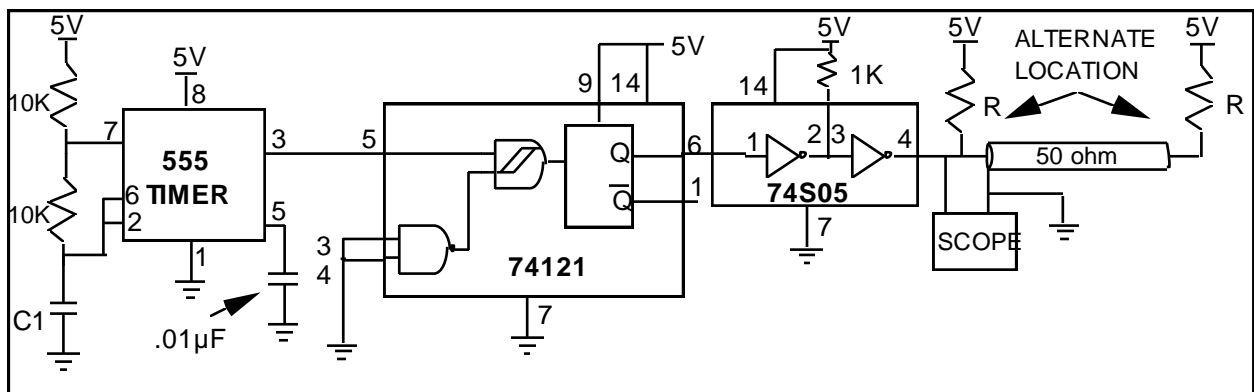


Figure 1: Wiring diagram for Part 1

## Part 2

Move the scope probe to the output of the 74S05 just in front of the coax cable. The 74S05 open collector Schottky gate has 20 mA sinking capability.

- It will not be possible to correctly drive the 50-ohm impedance cable with this gate. Why is this? Refer to the data sheet for the 74S05.
- Use a 1 Kohm resistor for R and place it at the end of the 50-ohm cable. Observe line reflections and show how to measure the velocity of propagation in the cable using those reflections. Show your calculations and record your result.
- Repeat b) with R relocated at the 74S05 output.
- Repeat b) with additional lengths of cable.
- Why does the leading edge of the pulse look different from the falling edge?
- What is the smallest safe value of R? What criteria determine this value?

- g) Use the criteria you found in f) to redesign the termination to have a pull-up and pull-down resistor, R1 and R2. Match to the minimum safe value of R. Repeat b) with this new termination.

### Part 3

The 74128 50-ohm cable driver is a TTL chip designed expressly for driving 50-ohm cable. Rebuild the circuit using the 74128 instead of the 74S05.

- Observe any reflections now on the cable.
- Recalculate the minimum safe R. Refer to the data sheet for the 72128 and note that the 74128 can sink 48 mA.
- Adjust R to minimize line reflection.

### Part 4

Try any of the other drivers or receivers whose data sheets are enclosed. Use a tri-state driver, like the 74ls241. Observe the signals on the line when there is no terminator (this is common on small computer busses). Some additional things to try are:

- Add pull-up resistors in the middle of the cable using T connectors. Describe their effect on the signal.
- Drive the line with multiple open collector gates. Think about how the circuit for a bus like this would look, and explain how it works.
- Try plugging the end of the 50-ohm cable directly into the scope input and observe the signal at the end of the line.


### Part 5

Try assembling a 7474 Edge Triggered flip-flop out of individual gates, as shown in Figure 2 (using the 7400, 7410, or 7420 as building blocks).

- Observe the edge triggering and give a verbal explanation of its behavior.
- Attempt to excite a race by driving both the data and clock inputs simultaneously (i.e. drive both inputs with the same signal).
- Try introducing some small parasitic capacitance on various gate outputs to influence the outcome.
- Try using 74S parts.

**Table 1: Typical characteristics of SN54 and SN74 series flip-flops**

	TYPICAL CHARACTERISTICS		DATA TIMES		TEMPERATURE RANGE	
DWG REF	Fmax (MHz)	Pwr/F-F (mW)	Setup(ns)	Hold(ns)	55 C - 125 C	0 C - 70 C
Q	110	75	3	2	SN54S74	SN74S74
	43	75	15	5	SN54H74	SN74H74
	33	10	25	5	SN54LS74	SN74LS74
	25	43	20	5	SN5474	SN7474
	3	4	50	0	SN54L74	SN74L74

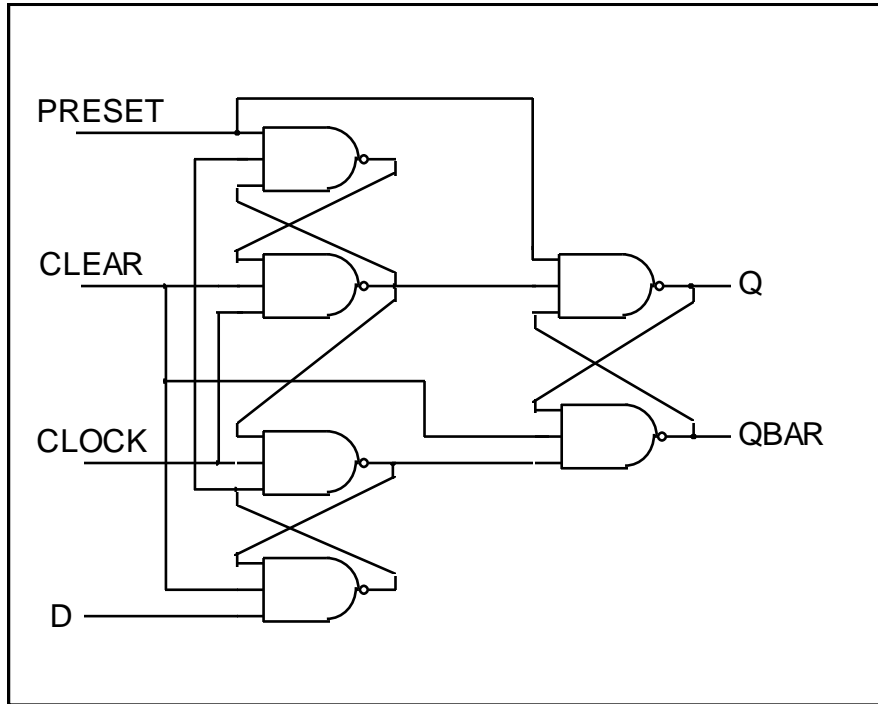

**Figure 2: Schematic of internal logic of '74 Edge Triggered D flip-flop**