

# ELECTRIC CIRCUITS ECSE-2010

Lecture 28: Course Wrap Up



## AGENDA


- Active Filter Building Blocks: Sallen-Key Configuration
- FINAL EXAM DETAILS
- Hand back EXAM 3
- Preliminary Exam 3 regrade
- Brief Overview of Topics (on your own)

sawyes@rpi.edu

www.rpi.edu/~sawyes




## SALLEN-KEY LOW PASS

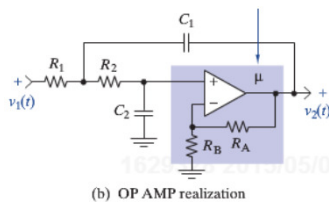

From Textbook, Thomas, Rosa, and Toussaint, pg. 739



## SALLEN-KEY HIGH PASS

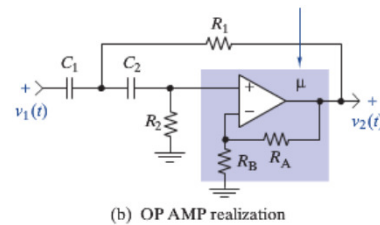

From Textbook, Thomas, Rosa, and Toussaint, pg. 744



## SALLEN-KEY BANDPASS

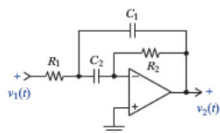


FIGURE 14-14 Second-order bandpass circuit.

From Textbook, Thomas, Rosa, and Toussaint, pg. 749



## SALLEN-KEY LOW PASS

$$H(s) = \frac{K \omega_0^2}{s^2 + 2\zeta \omega_0 s + \omega_0^2}$$

$$K = \mu = 1 + \frac{R_A}{R_B} \quad \omega_0 = \frac{1}{\sqrt{R_1 C_1 R_2 C_2}}$$

$$2\zeta = \sqrt{\frac{R_2 C_2}{R_1 C_1}} + \sqrt{\frac{R_1 C_2}{R_2 C_1}} + (1 - \mu) \sqrt{\frac{R_1 C_1}{R_2 C_2}}$$

2<sup>nd</sup> Order Low Pass Filter



## SALLEN-KEY LOW PASS: EQUAL ELEMENT

If Choose  $R_1 = R_2 = R$ ;  $C_1 = C_2 = C$

$$\omega_0 = \frac{1}{RC} \quad \zeta = \frac{3-\mu}{2} = 1 - \frac{R_A}{2R_B}$$

Note: Cannot Make  $\zeta > 1$

For  $R_A = 0 \Rightarrow \zeta = 1 \Rightarrow$  Critically Damped

For  $R_A < 2R_B \Rightarrow 0 < \zeta < 1 \Rightarrow$  Underdamped

For  $R_A = 2R_B \Rightarrow \zeta = 0 \Rightarrow$  Oscillator

For  $R_A > 2R_B \Rightarrow \zeta < 0 \Rightarrow$  Unstable



## EXAM DETAILS

- Monday, May 18th, **Sage 3303**, 11:30-2:30 pm
- Bring a calculator (no wireless, no cell phones please)
- One new crib sheet + 3 previous crib sheets, front and back!
- Folks with **approved extra time**, meet in my office **before test**.

sawyer@rpi.edu

www.rpi.edu/~sawyer



## FINAL EXAM STRUCTURE

- Short Answer (25 points) **Any conceptual question from any unit!**
- Unit 1: Basic Circuit Analysis (25 points)
  - First order transient
  - Laplace second order
- Unit 2: Transient Response (25 points)
  - Complex Power
  - Transformer
- Unit 3: AC Steady State and Power (25 points)
  - First/Second Order Bode plots with corrections and SLA
  - Cascading filters
- Unit 4: AC Steady State Frequency Response (25 points)
  - Filter Design Problem (25 points)

sawyer@rpi.edu

www.rpi.edu/~sawyer



## ADVICE ON FINAL EXAM AND BEYOND....

- Final Exam
  - Do homework 10 all questions as a review
  - Try to take some time to match process with theory
- After Circuits....
  - Stay ahead of the professor (read book/videos/go online.... anything)
  - It takes practice to match theory to analytical (give yourself enough time!)
  - Always check your exams for missed concepts
  - Stay engaged and ask questions during lecture...after lecture

sawyer@rpi.edu

www.rpi.edu/~sawyer



Congratulations, you are officially **electrical engineering students!**

Now you must become **electrical engineers/computer systems engineers/dual major engineers.....** may the (electromagnetic) Force be with you...

sawyer@rpi.edu

www.rpi.edu/~sawyer



## UNIT 1

DC Circuit Analysis and OP Amps



## REVIEW: LECTURE 1

- Passive Sign Convention
- Voltage Reference Point – Ground
- Linear Resistor – Ohm's Law
- Open/Short Circuits – Ideal Switches
- Ideal Voltage and Current Sources
- Reference Marks
- Kirkoff's Laws

sawyes@rpi.edu

www.rpi.edu/~sawyes



## CHECK SLIDES...

***▪ If you don't have Lecture 1 down,  
you're in trouble!!  
I'll skip.***

sawyes@rpi.edu

www.rpi.edu/~sawyes



## REVIEW: LECTURE 2

- Series and Parallel Connections
- Equivalent Circuits
  - Series and Parallel Resistors
  - Voltage and Current Dividers

sawyes@rpi.edu

www.rpi.edu/~sawyes



## CHECK SLIDES...

***▪ If you don't have Lecture 2 down,  
you're still in trouble!!  
I'll skip.***

sawyes@rpi.edu

www.rpi.edu/~sawyes



## REVIEW: LECTURE 3

- Node Analysis
- Mesh Analysis

sawyes@rpi.edu

www.rpi.edu/~sawyes



## SUMMARY

- **Node Voltage Analysis:**
  - Label All Node Voltages, Known and Unknown, Identifying Variables ( $v_1$ ,  $v_2$ , etc.)
  - # of Unknown Node Voltages = # of Nodes - # of Voltage Sources - 1 (Reference)
  - Write a KCL at Each Unknown Node Voltage
    - Best to Use: **Sum of Currents Out of Node = 0**
    - Express  $i$ 's in terms of Node Voltages
  - Solve Algebraic Equations for Node Voltages
    - Use MAPLE, MATLAB, Cramer's Rule, etc.
  - Solve for Currents Using Ohm's Law



### NODE ANALYSIS -SOLVING PROCEDURE

1. Identify all nodes
2. Choose a reference node (ground)
3. Label the unknown nodes
4. Locate all voltage sources
  1. Determine either absolute or relative voltages based on the voltage sources
5. Write a KCL equation for each node
6. Use Ohm's Law to rewrite the currents as voltage differences over resistance
  1. If a voltage source is on one of the current paths, 'follow' it to the next node to get an expression for current.
7. Set up the linear system
8. Solve the matrix



### NODE ANALYSIS-WITH VOLTAGE SOURCES SEE PG 84

Adding voltage sources to circuits modifies node analysis procedure because the current through a voltage source is not directly related to the voltage across it.

**Actually simplifies node analysis by reducing the number of equation required.**

**Method 1:** Use source transformation to replace the voltage source and series resistance with an equivalent current source and parallel resistance

**Method 2:** Strategically select reference node and write node equations at the remaining  $N-2$  non-reference nodes in the usual way (can be used whether or not there is a resistance in series with voltage source)

**Method 3:** Combine nodes to make a supernode

### SUMMARY

- **Mesh Current Analysis:**
  - Label and Define ALL Mesh Currents
    - Unknown Mesh Currents and Currents from Current Sources
  - # of Unknown Mesh Currents = # of Meshes - # of Current Sources;
  - Write a KVL around Each Unknown Mesh Current
    - Sum of Voltages due to All Mesh Currents = 0
    - Best to Go Backwards Around Current Arrow
  - Solve Algebraic Equations for Mesh Currents (Maple, Cramer's Rule, etc.)
  - Solve for Voltages Using Ohms Law



### MESH ANALYSIS -SOLVING PROCEDURE

1. Identify all loops
2. Locate all current sources
3. If possible, simplify the problem by redrawing the circuit with current sources on the 'outside'
4. Label the currents in each loop
5. Assign the current directly if a current source is on the 'outside'
6. Assign a relative current expression if the current source is shared by two loops.
7. Write a KVL expression for each loop
  1. If a current source is shared by two loops, combine them to form a larger loop.
8. Use Ohm's Law to write the KVL in terms of currents
9. Set up the linear system
10. Solve the matrix



### MESH ANALYSIS-WITH CURRENT SOURCES SEE PG 97

**Method 1:** Use source transformation to replace current source and parallel resistance with an equivalent voltage source and series resistance

**Method 2:** If current source is contained in only one mesh, then that mesh current is determined by the source current and is no longer an unknown. Write mesh equations around the remaining meshes in the usual way and move known mesh current to the source side of the equations in the final step.

**Method 3:** Create a supermesh by excluding the current source and any elements connected in series with it.



### REVIEW: LECTURE 4

- Linearity
- Superposition Principle
- Superposition Example
- Dependent Sources



## LINEARITY

- If have multiple inputs
- Input =  $x_1 + x_2 + x_3$
- Output must be additive
- $y = k_1x_1 + k_2x_2 + k_3x_3$
- Leads to Superposition Principle
  - Can use only for multiple inputs to a linear circuit

sawyer@rpi.edu

www.rpi.edu/~sawyer



## SUPERPOSITION

- Find Output due to each independent source with all other independent sources set = 0; then Add to find Total Output:
  - Source of 0 is called a “dead source”
  - “Dead” voltage source = 0 V = Short Circuit
  - “Dead” current source = 0 A = Open Circuit

sawyer@rpi.edu

www.rpi.edu/~sawyer



## SUPERPOSITION

- Total Output = Sum of all Outputs due to each independent source with all other independent sources “dead”:
  - Simply Add them
  - Works only for Linear Circuits; Only kind we will consider

sawyer@rpi.edu

www.rpi.edu/~sawyer



## DEPENDENT SOURCES


- Symbol:
  - Diamond = Symbol for Dependent Source
  - Circle = Symbol for Independent Source
- 4 Types of Dependent Sources
  - Voltage Controlled Voltage Source (VCVS), E
  - Current Controlled Current Source (CCCS), F
  - Voltage Controlled Current Source (VCCS), G
  - Current Controlled Voltage Source (CCVS), H

sawyer@rpi.edu

www.rpi.edu/~sawyer



## VCVS

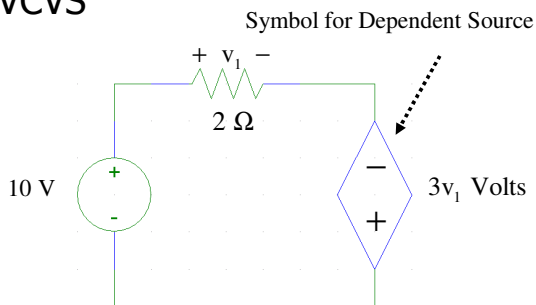

Voltage Controlled Voltage Source (VCVS)

sawyer@rpi.edu

www.rpi.edu/~sawyer



## REVIEW: LECTURE 5


- Wheatstone bridge
- Norton/Thevinin equivalent circuits

sawyer@rpi.edu

www.rpi.edu/~sawyer



## WHEATSTONE BRIDGE

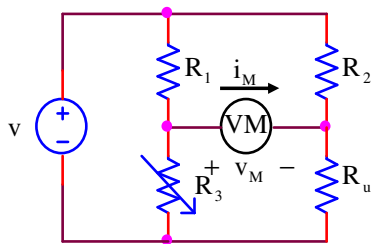


When Bridge is Balanced,  $i_M = 0$ ;  $v_M = 0$   
Meter Draws No Current

sawyes@rpi.edu

www.rpi.edu/~sawyes



## WHEATSTONE BRIDGE

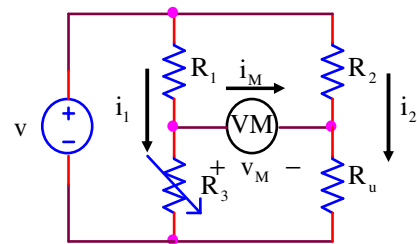


Bridge Balanced  
Solve for  $R_u$   $R_u = \frac{R_2 R_3}{R_1}$

sawyes@rpi.edu

www.rpi.edu/~sawyes



## THEVENIN'S THEOREM

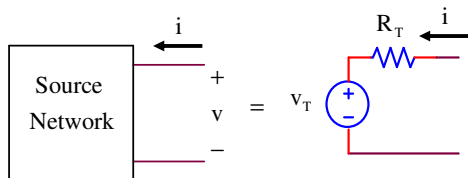

Any Source Network  
May be Replaced with its  
Thevenin Equivalent Circuit


$v_T$  = Thevenin Voltage  
 $R_T$  = Thevenin Resistance

sawyes@rpi.edu

www.rpi.edu/~sawyes



## THEVENIN'S THEOREM

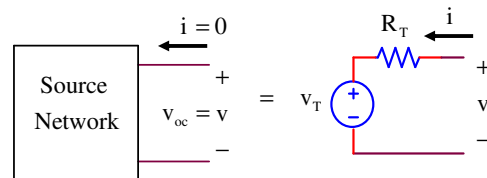


$v_T = v_{oc} = \text{Open Circuit Voltage}$   
 $v_T = v_{oc} = v$  when  $i = 0$   
 $R_T$  = Thevenin Resistance

sawyes@rpi.edu

www.rpi.edu/~sawyes



## NORTON'S THEOREM

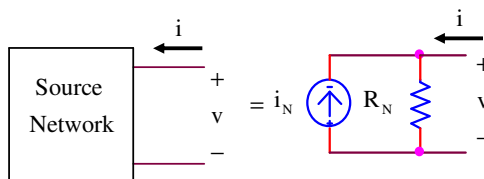

Any Source Network  
May be Replaced with its  
Norton Equivalent Circuit


$i_N$  = Norton Current  
 $R_N$  = Norton Resistance

sawyes@rpi.edu

www.rpi.edu/~sawyes



## NORTON'S THEOREM

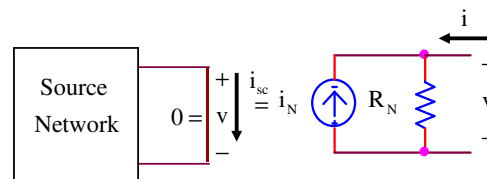


$i_N = i_{sc} = \text{Short Circuit Current}$   
 $i_N = i_{sc} = \text{Current Flowing from + to - when } v = 0$   
 $R_N$  = Norton Resistance

sawyes@rpi.edu

www.rpi.edu/~sawyes



## EQUIVALENT CIRCUITS

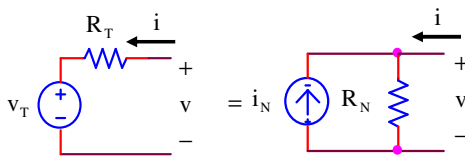

Thevenin Equivalent Circuit    Norton Equivalent Circuit

From Source Conversions:  $i_N = \frac{v_T}{R_T}$  and  $R_N = R_T$

$v_T = v_{oc}$  = Open Circuit Voltage

$i_N = i_{sc}$  = Short Circuit Current

sawyes@rpi.edu

www.rpi.edu/~sawyes



## THEVENIN/NORTON SOURCES-SOLVING PROCEDURE


1. **Thevenin** – Remove the load
  1. Find the voltage ( $V_{oc} = V_{TH}$ ) between the two nodes where the load was connected, using any method
2. **Norton** – Remove the load and connect a short circuit (wire) between the two nodes where the load was attached
  1. Find the current ( $I_{sc} = I_N$  through that short circuit (wire), using any method
  2. Note: the short circuit may 'combine' nodes. Recognize that you can do KCL at a node to find current through an individual wire connecting components.
3. **Resistance** – Remove the load
  1. Apply a test voltage source,  $V_{test}$ , at the nodes where the load was attached
  2. Short circuit all other independent voltage sources and open circuit all other independent current sources.
  3. Find the current through that source,  $I_{test}$
  4.  $R_{EO} = R_N = R_{TH} = V_{test}/I_{test}$
  4. Note: only two of these are needed since  $V_{TH} = (R_{TH})(I_N)$

sawyes@rpi.edu

www.rpi.edu/~sawyes



## MAXIMUM SIGNAL TRANSFER

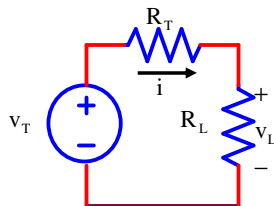

For Maximum Power Transfer; Choose  $R_L = R_T$   
Best You Can Do

sawyes@rpi.edu

www.rpi.edu/~sawyes



## REVIEW: LECTURE 6

- Amplifier circuit model
- Ideal Operational Amplifiers (Op Amps)

sawyes@rpi.edu

www.rpi.edu/~sawyes



## OPERATIONAL AMPLIFIERS


- An Operational Amplifier is a *High Gain Voltage Amplifier that can be used to perform **Mathematical Operations***:
  - Addition and Subtraction
  - Differentiation and Integration
  - Other Functions as Well
- Op Amps are the building blocks for many, many electronic circuits

sawyes@rpi.edu

www.rpi.edu/~sawyes



## OP AMP NOTATION

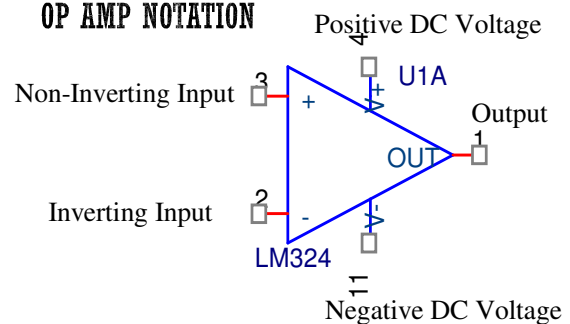


sawyes@rpi.edu

www.rpi.edu/~sawyes



## TRANSFER CHARACTERISTIC

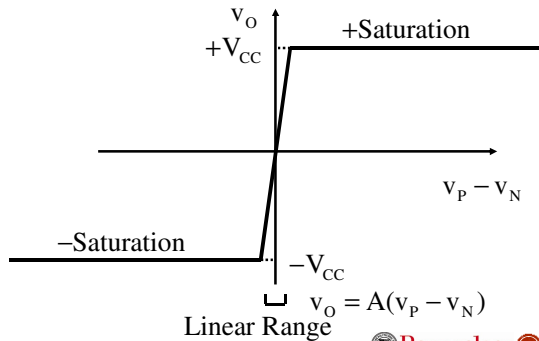


sawyes@rpi.edu

www.rpi.edu/~sawyes



## IDEAL OP AMP

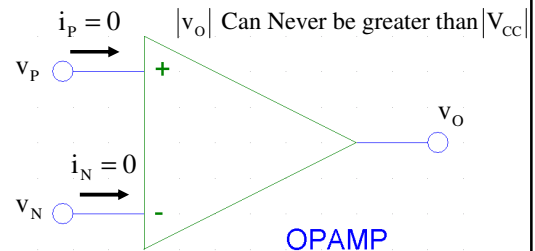

Since  $R_i \rightarrow \infty$ , Ideal Op Amp Draws No Current!


Since  $A \rightarrow \infty$ ,  $v_P = v_N$  in Linear Range

sawyes@rpi.edu

www.rpi.edu/~sawyes



## IDEAL OP AMP

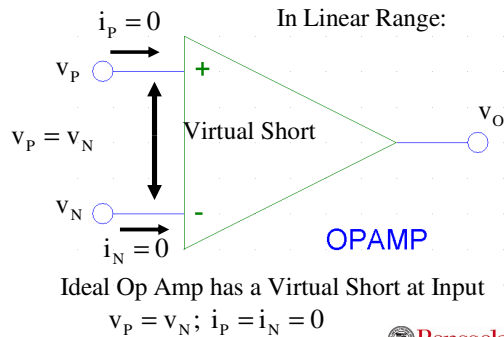


sawyes@rpi.edu

www.rpi.edu/~sawyes



## ZERO CROSSING DETECTOR

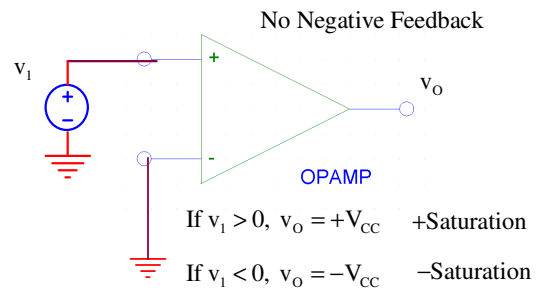


sawyes@rpi.edu

www.rpi.edu/~sawyes



## COMPARATOR

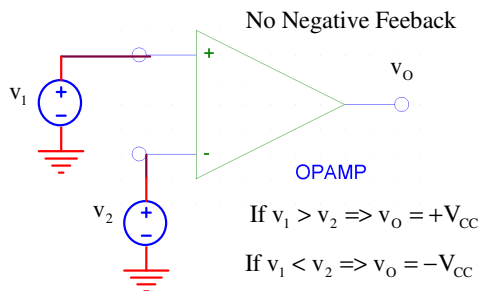

sawyes@rpi.edu

www.rpi.edu/~sawyes



## OP AMP CIRCUITS


- For most Op Amp circuits, we add negative feedback:
  - Circuit connection between  $v_O$  and  $v_N$
  - Helps to keep Op Amp in Linear Range
  - This will help keep  $v_P = v_N$
  - Output,  $v_O = A(v_P - v_N)$ , will be finite, as long as its magnitude is less than  $V_{CC}$
  - Output can never be greater than  $\pm V_{CC}$

sawyes@rpi.edu

www.rpi.edu/~sawyes



### VOLTAGE FOLLOWER

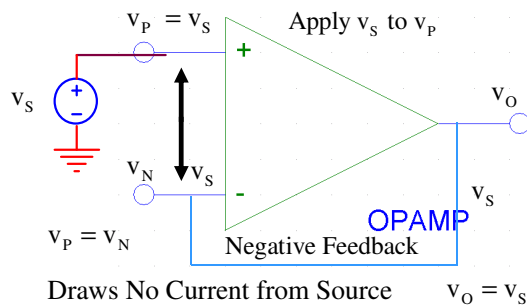


Draws No Current from Source  
Buffer, or Isolation Amplifier

sawyes@rpi.edu


www.rpi.edu/~sawyes



### INVERTING AMPLIFIER

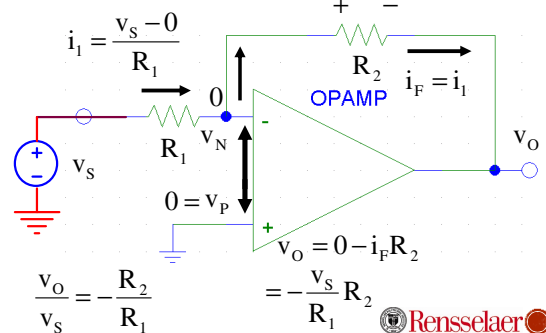

### NON-INVERTING AMPLIFIER

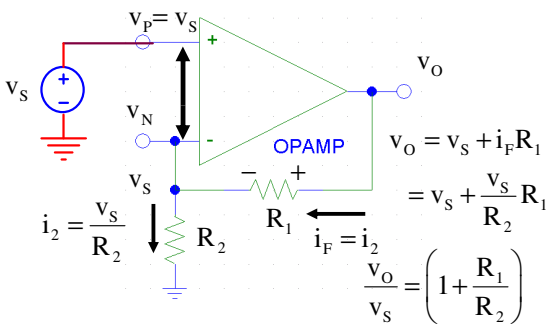


sawyes@rpi.edu

www.rpi.edu/~sawyes



### SUMMING AMPLIFIER

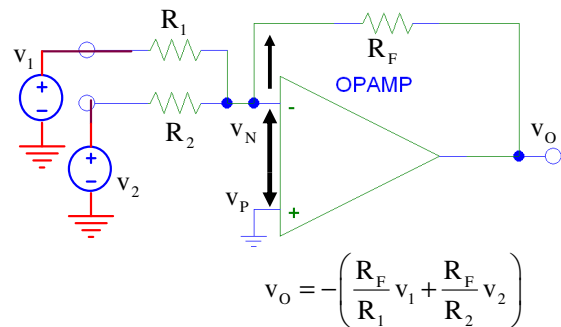


sawyes@rpi.edu

www.rpi.edu/~sawyes



### DIFFERENTIAL AMP

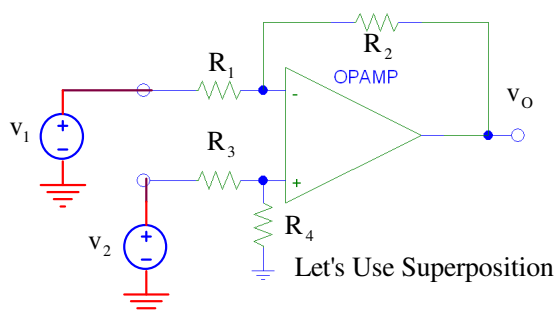

sawyes@rpi.edu

www.rpi.edu/~sawyes



### OP AMP CAD ILM

- Go to WebCT Site, Click on Modules
- Click on Op Amp CAD Module
- Move top slider to choose type of circuit
- Inverting, Non-Inverting Amplifier
- Differential Amplifier, Comparator
- Integrator, Differentiator (Later in Course)

[http://www.academy.rpi.edu/projects/ccli/module\\_display.php?ModulesID=11](http://www.academy.rpi.edu/projects/ccli/module_display.php?ModulesID=11)

sawyes@rpi.edu

www.rpi.edu/~sawyes



## UNIT 2

Transient Response: First Order/Second Order Circuits



## REVIEW: LECTURE 8


- Signals and waveforms
  - DC waveforms
  - Unit step functions
  - Ramp functions
  - Exponential functions
  - Sinusoidal functions

sawyer@rpi.edu


www.rpi.edu/~sawyer




### STEP FUNCTION

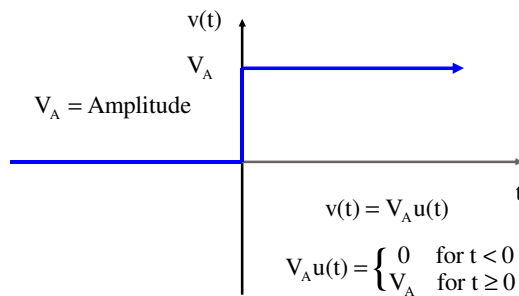

### DELAYED STEP FUNCTION

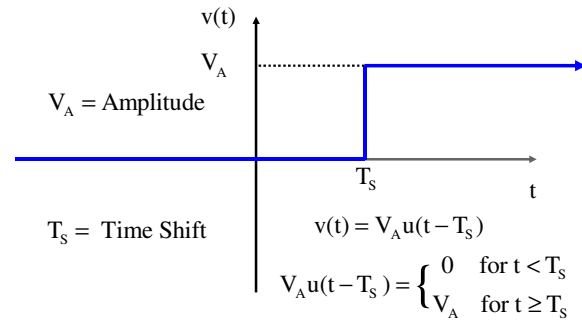

### EXPONENTIAL FUNCTION

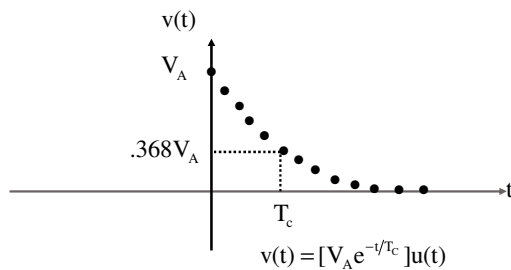

### SINUSOIDAL WAVEFORM

See Pages 219 - 226 Thomas and Rosa

$$v(t) = V_A \cos(\omega t + \phi)$$

<https://www.youtube.com/watch?v=QFi16s4RXXY>

Amplitude =  $V_A$ ; volts

Angular Frequency =  $\omega = 2\pi f$ ; radians/sec

$$f = \text{Frequency} = \frac{1}{T_0}; \text{ hertz}$$

[http://www.analyzema.com/unitcircle/unit\\_circle\\_applet.html](http://www.analyzema.com/unitcircle/unit_circle_applet.html)

$T_0$  = Period; seconds

$\phi$  = Phase Angle; degrees



## REVIEW: LECTURE 9

- First order RC and RL circuits
- Already a solved problem!
- Get RC and RL into the form of the solved problem
  - Find Thevenin Equivalent circuit
  - Find  $\tau$
- Find coefficients
  - Need  $t \rightarrow \infty$  and initial condition  $t=0+$

sawyer@rpi.edu

www.rpi.edu/~sawyer



## DYNAMIC CIRCUITS

$$y(t) = y_H + y_P$$

Homogeneous Response + Particular Response

$$y(t) = y_N + y_F$$

Natural Response + Forced Response

$$y_N = y_H; y_F = y_P$$

$$y(t) = y_{ZI} + y_{ZS}$$

Zero-Input Response + Zero-State Response



## RC CIRCUITS

Solution to Any Current or Voltage in Any Circuit Containing 1 C plus R's, Independent Sources and Dependent Sources, with a Switched DC Input:

$$y(t) = y_{SS} + (y_0 - y_{SS})e^{-(t-t_0)/\tau} \text{ for } t \geq t_0$$

$$\tau = R_{eq} C$$

Can Find  $y_0$ ,  $y_{SS}$ ,  $\tau$   
Directly From Circuit

$R_{eq}$  = Equivalent Resistance Seen at Terminals of C



## RL CIRCUITS

Solution to Any Current or Voltage in Any Circuit Containing 1 L plus R's, Independent Sources and Dependent Sources, with a Switched DC Input:

$$y(t) = y_{SS} + (y_0 - y_{SS})e^{-(t-t_0)/\tau} \text{ for } t \geq t_0$$

$$\tau = \frac{L}{R_{eq}}$$

Can Find  $y_0$ ,  $y_{SS}$ ,  $\tau$   
Directly From Circuit

$R_{eq}$  = Equivalent Resistance Seen at Terminals of L



## REVIEW: LECTURE 10


- Second order Series RLC and Parallel RLC
- Already solved problems!
- Get into standard form and find  $\alpha$ ,  $\omega_0$  and  $\beta$  (if needed)
- Compare  $\alpha$ ,  $\omega_0$  to find form of solution
- Find coefficients
- Need  $t \rightarrow \infty$  and initial conditions both  $V_C(0+)$  and  $dV_C(0+)/dt$  for example

sawyer@rpi.edu

www.rpi.edu/~sawyer



## SERIES RLC CIRCUITS

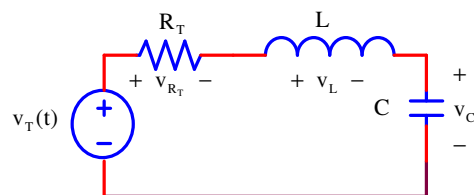

$$LC \frac{d^2 v_C}{dt^2} + R_T C \frac{dv_C}{dt} + v_C = v_T$$

$$\frac{d^2 v_C}{dt^2} + \frac{R_T}{L} \frac{dv_C}{dt} + \frac{1}{LC} v_C = \frac{1}{LC} v_T$$



## SERIES RLC CIRCUITS


$$\frac{d^2 v_C}{dt^2} + \frac{R_T}{L} \frac{dv_C}{dt} + \frac{1}{LC} v_C = \frac{1}{LC} v_T$$

$$\left[ \frac{1}{LC} \right] = \frac{1}{(\text{seconds})^2} = \omega_0^2 \quad \left[ \frac{R_T}{L} \right] = \frac{1}{\text{seconds}} = 2\alpha$$

$$\frac{d^2 v_C}{dt^2} + 2\alpha \frac{dv_C}{dt} + \omega_0^2 v_C = \omega_0^2 v_T$$



## SERIES RLC CIRCUITS

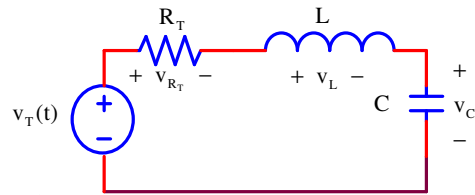

$$\frac{d^2 v_C}{dt^2} + 2\alpha \frac{dv_C}{dt} + \omega_0^2 v_C = \omega_0^2 v_T \quad \text{Need Initial Conditions}$$

$$v_C(0^+) \text{ and } \frac{dv_C}{dt}(0^+) \quad \frac{dv_C}{dt}(0^+) = \frac{1}{C} i_L(0^+)$$



## SERIES RLC CIRCUITS

$$\frac{d^2 v_{CN}}{dt^2} + 2\alpha \frac{dv_{CN}}{dt} + \omega_0^2 v_{CN} = 0$$

Assume  $v_{CN}(t) = K e^{st}$

$$s^2 + 2\alpha s + \omega_0^2 = 0$$

Characteristic Equation

Roots are  $s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$

$$v_{CN}(t) = K_1 e^{s_1 t} + K_2 e^{s_2 t}$$



## SERIES RLC CIRCUITS

$$s^2 + 2\alpha s + \omega_0^2 = 0$$

Roots are  $s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$

3 Possible Cases:

Case 1:  $\alpha^2 > \omega_0^2$ : 2 Real, Unequal Roots

Case 2:  $\alpha^2 = \omega_0^2$ : 2 Real, Equal Roots

Case 3:  $\alpha^2 < \omega_0^2$ : 2 Complex Conjugate Roots



## SERIES RLC CIRCUITS

Case 1:  $\alpha^2 > \omega_0^2$ : 2 Real, Unequal Roots

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \quad \alpha = \frac{R_T}{2L}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} \quad \omega_0^2 = \frac{1}{LC}$$

$$v_{CN} = K_1 e^{s_1 t} + K_2 e^{s_2 t}$$

2 Decaying Exponentials

Circuit is Overdamped



## SERIES RLC CIRCUITS

Case 2:  $\alpha^2 = \omega_0^2$ : 2 Real, Equal Roots

$$s_1 = -\alpha \quad \alpha = \frac{R_T}{2L} \quad \omega_0^2 = \frac{1}{LC}$$

$$s_2 = -\alpha$$

$$v_{CN} = K_1 e^{-\alpha t} + K_2 t e^{-\alpha t}$$

Decaying Exponential + Exponentially Damped Ramp

Circuit is Critically Damped



## SERIES RLC CIRCUITS

Case 3:  $\alpha^2 < \omega_0^2$  : 2 Complex Conjugate Roots

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -\alpha + j\sqrt{\omega_0^2 - \alpha^2} = -\alpha + j\beta$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -\alpha - j\sqrt{\omega_0^2 - \alpha^2} = -\alpha - j\beta$$

$$v_{CN} = K_1 e^{(-\alpha + j\beta)t} + K_2 e^{(-\alpha - j\beta)t}$$


$$v_{CN} = A e^{-\alpha t} \cos(\beta t + \phi)$$

Exponentially Damped Sinusoid

Circuit is Underdamped



## PARALLEL RLC CIRCUITS

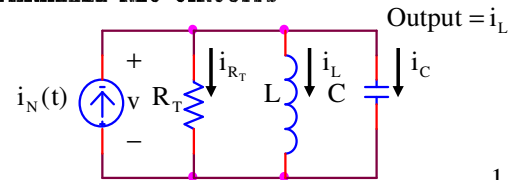

$$\frac{d^2 i_L}{dt^2} + 2\alpha \frac{di_L}{dt} + \omega_0^2 i_L = \omega_0^2 i_N$$

Same Form of Equation as for Series RLC

Slightly Different  $\alpha$

$$\alpha = \frac{1}{2R_T C}$$

$$\omega_0^2 = \frac{1}{LC}$$

sawyer@rpi.edu

www.rpi.edu/~sawyer



## PARALLEL RLC CIRCUITS

Parallel RLC Circuits

LHS of Differential Equation is Same for Any Output

Natural Response for Any Output

$$\frac{d^2 y_N}{dt^2} + 2\alpha \frac{dy_N}{dt} + \omega_0^2 y_N = 0$$

Same as for Series RLC Circuits

sawyer@rpi.edu

www.rpi.edu/~sawyer



## PARALLEL RLC CIRCUITS

Natural Response

$$\frac{d^2 y_N}{dt^2} + 2\alpha \frac{dy_N}{dt} + \omega_0^2 y_N = 0$$

Characteristic Equation

$$s^2 + 2\alpha s + \omega_0^2 = 0$$

Same Roots as for Series RLC

Overdamping, Critical Damping, Underdamping

sawyer@rpi.edu

www.rpi.edu/~sawyer



## REVIEW: LECTURE 12 AND 13

- Laplace transforms
- Finding poles and zeros
- Partial Fraction Expansion
  - Simple real poles
  - Complex conjugate poles
  - Double poles
- Relationship to differential equations
- S-domain impedances (zero and non-zero initial conditions)

sawyer@rpi.edu

www.rpi.edu/~sawyer



## LAPLACE TRANSFORMS

| Signal   | $f(t)$      | $F(s)$          |
|----------|-------------|-----------------|
| Impulse  | $\delta(t)$ | 1               |
| Step     | $u(t)$      | $\frac{1}{s}$   |
| Constant | $Au(t)$     | $\frac{A}{s}$   |
| Ramp     | $tu(t)$     | $\frac{1}{s^2}$ |

sawyer@rpi.edu

www.rpi.edu/~sawyer



## LAPLACE TRANSFORMS

| Signal        | $f(t)$                             | $F(s)$  |
|---------------|------------------------------------|---|
| Exponential   | $e^{-\alpha t}u(t)$                | $\frac{1}{s + \alpha}$                        |
| Damped Ramp   | $[te^{-\alpha t}]u(t)$             | $\frac{1}{(s + \alpha)^2}$                    |
| Cosine Wave   | $[\cos \beta t]u(t)$               | $\frac{s}{s^2 + \beta^2}$                     |
| Damped Cosine | $[e^{-\alpha t} \cos \beta t]u(t)$ | $\frac{s + \alpha}{(s + \alpha)^2 + \beta^2}$ |

sawyer@rpi.edu

www.rpi.edu/~sawyer



## LAPLACE TRANSFORMS

| Time Domain              | s-Domain            |
|--------------------------|---------------------|
| $Af_1(t) + Bf_2(t)$      | $AF_1(s) + BF_2(s)$ |
| $\int_0^t f(\tau) d\tau$ | $\frac{F(s)}{s}$    |
| $\frac{df(t)}{dt}$       | $sF(s) - f(0^-)$    |
| $e^{-\alpha t}f(t)$      | $F(s + \alpha)$     |
| $t f(t)$                 | $-dF(s)/ds$         |
| $f(t-a)u(t-a)$           | $e^{-as}F(s)$       |

sawyer@rpi.edu

www.rpi.edu/~sawyer



## POLES AND ZEROS

$$F(s) = \frac{b_m s^m + \dots + b_1 s + b_0}{a_n s^n + \dots + a_1 s + a_0}$$

Factor F(s):

$$F(s) = K \frac{(s - z_1)(s - z_2) \dots (s - z_m)}{(s - p_1)(s - p_2) \dots (s - p_n)}$$

$$K = \frac{b_m}{a_n} = \text{Scale Factor}$$

sawyer@rpi.edu

www.rpi.edu/~sawyer



## POLES AND ZEROS

$$F(s) = K \frac{(s - z_1)(s - z_2) \dots (s - z_m)}{(s - p_1)(s - p_2) \dots (s - p_n)}$$

At  $s = z_i \Rightarrow F(s) \rightarrow 0 \Rightarrow$  Zeros of F(s)

At  $s = p_j \Rightarrow F(s) \rightarrow \infty \Rightarrow$  Poles of F(s)

Poles and Zeros are "Critical Frequencies" of F(s)


Useful to Plot "Pole-Zero Diagram" in s-plane

sawyer@rpi.edu

www.rpi.edu/~sawyer



## POLE-ZERO DIAGRAMS

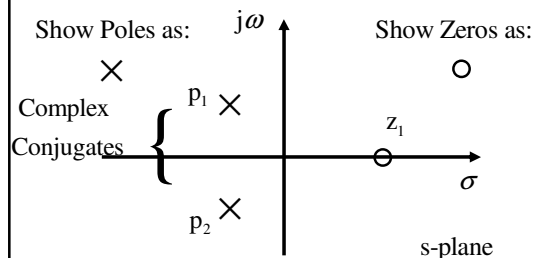

sawyer@rpi.edu

www.rpi.edu/~sawyer



## PARTIAL FRACTION EXPANSION

There are only 3 Types of Poles:

**Simple, Real Poles:**  $(s - 4)$ ,  $\Rightarrow p_1 = 4$

**Real, Equal Poles:**  $(s + 3)^2$ ,  $\Rightarrow p_1 = p_2 = -3$

**Complex Conjugate Poles:**  $(s^2 + 8s + 25)$   
 $\Rightarrow p_1, p_2 = -4 \pm j3$



## PARTIAL FRACTION EXPANSION

For  $m < n$ :

- Simple Real Poles

In General:

$$\text{Expand: } F(s) = \frac{A_1}{s-p_1} + \frac{A_2}{s-p_2} + \frac{A_3}{s-p_3} + \dots$$

$$A_n = [(s-p_n)F(s)]|_{s=p_n}; \quad \text{Cover-Up Rule}$$

$$\Rightarrow f(t) = (A_1 e^{p_1 t} + A_2 e^{p_2 t} + A_3 e^{p_3 t} + \dots) \quad t \geq 0$$



## PARTIAL FRACTION EXPANSION

- Complex Conjugate Poles

In General:

$$\text{Expand } F(s) = \frac{A_1}{s-p_1} + \dots + \frac{A}{s+\alpha-j\beta} + \frac{A^*}{s+\alpha+j\beta}$$

Find  $A_1$  and  $A = |A|/\phi$  from Cover-Up Rule

$$\Rightarrow f(t) = A_1 e^{p_1 t} + \dots + 2|A|e^{-\alpha t} \cos(\beta t + \phi) \quad t \geq 0$$

Simple Poles      Complex Poles



## PARTIAL FRACTION EXPANSION

- Real, Equal Poles – Double Pole:

$$\text{Expand } F(s) = \frac{A_1}{s-p_1} + \dots + \left[ \frac{A_{n1}}{s-p_n} + \frac{A_{n2}}{(s-p_n)^2} \right]$$

$$A_{n2} = [(s-p_n)^2 F(s)]|_{s=p_n}; \quad \text{Cover-Up Rule}$$

Usually Find  $A_{n1}$  from evaluating  $F(0)$  or  $F(1)$


$$\Rightarrow f(t) = (A_1 e^{p_1 t} + \dots + A_{n1} e^{p_n t} + A_{n2} t e^{p_n t}) \quad t \geq 0$$

Simple Poles      Repeated Poles



## IMPEDANCE

**Zero initial conditions**

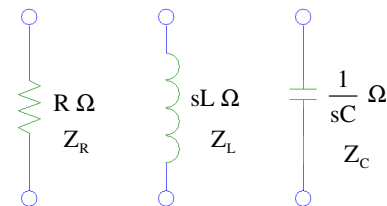


$$Z = \text{Impedance} = \frac{V(s)}{I(s)}$$

saeyes@rpi.edu

www.rpi.edu/~saeyes



## NON-ZERO INITIAL CONDITIONS

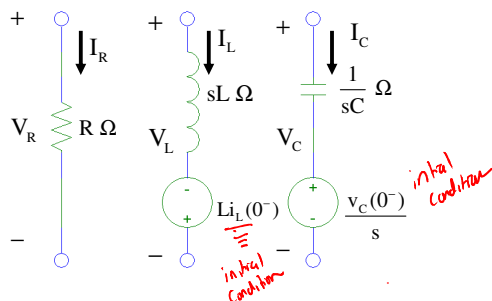

## REVIEW: LECTURE 14 CIRCUIT ANALYSIS


- Essentially Unit 1 + Unit 2 in one problem

saeyes@rpi.edu

www.rpi.edu/~saeyes



## GENERAL PROCESS

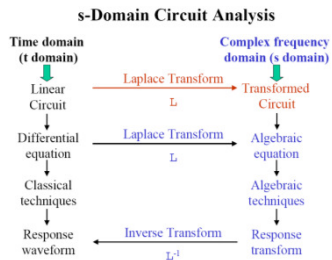

sawyer@rpi.edu

www.rpi.edu/~sawyer



## CIRCUITS WITH LAPLACE

1. Find Initial Conditions
2. Determine Laplace Equivalent circuit
3. Use Unit 1 concepts (node/mesh/voltage dividers etc.) to find an expression for the parameter of interest (impedances)
  - a. "Clean up" expression to have  $\frac{N(s)}{D(s)}$
4. Find poles (zeros, Unit 3)
5. Partial fraction expansion
  - a. Cover up rule for coefficients or  $F(0)$ ,  $F(1)$
6. Inverse Laplace gives time domain response



## UNIT 3

AC Steady State: Phasor Analysis and Power Circuits




## LECTURE 18.1 REVIEW

- Transfer Functions
- Phasors
- Phasor Math



## PHASORS

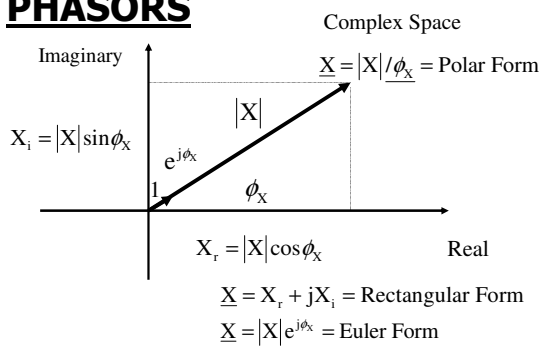

## PHASORS

- 3 Ways to Express Phasors
  - Rectangular Form;  $\underline{X} = X_r + jX_i$
  - Polar Form;  $\underline{X} = |X| \angle \phi_X$
  - Euler Form;  $\underline{X} = |X| e^{j\phi_X}$
- Will Need to Be Able to Easily Convert Between the 3 Different Forms



## LECTURE 19.1 AGENDA

- Kirkoff's laws for phasors
- AC steady state impedance



## K'S LAWS FOR PHASORS

- KCL:
  - If  $i_1 + i_2 = i$ ;  $\Rightarrow \underline{I}_1 + \underline{I}_2 = \underline{I}$
- KVL:
  - If  $v_1 + v_2 = v$ ;  $\Rightarrow \underline{V}_1 + \underline{V}_2 = \underline{V}$
- K's Laws Work for Phasors!
  - Complex Addition, not Simple Addition



## AC STEADY STATE IMPEDANCE

$$Z_R = R \Omega$$

$$Z_L = j\omega L \Omega$$

$$Z_C = -\frac{j}{\omega C} = \frac{1}{j\omega C} \Omega$$



## AC STEADY STATE IMPEDANCE

- In General,  $\underline{V} = \underline{Z} \underline{I}$  in AC Steady State:
  - $\underline{Z}$  = AC SS Impedance
  - Units of Ohms
  - Ohm's Law for AC Steady State
- $\underline{Y}$  = AC Steady State Admittance
  - =  $1/\underline{Z}$  (Units of mhos)



## AC STEADY STATE IMPEDANCE

$\underline{V} = \underline{Z} \underline{I}$ ; Ohm's Law for AC Steady State

$\underline{Z} = R(\omega) + jX(\omega)$  = AC Steady State Impedance

$R(\omega)$  = AC Steady State Resistance

$X(\omega)$  = AC Steady State Reactance

$\underline{Y} = G(\omega) + jB(\omega)$  = AC Steady State Admittance

$G(\omega)$  = AC Steady State Conductance

$B(\omega)$  = AC Steady State Susceptance



## LECTURE 20.1 AGENDA


- AC Thevenin/Norton circuits
- AC node equations
- ~~AC mesh equations (not on the test)~~
- ~~AC bridge circuits (not on the test)~~

saeyes@rpi.edu

www.rpi.edu/~saeyes



## EQUIVALENT IMPEDANCE

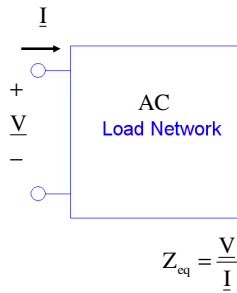


sawyes@rpi.edu

www.rpi.edu/~sawyes



## AC THEVENIN/NORTON

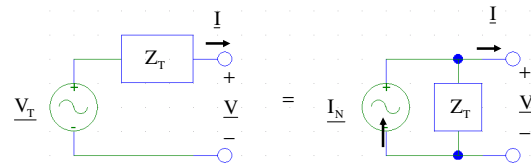

AC Thevenin Circuit

AC Norton Circuit

$$V_T = I_N Z_T$$


$$Z_T = Z_{eq} \text{ of Dead Source Network}$$

sawyes@rpi.edu

www.rpi.edu/~sawyes



## AC SOURCE CONVERSIONS

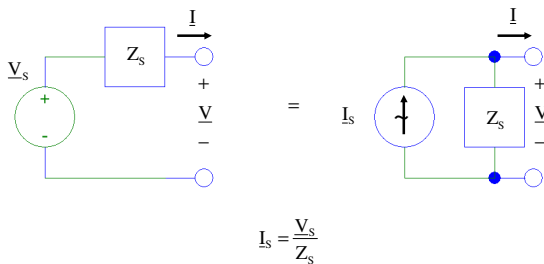

sawyes@rpi.edu

www.rpi.edu/~sawyes



## IMPEDANCE BRIDGES

Parallel voltage dividers

$$V_{.M} = V_{.A} - V_{.B} = \left( \frac{Z_{.2}}{Z_{.1} + Z_{.2}} \right) \cdot V_{.s} - \left( \frac{Z_{.u}}{Z_{.3} + Z_{.u}} \right) \cdot V_{.s}$$

$$V_{.M} = \left[ \frac{Z_{.2} \cdot Z_{.3} - Z_{.1} \cdot Z_{.u}}{(Z_{.1} + Z_{.2}) \cdot (Z_{.3} + Z_{.u})} \right] \cdot V_{.s}$$

**VM is zero when  $Z_2 Z_3 = Z_1 Z_u$**

$$Z_{.u} = \frac{Z_{.2} \cdot Z_{.3}}{Z_{.1}} = R_{.X} + jX_{.X}$$

sawyes@rpi.edu

www.rpi.edu/~sawyes



## LECTURE 21.1

- Review AC Power
  - Complex Power
  - Real Power
  - Reactive Power
  - Apparent Power
- Power Factor

sawyes@rpi.edu

www.rpi.edu/~sawyes



## REACTIVE POWER

$$\text{Define } P = \text{"Real Power"} = V_{\text{RMS}} I_{\text{RMS}} \cos \theta$$

P is Measured in Watts

$$\text{Define } Q = \text{"Reactive Power"} = V_{\text{RMS}} I_{\text{RMS}} \sin \theta$$

Q is Measured in VAR's

(Volt-Amperes-Reactive)



## REACTIVE POWER

- **Q is a Measure of the Rate of Change of Energy Stored in the Reactive Elements (L, C):**

- **Power companies must worry about Q since they supplied this energy**
- **Supplied Q over their Lines => Real Cost**
- **Power companies want customers to have Low Q**



## REACTIVE POWER

$$\begin{aligned} P &= I_{\text{RMS}}^2 |Z| \cos \theta \\ &= I_{\text{RMS}}^2 R(\omega) \\ &= V_{\text{RMS}} I_{\text{RMS}} \cos \theta \end{aligned} \quad \left\{ \begin{array}{l} \text{Equivalent ways of} \\ \text{expressing Real Power} \end{array} \right. \quad [\text{Watts}]$$

$$\begin{aligned} Q &= I_{\text{RMS}}^2 |Z| \sin \theta \\ &= I_{\text{RMS}}^2 X(\omega) \\ &= V_{\text{RMS}} I_{\text{RMS}} \sin \theta \end{aligned} \quad \left\{ \begin{array}{l} \text{Equivalent ways of} \\ \text{expressing Reactive Power} \end{array} \right. \quad [\text{VAR's}]$$



## REACTIVE POWER

- **Notes on Reactive Power:**

- **Real Power = P is always  $\geq 0$**
- **Reactive Power = Q can be  $\geq 0$  or  $\leq 0$**
- **For Inductive Load,  $X > 0 \Rightarrow Q > 0$**
- **For Capacitive Load,  $X < 0 \Rightarrow Q < 0$**



## APPARENT POWER


$$\text{Magnitude of } \underline{S} = |\underline{S}| = \sqrt{P^2 + Q^2} = V_{\text{RMS}} I_{\text{RMS}}$$

$$|\underline{S}| = \text{"Apparent Power"} \Rightarrow [\text{Volt-Amperes}]$$


$$|\underline{S}| = \text{Product of } V_{\text{RMS}} \times I_{\text{RMS}} \text{ at Terminals}$$



## POWER TRIANGLE

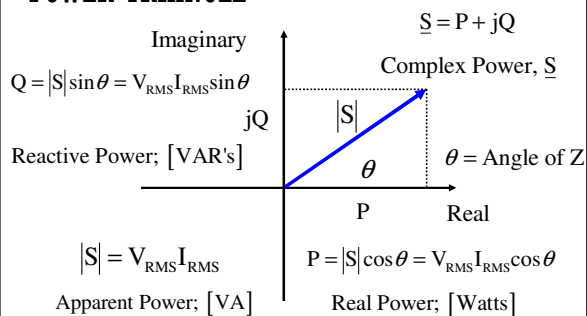

## POWER FACTOR

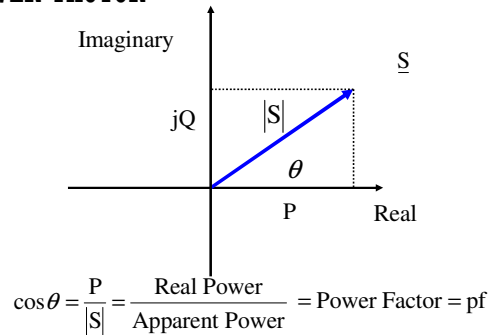

## POWER FACTOR

For Inductive Loads,  $\theta > 0$ ;  $\cos \theta > 0$

For Capacitive Loads,  $\theta < 0$ ;  $\cos \theta > 0$

Need a Way to Distinguish

$$\underline{I} = \frac{\underline{V}}{\underline{Z}} = \frac{|\underline{V}| \angle \phi}{|\underline{Z}| \angle \theta} = \frac{|\underline{V}|}{|\underline{Z}|} \angle \phi - \theta$$

If  $\theta > 0$ ;  $\Rightarrow$  Lagging Power Factor ( $\underline{I}$  lags  $\underline{V}$ )

If  $\theta < 0$ ;  $\Rightarrow$  Leading Power Factor ( $\underline{I}$  leads  $\underline{V}$ )



## POWER FACTOR

Power Factor:

Define  $\text{pf} = \cos \theta$ ;  $0 \leq \text{pf} \leq 1$

Must distinguish between  $\theta \geq 0$ ,  $\theta \leq 0$ :

$\theta \geq 0$ ;  $X \geq 0$ ;  $Q \geq 0$ ;  $\underline{I}$  lags  $\underline{V}$ ; lagging pf

$\theta \leq 0$ ;  $X \leq 0$ ;  $Q \leq 0$ ;  $\underline{I}$  leads  $\underline{V}$ ; leading pf

e.g:  $\text{pf} = .8$  lagging  $\Rightarrow$  Inductive Load

$\text{pf} = .8$  leading  $\Rightarrow$  Capacitive Load



## LECTURE 22.1


- Coupled Inductors
- Ideal Transformer
- Transformer Circuit
- Power Transfer
- Impedance Matching
- Mutual Inductance (Tee Model)

sawyer@rpi.edu

www.rpi.edu/~sawyer



## TRANSFORMER CIRCUIT

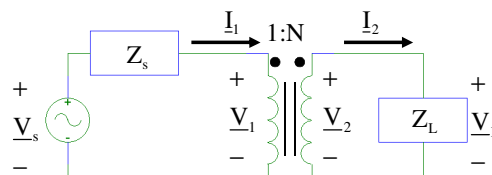

2 Choices for the Equivalent Circuit

Refer Secondary Circuit to the Primary

OR


Refer Primary Circuit to the Secondary

sawyer@rpi.edu

www.rpi.edu/~sawyer



## REFERRAL TO PRIMARY

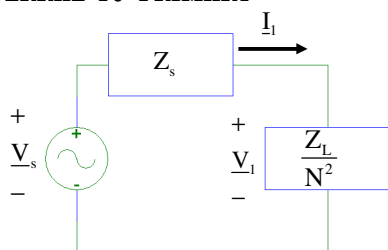

Equivalent to Basic Transformer Circuit


Can Now Do AC Steady State Circuit Analysis

sawyer@rpi.edu

www.rpi.edu/~sawyer



## REFERRAL TO SECONDARY

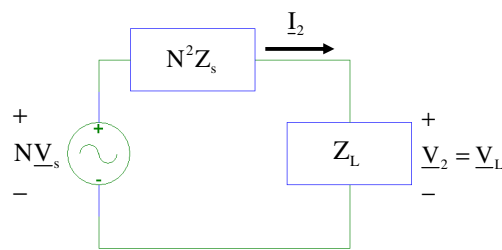

Equivalent to Basic Transformer Circuit


Can Now Do AC Steady State Circuit Analysis

sawyer@rpi.edu

www.rpi.edu/~sawyer



## POWER TRANSFER

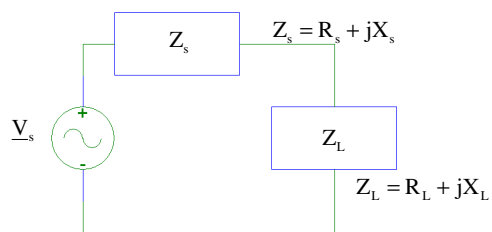


For Maximum Power to  $Z_L$  Choose  $Z_L = Z_s^*$   
 $\Rightarrow R_L = R_s$  and  $X_L = -X_s$

sawyer@rpi.edu

www.rpi.edu/~sawyer



## MUTUAL INDUCTANCE

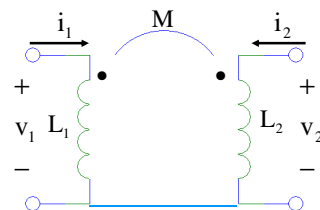


$$v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$v_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$



## TEE MODEL

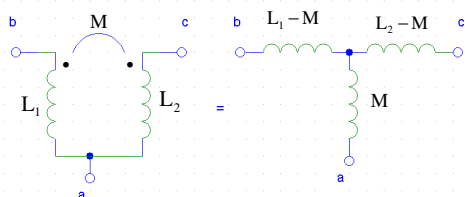

Transformer-like Model

Tee Model

If Dots on Opposite Sides  $\Rightarrow M \rightarrow -M$

Some Inductors in Tee Model May Be Negative!




## UNIT 4

AC Steady State: Frequency Response



## 1<sup>st</sup> ORDER LOW PASS FILTER

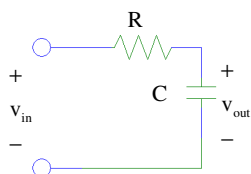


$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{1/RC}{s + 1/RC} = \frac{\omega_c}{s + \omega_c} \Rightarrow \text{Low Pass Filter}$$

Low Frequencies "Pass"; High Frequencies "Stopped"



## 1<sup>st</sup> ORDER HIGH PASS FILTER

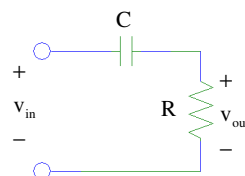

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{s}{s + 1/RC} = \frac{s}{s + \omega_c} \Rightarrow \text{High Pass Filter}$$

High Frequencies "Pass"; Low Frequencies "Stopped"



### LOW PASS + HIGH PASS

$$H(s) = K \left( \frac{s}{s + \omega_{CH}} \right) \left( \frac{\omega_{CL}}{s + \omega_{CL}} \right)$$

$$|H(j\omega)| = |K| \left( \frac{\omega}{\sqrt{\omega^2 + \omega_{CH}^2}} \right) \left( \frac{\omega_{CL}}{\sqrt{\omega^2 + \omega_{CL}^2}} \right)$$


High Pass Low Pass

Let's Design Such that  $\omega_{CL} > \omega_{CH}$

$$\Rightarrow R_H C_H > R_L C_L$$



### BANDPASS FILTER

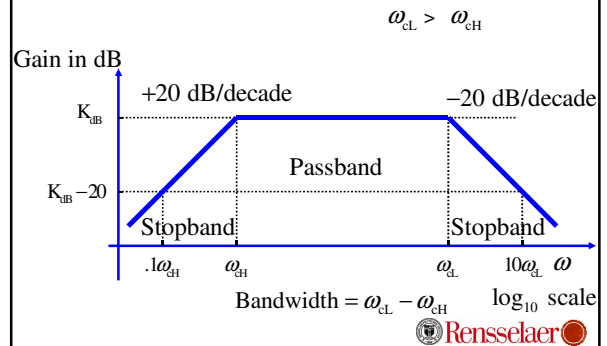

### LOW PASS + HIGH PASS

$$H(s) = H_L(s) + H_H(s) = \left( 1 + \frac{R_A}{R_B} \right) \left( \frac{\omega_{CL}}{s + \omega_{CL}} + \frac{s}{s + \omega_{CH}} \right)$$

For Low Frequencies  $\Rightarrow$  Looks Like a 1<sup>st</sup> Order Low Pass


For High Frequencies  $\Rightarrow$  Looks Like a 1<sup>st</sup> Order High Pass

Let's Design Such that  $\omega_{CH} > \omega_{CL}$

$$\Rightarrow R_L C_L > R_H C_H$$



### BANDGAP OR NOTCH FILTER

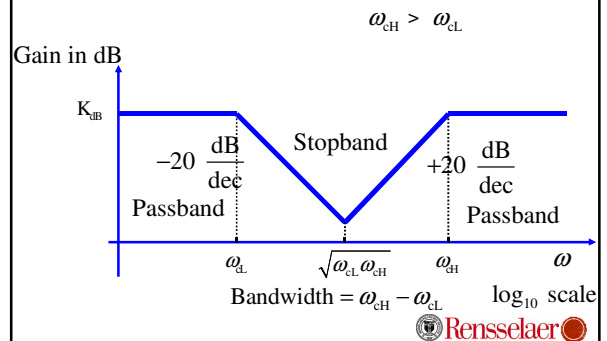

### 2<sup>ND</sup> ORDER PROCESS SUMMARY

#### Overdamped

- 1) Find Poles
- 2) Identify Regions
- 3) Build Straight Line Approximations
- 4) Add corrections (-3db)



### 2<sup>ND</sup> ORDER PROCESS SUMMARY

#### Critically Damped

- 1) Find Poles
- 2) Identify Regions
- 3) Build Straight Line Approximations
- 4) Add corrections (-6db)



## 2<sup>ND</sup> ORDER PROCESS SUMMARY

### Underdamped LPF, HPF

- 1) Start with critically damped case  $\omega_c = \omega_o$
- 2) Sketch Straight Line Approximations away from  $\omega_o$
- 3) At  $\omega_o$   $20 \log \text{abs } H(j \omega_o) = 20 \log(1/(2 \zeta)) > -6 \text{ dB}$  relative to passband



## 2<sup>ND</sup> ORDER PROCESS SUMMARY

### Underdamped BPF

1. Asymptotes take the form of inverted V
2. Each side of V has 20 dB rolloff
3. At  $\omega_o$   $20 \log \text{abs } H(j \omega_o) = 0 \text{ dB}$  ALWAYS
4. The point of the inverted V is  $20 \log \text{abs } H(j \omega_o)$  away from 0dB
5. Use  $20 \log(2 \zeta)$  to find this point pulling V up or down relative to 0dB making it narrow or wide



## FILTER TYPE SUMMARY (FROM H(S))

- **First order filters**
  - Low pass: (no zeros), 1 pole
  - High pass: 1 zero at origin, 1 pole
- **Second order filters**
  - Low pass: 2 poles
  - High pass: 2 zeros at origin, 2 pole
  - Bandpass filter: 1 zero, 2 poles
  - Notch filter:



## DAMPING RATIO

$$\zeta = \alpha / \omega$$

- $\zeta > 1$  Overdamped
- $\zeta = 1$  Critically damped
- $\zeta < 1$  Underdamped
  - $1 > \zeta > 0.5$  Correction is a -db of some value
  - $\zeta = 0.5$  Correction is 0db
  - $\zeta < 0.5$  Correction is +db (Strongly underdamped which means there is a peak!)

sawyer@rpi.edu

www.rpi.edu/~sawyer



Congratulations, you are officially  
**electrical engineering students!**

Now you must become **electrical  
engineers/computer systems  
engineers/dual major  
engineers**.....may the  
(electromagnetic) Force be with you...

sawyer@rpi.edu

www.rpi.edu/~sawyer

