Questions: What do I need to know about this class? What is voltage? What is a voltage difference/voltage drop? What is current? What is polarity? How do we define power? What is a circuit model? What is a ground? What is the IV characteristic of an open circuit? a short circuit? an ideal voltage source? an ideal current source? a resistor? a diode? What is Ohm's Law? What is a node in a circuit? What is a closed loop in a circuit? How do we apply Kirchhoff's Voltage Law (KVL)? Kirchhoff's Current Law (KCL)?



Node 2





Assign polarities to each resistor and apply KCL or KVL to obtain three independent expression for the voltage across each resistor

VR1 = VR2 = VR3 = 6V

-///-3k R1

R3

Ŵ

1k

R2 [₹] 2k



Node 2

Node 1



Ask about polarity

Assign polarities to each resistor and apply KCL or KVL to obtain three independent expressions for the voltage across each resistor

$$R_{1c} \coloneqq 3k\Omega$$
$$R_{2c} \coloneqq 2k\Omega$$
$$R_{3c} \coloneqq 1k\Omega$$

Do KVL

$$-6 + V_{R1c} + V_{R2c} + V_{R3c} = 0$$

Then do KCL at nodes

$$i_{1c} - i_{2c} = 0$$

substitute ohms law

$$\frac{V_{R1c}}{R_{1c}} - \frac{V_{R2c}}{R_{2c}} = 0$$

Node 2

$$\frac{V_{R2c} - i_{3c} = 0}{R_{2c}} - \frac{V_{R3c}}{R_{3c}} = 0$$

solve for VR1c and VR3c (get in terms of VR2c

$$V_{R1c} = \frac{V_{R2c}}{R_{2c}} \cdot R_{1c}$$
$$V_{R3c} = \frac{R_{3c} \cdot V_{R2c}}{R_{2c}}$$

Put in KVL equation

$$\frac{-6 + \frac{R_{1c} \cdot V_{R2}}{R_{2c}} + \frac{R_{3c} \cdot V_{R2}}{R_{2c}} + V_{R2} = 0$$

$$\frac{6 \cdot R_{2c}}{R_{1c} + R_{2c} + R_{3c}} = 2 \qquad V_{R2c} := 2$$

Do the matrix!

$$V_{R1c} + V_{R2c} + V_{R3c} = 6$$

$$\frac{1}{R_{1c}} \cdot V_{R1c} - \frac{1}{R_{2c}} \cdot V_{R2c} + 0 = 0$$

$$0 + \frac{1}{R_{2c}} \cdot V_{R2c} - \frac{1}{R_{3c}} \cdot V_{R3c} = 0$$

$$M_{1} := \begin{pmatrix} 1 & 1 & 1 \\ \frac{1}{3 \cdot 10^{3}} & \frac{-1}{2 \cdot 10^{3}} & 0 \\ 0 & \frac{1}{2 \cdot 10^{3}} & \frac{-1}{1 \cdot 10^{3}} \end{pmatrix}$$

$$C_{1} := \begin{pmatrix} 6 \\ 0 \\ 0 \end{pmatrix}$$

$$X_{1} := M_{1}^{-1} \cdot C_{1}$$

$$X_{1} = \begin{pmatrix} 3 \\ 2 \\ 1 \end{pmatrix}$$

$$V_{R1c} = 3$$

$$V_{R2c} = 2$$

$$V_{R3c} = 1$$

3 of 10

Electric Circuits ECSE 2010

To find VR3

 $V_{R3c} \coloneqq \frac{R_{3c}}{R_{2c}} \cdot V_{R2c}$

$$V_{R3c} = 1$$

To find VR1

$$V_{R1c} := \frac{R_{1c} \cdot V_{R2c}}{R_{2c}}$$

$$V_{R1c} = 3$$



Assign polarities to each resistor and apply KCL and/or KVL to obtain three independent expression for the voltage across each resistor



Solve first

equation

for VR1d

At node 1

$$R_{1d} \coloneqq 4k\Omega \qquad R_{2d} \coloneqq 2k\Omega \qquad R_{3d} \coloneqq 1k\Omega \qquad I_{1d} \coloneqq 2mA$$

$$I_{2d} \coloneqq 1mA$$

(2)
$$I_{R2d} - I_{2d} - I_{R3d} = 0$$
 or

 $V_{R1d} = \frac{R_{1d} \cdot V_{R3d} + I_{1d} \cdot R_{1d} \cdot R_{2d}}{R_{1d} + R_{2d}}$

Put in (2) equation

Solve for VR3

$$\frac{V_{R1d} - V_{R3d}}{R_{2d}} - I_{2d} \cdot -\frac{V_{R3d}}{R_{3d}} = 0$$

Also need loop to solve matrix equation!

(3)
$$-V_{R1d} + V_{R2d} + V_{R3d} = 0$$

So put all equations together

$$-V_{R1d} + V_{R2d} + V_{R3d} = 0$$

$$-\left(\frac{1}{R_{1d}} + \frac{1}{R_{2d}}\right) \cdot V_{R1d} + 0 + \frac{1}{R_{2d}} \cdot V_{R3d} = -2$$
$$\frac{1}{R_{2d}} \cdot V_{R1d} + 0 - \left(\frac{1}{R_{2d}} + \frac{1}{R_{3d}}\right) \cdot V_{R3d} = 1$$

$$\frac{I_{2d} \cdot R_{1d} \cdot R_{3d} - I_{1d} \cdot R_{1d} \cdot R_{3d} + I_{2d} \cdot R_{2d} \cdot R_{3d}}{R_{1d} + R_{2d} + R_{3d}} = 285.714 \cdot \text{mV}$$

 $\frac{-V_{R3d} + \frac{R_{1d} \cdot V_{R3d} + I_{1d} \cdot R_{1d} \cdot R_{2d}}{R_{1d} + R_{2d}}}{R_{2d}} - I_{2d} - \frac{V_{R3d}}{R_{3d}} = 0$

$$V_{R3d} \coloneqq 285.7 mV$$

Put VR3d in equation (3)

 $V_{R1d} \coloneqq \frac{R_{1d} \cdot V_{R3d} + I_{1d} \cdot R_{1d} \cdot R_{2d}}{R_{1d} + R_{2d}}$ $V_{R1d} = 2.857 V$

To find the voltage across R2d you subtract the node 1 from node 2 voltages.

$$V_{R1d} - V_{R3d} = 2.571 V$$

$$M_{2} := \begin{bmatrix} -1 & 1 & 1 \\ -\left(\frac{1}{4 \cdot 10^{3}} + \frac{1}{2 \cdot 10^{3}}\right) & 0 & \frac{1}{2 \cdot 10^{3}} \\ \frac{1}{2 \cdot 10^{3}} & 0 & -\left(\frac{1}{2 \cdot 10^{3}} + \frac{1}{1 \cdot 10^{3}}\right) \end{bmatrix}$$
$$C_{2} := \begin{bmatrix} 0 \\ -2 \cdot 10^{-3} \\ 1 \cdot 10^{-3} \end{bmatrix}$$
$$X_{2} := M_{2}^{-1} \cdot C_{2}$$
$$X_{2} = \begin{bmatrix} 2.857 \\ 2.571 \\ 0.286 \end{bmatrix}$$