


Questions:

What is superposition?

What is a dependent source?

Mesh/Node again


a)

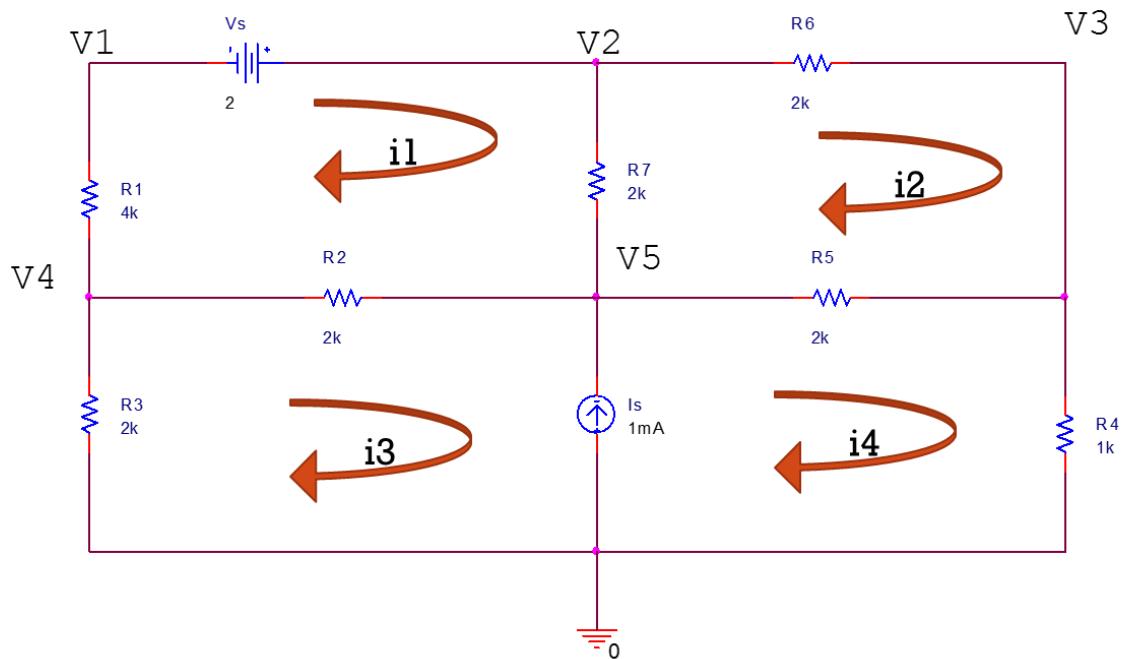

1. Using the labeled nodes and mesh loops, determine the linear equations for both methods.
2. Solve using both mesh and node equations  
*(Answer:  $V_1 = -0.57\text{V}$ ,  $V_2 = 1.42\text{V}$ ,  $V_3 = 0.74\text{V}$ ,  $V_4 = 0.51\text{V}$ ,  $V_5 = 1.56\text{V}$ ,  $V_6 = 0\text{V}$ )*  
*(Answer:  $i_1 = 0.27\text{mA}$ ,  $i_2 = 0.34\text{mA}$ ,  $i_3 = -0.25\text{mA}$ ,  $i_4 = 0.75\text{mA}$ )*
3. Determine the voltage across  $R_7$   
*(Answer:  $V_{R7} = 0.13\text{V}$ )*


b)

Superposition

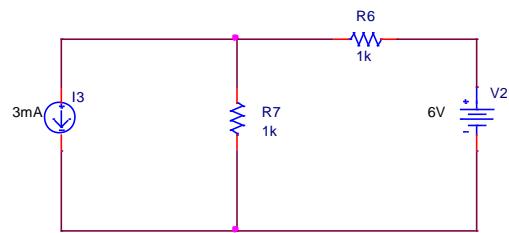

1. Draw the superposition circuit for each source
2. Use superposition to determine the voltage across  $R_7$  (Answer:  $V_{TOT}=V_{V2}+V_{I3}=-2V$ )


c)

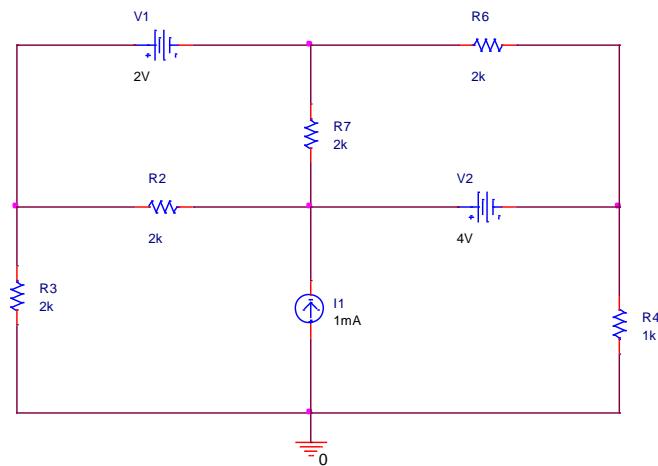

1. Apply superposition to the circuit above to find  $V_{R7}$   
(Answer:  $V_{TOT}=V_{V1}+V_{V2}+V_{I1}=0.91 - 1.81 - 0.182 = -1.078 \text{ V}$ )

Dependent sources

d)

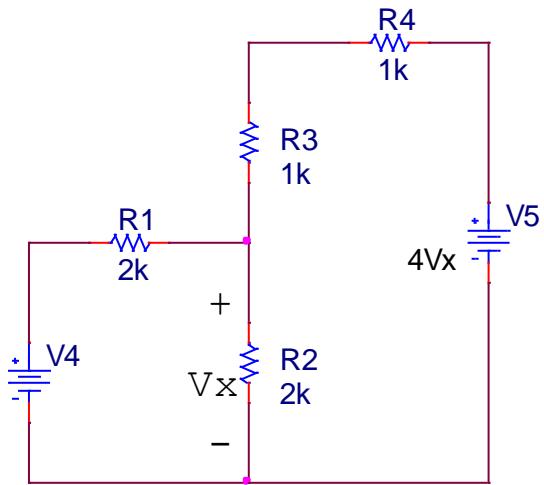

1. Determine the voltage  $V_5$  when  $V_4 = 1$  [V]
2. Determine the voltage  $V_5$  when  $V_4 = 2$  [V]
3. Determine the voltage  $V_5$  when  $V_4 = 4$  [V]