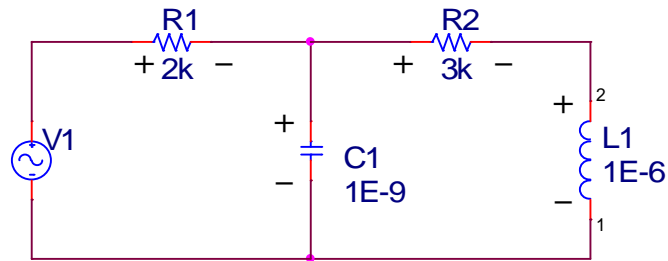


### Voltage/Current continuity

1) In the circuit below, the voltage source is defined as follows:

$$V_s = \begin{cases} 0 & t < 0 \\ 10V & 0 < t \end{cases} \quad (\text{the voltage source turns on at } t = 0)$$




a. What are the initial conditions for the circuit?

b. Determine the mathematical expression for the source.

c. At  $t = 0^+$ , (just after the voltage source turns on), for the polarities indicated in the circuit, determine the voltage across each component and the current through each component.

d. At  $t$  goes to  $\infty$ , the polarities indicated in the circuit, determine the voltage across each component and the current through each component.


2) RC series circuit

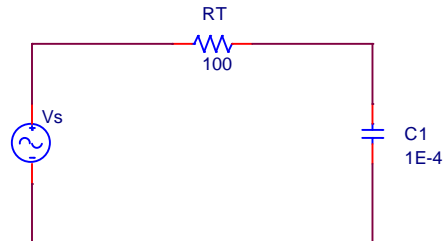

a) Exponential source input

$$v_s(t) = 5e^{-50t}u(t)$$

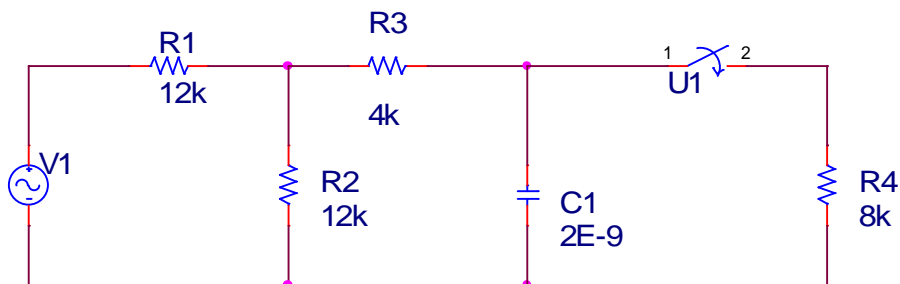3) Circuit Analysis and Thevenin/Norton Circuits



In the above circuit,

1. The voltage source turns on at  $t=0$  with a voltage of 20V
2. Switch U1 closes at  $15E-6s$
3. The voltage source turns off at  $t = 25E-6$

a. Determine the voltage across C1 as a function of time for  $t > 0$ .

For  $0 < t < 15\text{E-}6$

For  $15\text{E-}6\text{s} < t < 25\text{E-}6$

For  $t > 25\text{E-}6$