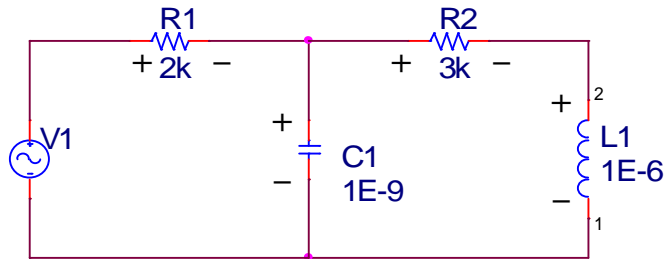


Voltage/Current continuity

1) In the circuit below, the voltage source is defined as follows:

$$V_s = \begin{cases} 0 & t < 0 \\ 10V & 0 < t \end{cases} \quad (\text{the voltage source turns on at } t = 0)$$



a. What are the initial conditions for the circuit?


The source is zero for $t < 0$, indicating that the initial conditions are zero.

b. Determine the mathematical expression for the source.

$$V_s = 10u(t)$$

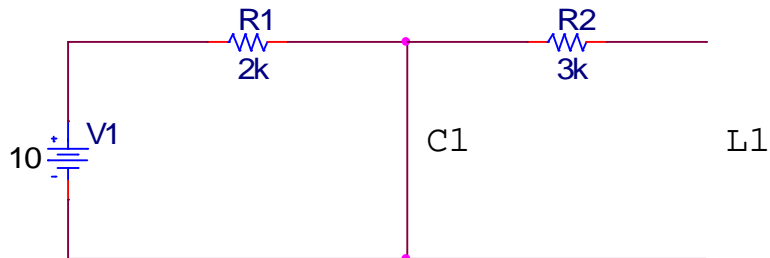c. At $t = 0^+$, (just after the voltage source turns on), for the polarities indicated in the circuit, determine the voltage across each component and the current through each component.

At $t = 0^+$, the source is 10V. We enforce the continuity condition for inductors to get $I_L(0^+) = I_L(0^-)$ and for capacitors $V_C(0^+) = V_C(0^-)$. Since the initial conditions are zero, the current through the inductor at $t = 0^+$, must be zero, effectively an open circuit and the voltage across the capacitor at $t = 0^+$ must be zero, effectively a short circuit. The $t = 0^+$ circuit can be drawn as




Circuit analysis gives the following results

Component	Voltage	Current
R1	10 V	5mA
R2	0	0
C1	0 (continuity)	5mA
L1	0	0 (continuity)

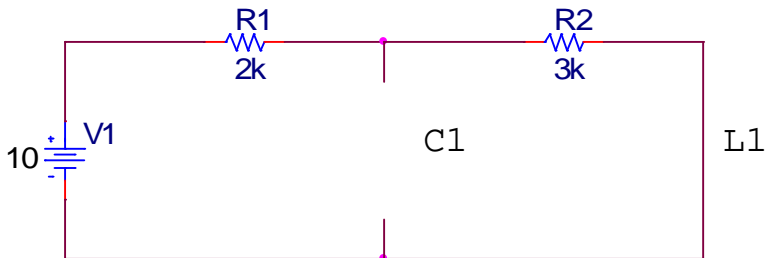d. At $t \rightarrow \infty$, the polarities indicated in the circuit, determine the voltage across each component and the current through each component.

As $t \rightarrow \infty$ for a step function source, we approach the DC steady state conditions. At DC steady state, a capacitor acts as an open circuit and an inductor acts as a short circuit.

When $t \rightarrow \infty$ the circuit can be drawn as



Circuit analysis gives the following results

Component	Voltage	Current
R1	4 V	2mA
R2	6 V	2mA
C1	6 V	0 (open circuit)
L1	0 (short circuit)	2mA

Voltage across R1 is a voltage divider

$$10V \cdot \frac{2k\Omega}{2k\Omega + 3k\Omega} = 4 \text{ V}$$

$$I_{R1} := \frac{4V}{2k\Omega} = 2 \text{ mA}$$

Voltage across R2 is a voltage divider

$$10V \cdot \frac{3k\Omega}{2k\Omega + 3k\Omega} = 6 \text{ V}$$

$$I_{R2} := \frac{6V}{3k\Omega} = 2 \text{ mA}$$

Voltage across capacitor

Same a voltage across R2 = 6V

$$I_{C1} := 0 \text{ mA} \quad (\text{open circuit})$$

Voltage across the inductor

I_{IL} is the same as the current through R1 and R2

$V_{L1} := 0$ short circuit

$I_{IL} := I_{R1} = 2 \text{ mA}$

2) RC series circuit




a) Exponential source input

$t := 0, 0.001 \dots 0.2$

$$v_s(t) = 5e^{-50t} u(t)$$

$$v_s(t) := 5 \cdot e^{-50t}$$

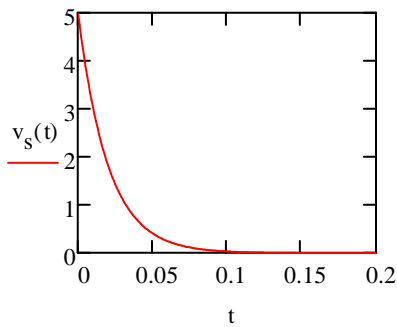

exponential source that turns on at $t = 0$

Initial conditions

$$v_c(0^-) = 0 \quad \text{still this way because of the step function}$$

$$v_c(t) = A_1 \cdot e^{\frac{-t}{\tau}} + A_2 \cdot e^{-50t} \quad \text{VCF must look like input}$$

V_{CN} + V_{CF}

$$v_c(t) = A_1 \cdot e^{-100t} + A_2 \cdot e^{-50t}$$

$$\tau := 100 \cdot 1 \times 10^{-4}$$

$$\tau = 0.01 \quad \frac{1}{\tau} = 100$$

Find A_2 coefficient from differential equation for a particular solution

substitute VCF into diff eq. formed by KVL

$$RC \frac{dv_{CF}}{dt} + v_{CF} = V_s$$

$$0.01 \cdot \frac{d}{dt} (A_2 \cdot e^{-50t}) + A_2 \cdot e^{-50t} = 5 \cdot e^{-50t}$$

$$-0.5 \cdot A_2 \cdot e^{-50t} + A_2 \cdot e^{-50t} = 5 \cdot A_2 \cdot e^{-50t}$$

Divide out e^{-50t}

$$-0.5A_2 + A_2 = 5$$

$$A_2 \cdot (-0.5 + 1) = 5$$

$$A_2 = 10$$

Find A1 using initial conditions


$$v_C(t) = A_1 \cdot e^{-100t} + 10 \cdot e^{-50t}$$

$$v_C(0^-) = v_C(0^+) = 0$$

$$v_C(t) := -10e^{-100t} + 10e^{-50t}$$


$$A_1 + 10 = 0$$

$$A_1 = -10$$

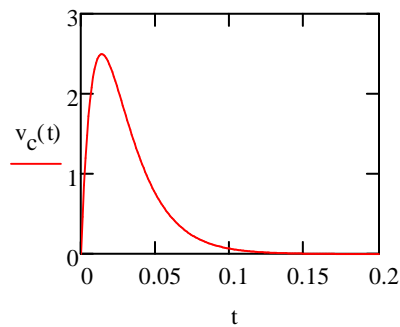

$$t := 0, 0.001 \dots 0.2$$

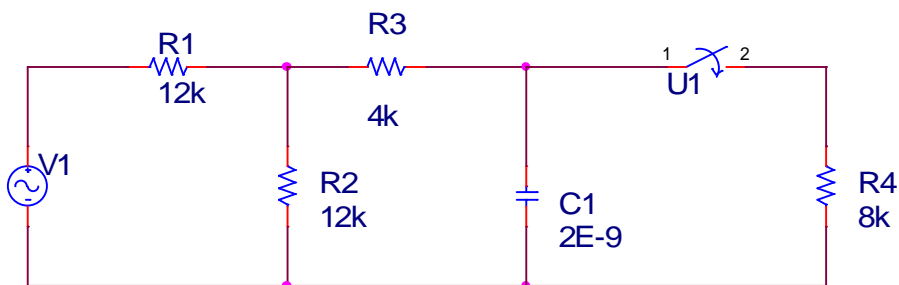3) Circuit Analysis and Thevenin/Norton Circuits



In the above circuit,

1. The voltage source turns on at $t=0$ with a voltage of 20V
2. Switch U1 closes at $15E-6s$
3. The voltage source turns off at $t = 25E-6$




a. Determine the voltage across C1 as a function of time for $t>0$.

For $0 < t < 15E-6$

Find the thevenin equivalent then solve the simple RC circuit with a step function source

$$R_{\text{Thevenin}} = \frac{12k \cdot 12k}{24k} + 4k = 10k$$
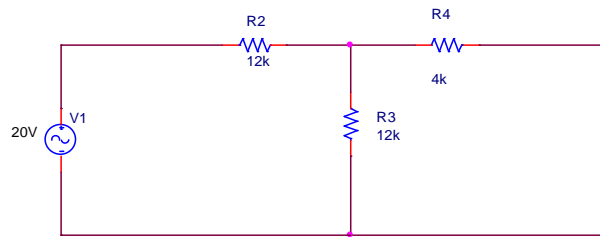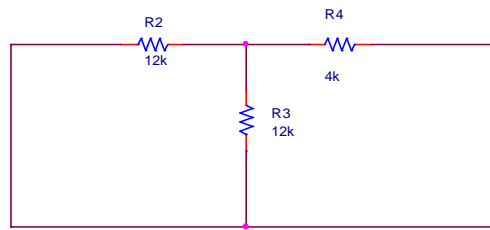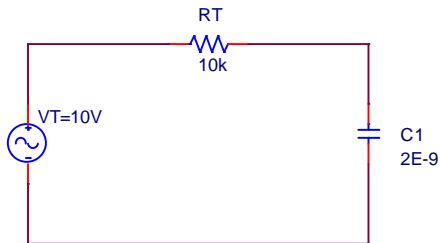
$$V_{\text{Thevenin}} = 20 \cdot \frac{12k}{24k} = 10V$$



The simple RC circuit with a step function source has a solution of the form

$$V_{C1} = A_1 \cdot e^{\frac{-t}{2 \cdot 10^{-5}}} + A_2$$

$$\tau := 10 \cdot 10^3 \cdot 2 \cdot 10^{-9}$$

$$\tau = 2 \times 10^{-5}$$

Since the source is a step function, the DC steady state as t goes to ∞ is V_{thevenin} , giving A_2

(note: what happens to the capacitor at DC steady state? open circuit)

$$A_2 = 10V$$

The initial conditions are zero giving

$$V_c(0^+) = 0 = A_1 + A_2$$

$$A_1 = -10V$$

$$V_{C1}(t) = -10 \exp\left(\frac{-t}{2 \times 10^{-5}}\right) + 10 \quad V$$

For $15E-6s < t < 25E-6$

Switch closes and now a 8k resistor is added


$$R_{\text{Thevenin}} = \frac{10k \cdot 8k}{18k} = 4.4k$$


$$V_{\text{Thevenin}} = 4.4V$$

two voltage dividers

$$20 \cdot \frac{6}{18} = 6.667$$

$$6.6 \cdot \frac{8}{12} = 4.4$$

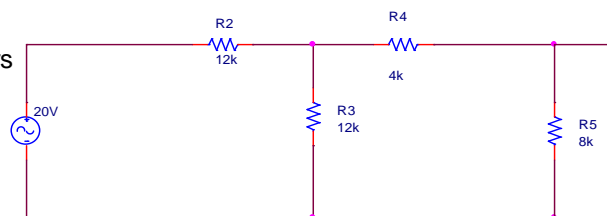

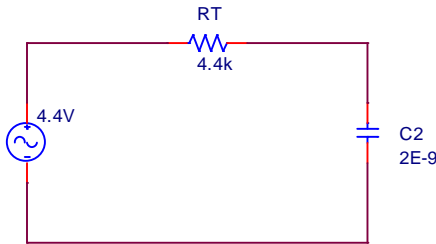

$$\tau_1 := 4.4 \cdot 10^3 \cdot 2 \cdot 10^{-9}$$

$$\tau_1 = 8.8 \times 10^{-6}$$

$$V_{c2}(t) = A_3 \cdot e^{\frac{-(t-15 \cdot 10^{-6})}{8.88 \cdot 10^{-6}}} + A_4$$

Since the source is a step function source, the DC steady state as t approaches ∞ is $V_{Thevenin}$ giving

$$A_4 = 4.4v$$

Enforcing continuity conditions, $V_{c1}(15E-6)=V_{c2}(15E6+)=5.28$

$$\frac{-15 \cdot 10^{-6}}{-10 \cdot e^{2 \cdot 10^{-5}}} + 10 = 5.276$$

$$5.28 = A_3 \cdot e^0 + A_4$$

$$5.28 = A_3 + 4.4$$

$$V_{c2}(t) = 0.84e^{-\left(\frac{t-15 \cdot 10^{-6}}{8.88 \cdot 10^{-6}}\right)} + 4.44$$

For $t > 25E-6$ switch is still down so R_{th} is the same

$$R_{Thevenin} = 4.4k$$

$$V_{Thevenin} = 0 \quad \text{the source is off}$$

$$\tau_1 := 4.4 \cdot 10^3 \cdot 2 \cdot 10^{-9}$$

$$\tau_1 = 8.8 \times 10^{-6}$$

$$V_{c3}(t) = A_5 \cdot e^{\frac{-(t-25 \cdot 10^{-6})}{8.88 \cdot 10^{-6}}} + A_6$$

$$A_6 = V_{thevenin} = 0$$

Enforcing the continuity conditions $V_{c2}(25 \cdot 10^{-6}) = V_{c3}(25 \cdot 10^{-6})$

$$0.84e^{-\left(\frac{25 \cdot 10^{-6} - 15 \cdot 10^{-6}}{8.88 \cdot 10^{-6}}\right)} + 4.44 = 4.712$$

$$V_{c3} = 4.71 \cdot e^{\frac{-(t-25 \cdot 10^{-6})}{8.88 \cdot 10^{-6}}}$$

$$V_c(t) = \begin{cases} -10 \exp\left(\frac{-t}{2E-5}\right) + 10 & 0 < t < 15E-6 \\ 5.28 \exp\left(\frac{-(t-15 \times 10^{-6})}{8.888E-6}\right) & 15E-6 < t < 25E-7 \\ 4.71 \exp\left(\frac{-(t-25 \times 10^{-6})}{8.888E-6}\right) & 25E-7 < t \end{cases}$$