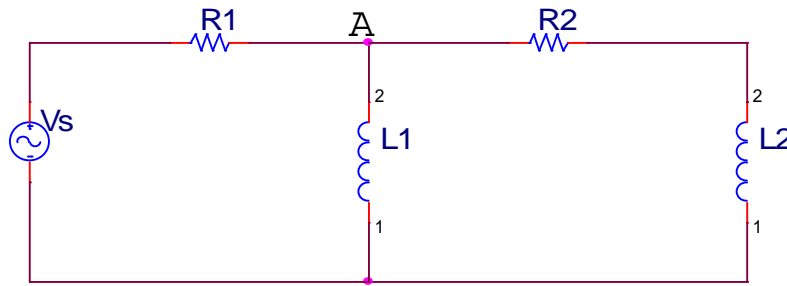


1)



a). In the above circuit, find a differential equation for the current through L2, $I_{L2}(t)$. The source is an arbitrary source. (Hint: Consider applying KCL at A and determine an expression for V_A in terms of I_{L2} .)

$$\text{KCL at A: } \frac{V_A - V_s}{R_1} + I_{L1} + I_{L2} = 0$$

Using the differential relationship between current and voltage in a capacitor

$$I_{L1} = \frac{1}{L_1} \cdot \int V_{L1} dt$$

Recognizing that $V_{L1} = V_A$

$$I_{L1} = \frac{1}{L_1} \cdot \int V_A dt$$

Substituting and rearranging

$$\frac{V_A}{R_1} + \frac{1}{L_1} \cdot \int V_A dt + I_{L2} = \frac{V_s}{R_1}$$

Recognizing that $V_A = V_{R2} + V_{L2}$. Applying ohm's law and the differential relationship between current and the voltage in an inductor.

$$V_A = I_{L2} \cdot R_2 + L_2 \cdot \frac{dI_{L2}}{dt}$$

substituting

$$\frac{1}{R_1} \cdot \left(I_{L2} \cdot R_2 + L_2 \cdot \frac{dI_{L2}}{dt} \right) + \frac{1}{L_1} \cdot \int \left(I_{L2} \cdot R_2 + L_2 \cdot \frac{dI_{L2}}{dt} \right) dt + I_{L2} = \frac{V_s}{R_1}$$

Differentiating to get rid of the integral term

$$\frac{1}{R_1} \cdot \left(R_2 \cdot \frac{dI_{L2}}{dt} + L_2 \cdot \frac{d^2 I_{L2}}{dt^2} \right) + \frac{1}{L_1} \cdot \left(I_{L2} \cdot R_2 + L_2 \cdot \frac{dI_{L2}}{dt} \right) + \frac{dI_{L2}}{dt} = \frac{1}{R_1} \cdot \frac{dV_s}{dt}$$

Rearranging


$$\frac{L_2}{R_1} \cdot \frac{d^2 I_{L2}}{dt^2} + \left(\frac{R_2}{R_1} + \frac{L_2}{L_1} + 1 \right) \frac{dI_{L2}}{dt} + \frac{R_1 \cdot R_2}{L_1 \cdot L_2} \cdot I_{L2} = \frac{1}{R_1} \frac{dV_s}{dt}$$

For the differential equation, determine symbolic expressions for the attenuation constant, α , and the resonant frequency, ω_0 , in terms of R_1 , R_2 , L_1 and L_2 .

$$2\alpha = \frac{R_2}{L_2} + \frac{R_1}{L_1} + \frac{R_1}{L_2} \quad \text{so} \quad \alpha = \frac{1}{2} \cdot \left(\frac{R_2}{L_2} + \frac{R_1}{L_1} + \frac{R_1}{L_2} \right)$$

$$\omega_0^2 = \frac{R_1 \cdot R_2}{L_1 \cdot L_2} \quad \text{so} \quad \omega_0 = \sqrt{\frac{R_1 \cdot R_2}{L_1 \cdot L_2}}$$

2) RLC series circuits

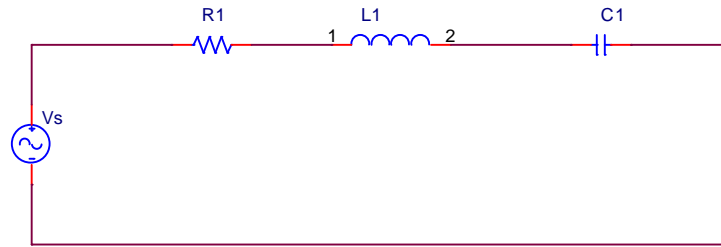

In the above circuit, V_s is a step function source and that turns on at $t = 0$. Determine the form of the solution for the following conditions (you do not need to solve for the coefficients A_1 , A_2 , and A_3). Indicate the damping for each case and include calculations of the attenuation constant and resonant frequency in your solution.

a). $R_1 := 10\Omega$ $L_1 := 1 \cdot 10^{-2}\text{H}$ $C_1 := 1 \cdot 10^{-6}\text{F}$

$$\alpha := \frac{R_1}{2 \cdot L_1}$$

$$\alpha = 500 \frac{1}{\text{s}} \quad \text{don't use units}$$

$$\omega_0 := \sqrt{\frac{1}{L_1 \cdot C_1}}$$

$$\omega_0 = 1 \times 10^4 \frac{1}{\text{s}}$$

$\alpha < \omega_0$ therefor the circuit is (strongly) underdamped and the solution takes the form

$$\beta := \sqrt{\omega_0^2 - \alpha^2} = 9.987 \times 10^3 \frac{1}{\text{s}}$$

$$f(t) = e^{-500t} \cdot (A_1 \cdot \cos(9987t) + A_2 \cdot \sin(9987t)) + A_3$$

A_3 is because V_s is a step function!

$$\text{b).} \quad R_{1b} := 200\Omega \quad L_{1b} := 1 \cdot 10^{-2}\text{H} \quad C_{1b} := 1 \cdot 10^{-6}\text{F}$$

$$\alpha_b := \frac{R_{1b}}{2L_{1b}}$$

$$\alpha_b = 1 \times 10^4 \frac{1}{\text{s}}$$

$$\omega_{0b} := \sqrt{\frac{1}{L_{1b} \cdot C_{1b}}}$$

$$\omega_{0b} = 1 \times 10^4 \frac{1}{\text{s}}$$

$\alpha = \omega_0$ therefore the circuit is critically damped

$$f(t) = A_1 \cdot \exp(-10^4 t) + A_1 \cdot t \cdot \exp(-10^4 t) + A_3$$

$$\text{c).} \quad R_{1c} := 1000\Omega \quad L_{1c} := 1 \cdot 10^{-2}\text{H} \quad C_{1c} := 1 \cdot 10^{-6}\text{F}$$

$$\alpha_c := \frac{R_{1c}}{2L_{1c}} = 5 \times 10^4 \frac{1}{\text{s}}$$

$$\omega_{0c} := \sqrt{\frac{1}{L_{1c} \cdot C_{1c}}}$$

$$\omega_{0c} = 1 \times 10^4 \frac{1}{\text{s}}$$

$\alpha > \omega_0$ therefore the circuit is overdamped

$$s_1 := -\alpha_c + \sqrt{\alpha_c^2 - \omega_{0c}^2} = -1.01 \times 10^3 \frac{1}{s}$$

$$s_2 := -\alpha_c - \sqrt{\alpha_c^2 - \omega_{0c}^2} = -9.899 \times 10^4 \frac{1}{s}$$

$$f(t) = A_1 \cdot \exp(-9.899 \times 10^4 t) + A_2 \cdot \exp(-1.01 \times 10^3 t) + A_3$$

