

Questions:

What are some important Laplace transforms?

What is a transfer function?


What are poles?

What are zeros?

Why is the left half plane significant?

Review RLC series circuit: 2nd order differential equations

1)
RLC series circuits

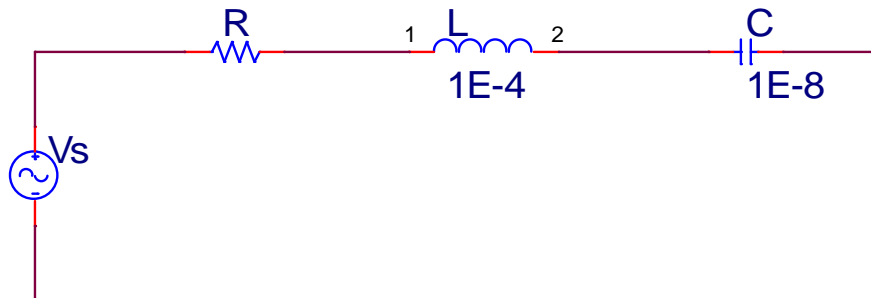

In the above circuit, the voltage source is $V_s = \begin{cases} 5V & t < 0 \\ 10V & 0 < t \end{cases}$

$$L_1 := 1 \cdot 10^{-4} \text{H} \quad C_1 := 1 \cdot 10^{-8} \text{F}$$

a. For what range of resistor values is the circuit overdamped?

The circuit is overdamped when $\alpha > \omega_0$, giving

$$\alpha = \frac{R}{2L} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\frac{R}{2L} > \frac{1}{\sqrt{LC}}$$

$$R > \frac{2L}{\sqrt{LC}} \quad \frac{2 \cdot 1 \cdot 10^{-4}}{\sqrt{1 \cdot 10^{-4} \cdot 1 \cdot 10^{-8}}} = 200$$

$$R > 200$$

b. For what resistor value is the circuit critically damped?

The circuit is critically damped when $\alpha = \omega_0$

$$R = \frac{2L}{\sqrt{LC}} \quad R = 200\Omega$$

c. For what range of resistor values is the circuit underdamped?

The circuit is underdamped when $\alpha < \omega_0$

$$R < 200\Omega$$

Determine the voltage across the capacitor as a function of time, $V_C(t)$, when

d. $R=2000\Omega$

$$R_d := 2000\Omega \quad (\text{circuit will be overdamped})$$

$$\alpha := \frac{R_d}{2L_1}$$

$$\alpha = 1 \times 10^7 \frac{1}{s}$$

$$\omega_0 := \frac{1}{\sqrt{L_1 \cdot C_1}}$$

$$\omega_0 = 1 \times 10^6 \frac{1}{s}$$

$$s_{1d} := -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_{1d} = -5.013 \times 10^4 \frac{1}{s}$$

$$s_{2d} := -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$s_{2d} = -1.995 \times 10^7 \frac{1}{s}$$

Overdamped takes the form of two decaying exponentials

$$V_C(t) = A_1 \cdot \exp(-5.013 \cdot 10^4 t) + A_2 \cdot \exp(-1.99 \cdot 10^7 t) + A_3$$

The t goes to ∞ DC steady state solution give the A_3 term $A_3=10$

The initial conditions give

$$V_C(0^+) = A_1 \cdot e^0 + A_2 \cdot e^0 + 10 = 5$$

$$dV_C(0^+) = \frac{I_C(0^+)}{C} = \frac{I_L(0^+)}{C} = 0 = -5.01 \cdot 10^4 \cdot A_1 - 1.99 \cdot 10^7 \cdot A_2$$

this equation is the derivative of the one above it, the left side comes from the definition of the capacitor and the series condition of the RLC

$$M_1 := \begin{pmatrix} 1 & 1 \\ -5.01 \cdot 10^4 & -1.99 \cdot 10^7 \end{pmatrix}$$

$$v_{CN} = K_1 e^{s_1 t} + K_2 e^{s_2 t}$$

$$C_d := \begin{pmatrix} -5 \\ 0 \end{pmatrix}$$

$$X_1 := M_1^{-1} \cdot C_d$$

$$X_1 = \begin{pmatrix} -5.013 \\ 0.013 \end{pmatrix}$$

$$A_{1d} := -5.013$$

$$A_{2d} := 0.013$$

$$A_3 := 10$$

$$V_C(t) = -5.013 \cdot \exp(-5.013 \cdot 10^4 t) + 0.013 \cdot \exp(1.99 \cdot 10^7 t) + 10$$

Determine the voltage across the capacitor as a function of time, $V_C(t)$, when

e. $R=200\Omega$

$R_e := 200\Omega$ we know from above that this is critically damped

$$\alpha := \frac{R_e}{2L_1}$$

$$\alpha = 1 \times 10^6 \frac{1}{s}$$

$$\omega_0 := \frac{1}{\sqrt{L_1 \cdot C_1}}$$

$$\omega_0 = 1 \times 10^6 \frac{1}{s}$$

$$V_C(t) = A_1 \cdot \exp(-1 \cdot 10^6 t) + A_2 \cdot t \cdot \exp(-1 \cdot 10^6 t) + A_3$$

The t goes to ∞ DC steady state solution give the A_3 term, $A_3 = 10$

The initial conditions give

$$V_C(0^+) = A_1 e^0 + A_2 \cdot 0 \cdot e^0 + 10 = 5$$

$$A_1 + 10 = 5$$

$$A_1 := -5$$

$$dV_C(0^+) = \frac{I_C(0^+)}{C} = \frac{I_L(0^+)}{C} = 0 = -1 \cdot 10^6 \cdot A_1 + A_2$$

$$0 = -5 \cdot (-1 \cdot 10^6) + A_2$$

$$A_2 = -5 \cdot 10^6$$

$$V_C(t) = -5 \cdot \exp(-1 \cdot 10^6 t) - 5 \cdot 10^6 \cdot \exp(-1 \cdot 10^6 t) + 10$$

Determine the voltage across the capacitor as a function of time, $V_C(t)$, when

f. $R=20\Omega$

$$R_f := 20\Omega \quad \text{we know from above that this is underdamped}$$

$$\alpha := \frac{R_f}{2L_1}$$

$$\alpha = 1 \times 10^5 \frac{1}{s}$$

$$\omega_0 := \frac{1}{\sqrt{L_1 \cdot C_1}}$$

$$\omega_0 = 1 \times 10^6 \frac{1}{s}$$

$$\beta := \sqrt{\omega_0^2 - \alpha^2}$$

$$\beta = 9.95 \times 10^5 \frac{1}{s}$$

$$V_C(t) = \exp^{-1 \cdot 10^5 t} \cdot \left(\left(A_1 \cdot \cos(9.95 \cdot 10^5 t) + A_2 \cdot \sin(9.95 \cdot 10^5 t) \right) \right) + A_3$$

The t goes to ∞ DC steady state solution give the A_3 term $A_3 = 10$

The initial conditions give

$$V_C(0^+) = A_1 + 10 = 5 \quad \begin{array}{l} \cos(0) = 1 \\ \sin(0) = 0 \end{array}$$

$$A_1 = -5$$

$$\frac{dV_C(0^+)}{dt} = \frac{I_C(0^+)}{C} = \frac{I_L(0^+)}{C} = 0 = -1 \cdot 10^5 \cdot A_1 + 9.95 \cdot 10^5 A_2$$

$$-5 \cdot (-1 \cdot 10^5) \cdot A_1 + 9.95 \cdot 10^5 A_2 = 0$$

$$A_2 = 0.503$$

$$V_C(t) = \exp^{-1 \cdot 10^5 t} \cdot \left(\left(-5 \cdot \cos(9.95 \cdot 10^5 t) + 0.503 \cdot \sin(9.95 \cdot 10^5 t) \right) \right) + 10$$

- 2) Find the Laplace transform of the following function

$$f(t) = (5 \cdot \exp(-5t) - 10t \cdot \exp(-5t) + 10)u(t)$$

multiply it out

$$5 \cdot \exp(-5t) \cdot u(t) - 10t \cdot \exp(-5t) \cdot u(t) + 10 \cdot u(t)$$

$$\exp(-\alpha t) u(t) \quad \text{mean } +5$$

$$\frac{5}{s+5} + \frac{-10}{(s+5)^2} + \frac{10}{s}$$

$$3). \quad F(s) = \frac{2s+1}{s^3+6s^2+8s}$$

What are the poles and zeros

$$\text{Zeros} \quad 2s+1=0 \quad s = \frac{-1}{2} \quad z = -0.5$$

$$\begin{aligned} \text{Poles} \quad & s(s^2+6s+8) & p_1 &= 0 \\ & s(s+4)(s+2) & p_2 &= -4 \\ & & p_3 &= -2 \end{aligned}$$

Write F(s) as

$$\frac{2(s+0.5)}{s \cdot (s+2) \cdot (s+4)}$$

Draw the pole zero diagram

poles are on the real axis and negative
overdamped response
No imaginary term

pole at zero implies a DC term

Using partial fraction expansion find f(t) including values for all A coefficients

$$\frac{2(s+0.5)}{s \cdot (s+2) \cdot (s+4)} = \frac{A_1}{s} + \frac{A_2}{s+2} + \frac{A_3}{s+4}$$

$$\mathcal{L}^{-1}\{F(s)\} = \mathcal{L}^{-1}\left(\frac{A_1}{s} + \frac{A_2}{s+2} + \frac{A_3}{s+4}\right) \quad \text{break into parts}$$

$$\mathcal{L}^{-1}\left(\frac{A_1}{s}\right) + \mathcal{L}^{-1}\left(\frac{A_2}{s+2}\right) + \mathcal{L}^{-1}\left(\frac{A_3}{s+4}\right) = A_1 \cdot u(t) + A_2 \cdot e^{-2t} u(t) + A_3 \cdot e^{-4t} u(t)$$

$$f = (A_1 + A_2 \cdot e^{-2t} + A_3 \cdot e^{-4t}) \cdot u(t)$$

Use the cover up rule

Find A1, multiply both sides by s (denominator of A1 term), evaluate at the pole, s=0

A₁

$$\frac{2(s+0.5) \cdot s}{s \cdot (s+2) \cdot (s+4)} = A_1 + \frac{A_2 \cdot s}{s+2} + \frac{A_3 \cdot s}{s+4} \quad \text{at } s=0$$

$$\frac{1}{8} = A_1 \quad A_1 = 0.125$$

Find A2, multiply by s+2, evaluate at -2

A₂

$$\frac{2(s+0.5)(s+2)}{s \cdot (s+2) \cdot (s+4)} = A_1(s+2) + \frac{A_2 \cdot (s+2)}{s+2} + \frac{A_3 \cdot (s+2)}{s+4} \quad \text{at } s=-2$$

$$A_2 = 0.75$$

Find A3, multiply by s+4, evaluate at s=-4

$$A_3 = -0.875$$

$$F(s) = \frac{0.125}{s} + \frac{0.75}{s+2} - \frac{0.875}{s+4}$$

$$f(t) = (0.125 + 0.75e^{-2t} - 0.875e^{-4t}) \cdot u(t)$$

poles are real and negative, exponentially decaying terms

What happens with a pole at +4

$$F(s) = \frac{A_1}{s-4}$$

$$L^{-1} = A_1 \cdot e^{4t} \quad \text{not decaying!!!} \quad \text{Not stable}$$

For a stable response poles must be in the left half of the pole zero diagram

Real component of a pole must be negative

$$3) \quad F(s) = \frac{s+1}{(s+4) \cdot (s+3) \cdot (s+2)}$$

Zeros -1

Poles $-2, -3, -4$

$$\frac{s+1}{(s+4) \cdot (s+3) \cdot (s+2)} = \frac{A_1}{s+4} + \frac{A_2}{s+3} + \frac{A_3}{s+2}$$

Find A1 using the cover up rule

$$\frac{s+1}{(s+3) \cdot (s+2)} = A_1 \quad \text{at } s = -4 \quad A_1 = \frac{-4+1}{(-4+3) \cdot (-4+2)} = -1.5$$

Find A2 using the cover up rule

$$\frac{s+1}{(s+4) \cdot (s+2)} = A_2 \quad \text{at } s = -3 \quad A_2 = \frac{-3+1}{(-3+4) \cdot (-3+2)} = 2$$

Find A_3 using the cover up rule

$$\frac{s+1}{(s+4)(s+3)} = A_3 \quad \text{at } s=-2 \quad A_3 = \frac{-2+1}{(-2+4)(2+3)} = 0 \cdot -0.5$$

$$f(t) = (-1.5 \cdot \exp(-4t) + 2 \cdot \exp(-3t) - 0.5 \exp(-2t)) \cdot u(t)$$

Pole zero diagram