## Questions

What is partial fraction expansion? What is the cover-up rule? What is the impedance of a capacitor, including initial conditions? What is the impedance of an inductor, including initial conditions? How do we analyze voltage dividers in the s-domain? How do we analyze current dividers in the s-domain? How do we implement source transformations in the s-domain? How do we apply s-domain analysis to circuits?

1) 
$$F(s) = \frac{s+1}{(s+4) \cdot (s+3) \cdot (s+2)}$$

a. Find the poles and zeros b. Draw the pole zero diagram

Zeros -1

Poles -2, -3, -4

$$\frac{s+1}{(s+4)\cdot(s+3)\cdot(s+2)} = \frac{A_1}{s+4} + \frac{A_2}{s+3} + \frac{A_3}{s+2}$$

Find A1 using the cover up rule

$$\frac{s+1}{(s+3)\cdot(s+2)} = A_1 \qquad \text{at } s = -4 \qquad A_1 = \frac{-4+1}{(-4+3)\cdot(-4+2)} = -1.5$$

Find A2 using the cover up rule

$$\frac{s+1}{(s+4)\cdot(s+2)} = A_2 \quad \text{at } s = -3 \qquad A_2 = \frac{-3+1}{(-3+4)\cdot(-3+2)} = 2$$

Find A3 using the cover up rule

$$\frac{s+1}{(s+4)(s+3)} = A_3 \qquad \text{at s=-2} \qquad A_3 = \frac{-2+1}{(-2+4)(2+3)} = -0.5$$

 $f(t) = (-1.5 \cdot \exp(-4t) + 2 \cdot \exp(-3t) - 0.5 \exp(-2t)) \cdot u(t)$ 

Pole zero diagram

2) Transfer functionsFind the poles and zeros for the following functionsApply partial fraction expansion to the following functions to find f(t)

a. 
$$F(s) = \frac{2 \cdot s}{s^2 + 8s + 25}$$

See course notes

b.  $F(s) = \frac{2s}{(s+3)^2}$ 

To find 
$$L^{-1}(F(s))$$

 $p_1, p_2 = -3$ 

Expand 
$$F(s) = \frac{A_1}{s+3} + \frac{A_2}{(s+3)^2}$$

 $f(t) = A_1 \cdot e^{-3t} + A_2 \cdot t \cdot e^{-3t}$  t > 1 = 0

Need only to find A1 and A2

To find A2 use the cover up rule

$$A_2 = \left[ (s+3)^2 \cdot F(s) \right] \cdot \begin{vmatrix} \mathbf{a} & A_2 = 2 \cdot s \cdot \\ \mathbf{a} & s = -3 \end{vmatrix} = A_2 = -6$$

Cannot use cover up rule for A1

Use F(0) with A2 subsituted in

$$F(s) = \frac{A_1}{s+3} + \frac{A_2}{(s+3)^2} \qquad F(s) = \frac{2s}{(s+3)^2}$$

$$F(0) = \frac{2 \cdot 0}{(0+3)^2} = 0 = \frac{A_1}{0+3} + \frac{-6}{(0+3)^2} \qquad \frac{A_1}{3} + \frac{-2}{3} = 0 \qquad A_1 = 2$$

$$f(t) = 2 \cdot 3^{-3t} - 6 \cdot t \cdot e^{-3t}$$

can also do

F(1) 
$$\frac{2}{16} = \frac{A_1}{4} + \frac{-6}{16}$$
  $\frac{8}{16} = \frac{A_1}{4}$   $A_1 = 2$ 

c. 
$$F(s) = \frac{4s^2 + 12s + 8}{(s+8)(s+4)^2(s+1)}$$
$$\bullet = \frac{4 \cdot (s+2) \cdot (s+1)}{(s+8) \cdot (s+4)^2 \cdot (s+1)} = 4 \cdot \frac{(s+2)}{(s+8) \cdot (s+4)^2}$$

Zeros –2

Poles -8, -4double

$$F(s) = \frac{A_1}{s+8} + \frac{A_2}{s+4} + \frac{A_3}{(s+4)^2}$$

$$f(t) = A_1 \cdot e^{-8t} + A_2 \cdot e^{-4t} + A_3 \cdot t \cdot e^{-4t}$$

Find A1 using cover up rule

$$4 \cdot \frac{(s+2) \cdot (s+8)}{(s+8) \cdot (s+4)^2} = \frac{4 \cdot (s+2)}{(s+4)^2}$$
 at s=-8

$$A_{1c} := \frac{4 \cdot (-8+2)}{(-8+4)^2}$$

$$A_{1c} = -1.5$$

Find A3 using the coverup rule for s+4 at s=-4

$$4 \cdot \frac{(s+2)(s+4)^2}{(s+8) \cdot (s+4)^2} = \frac{4 \cdot (s+2)}{(s+8)}$$
 at s= -4  
A<sub>3c</sub> :=  $\frac{4 \cdot (-4+2)}{(-4+8)}$ 

$$A_{3c} = -2$$

Find A2 using F(0) or F(1)

$$4 \cdot \frac{(s+2)}{(s+8) \cdot (s+4)^2} = \frac{-1.5}{s+8} + \frac{A_2}{s+4} + \frac{-2}{(s+4)^2} \qquad F(0)$$
$$0.063 = \frac{-1.5}{8} + \frac{A_2}{4} + \frac{-2}{16}$$
$$A_2 = 1.5$$

 $f(t) = -1.5 \cdot e^{-8t} + 1.5 \cdot e^{-4t} - 2 \cdot t \cdot e^{-4t}$ 

S-domain analysis



- a. Draw the s-domain equivalent circuit. V1 is an arbitrary source.
- b. Symbolically, determine the transfer function for the voltage across the capacitor.
- c. If the initial conditions are zero and V1 is a step function 5u(t),  $R = 1k\Omega$  and C = 2E-6F, find the voltage across the capacitor.
- d. If the source voltage is 10V for t < 0 and 5V for t >0, R = 1k $\Omega$  and C = 2E-6F, find the voltage across the capacitor.



Voltage is across both components!

$$V_{C}(s) = V_{Zc} + V_{c}(0^{-})$$

What is VZc? How do you find it? Voltage divider but account for the other source

b 
$$V_{C}(s) = \frac{\frac{1}{RC}}{s + \frac{1}{RC}} \cdot \left(V_{s}(s) - \frac{V_{c}(0^{-})}{s}\right) + \frac{V_{c}(0^{-})}{s}$$

First order circuits in the s-domain for capacitors

c. If the intial conditions are zero and V1 is a step function

$$V_{1} = 5 u(t) \qquad V_{1}(s) = \frac{5}{s} \qquad V_{c}(0^{+}) = V_{c}(0^{-}) = 0$$
  

$$R_{1} := 1k\Omega \qquad R_{1}(s) = 1k\Omega$$
  

$$C_{1} := 2 \cdot 10^{-6} F \qquad C_{1}(s) = \frac{1}{2 \cdot 10^{-6} \cdot s}$$
  
Just by inser-

Just by inspection



Find poles and zeros

poles 0,-500 zeros 0

$$F(s) = \frac{2500}{s \cdot (s + 500)} = \frac{A_1}{s} + \frac{A_2}{s + 500}$$

Coverup rule for A1  

$$\frac{2500 \cdot s}{s \cdot (s + 500)} = \frac{2500}{(s + 500)} \text{ at } s=0$$

$$A_1 := \frac{2500}{500}$$

$$A_1 = 5$$

Coverup rule for A2

$$\frac{2500 \cdot (s+500)}{s \cdot (s+500)} = \frac{2500}{s} \quad \text{at s=-500} \quad A_2 := \frac{2500}{-500}$$
$$A_2 = -5$$

$$V_{c}(s) = \frac{5}{s} + \frac{-5}{s+500}$$

$$V_{c}(t) = 5 - 5e^{-500t}$$

d.

because at t<0 10V

Set up part d only!

$$V_{c}(0^{+}) = V_{c}(0^{-}) = 10V$$

$$V_{\rm s}({\rm s}) = \frac{5}{{\rm s}}$$

but because Vs goes to 5V

$$\mathbf{V}_{\mathbf{C}}(s) = \frac{\frac{1}{\mathbf{RC}}}{s + \frac{1}{\mathbf{RC}}} \cdot \left(\mathbf{V}_{\mathbf{S}}(s) - \frac{\mathbf{V}_{\mathbf{C}}(0^{-})}{s}\right) + \frac{\mathbf{V}_{\mathbf{C}}(0^{-})}{s}$$



$$V_{C}(s) = \frac{500}{s+500} \cdot \left(\frac{5}{s} - \frac{10}{s}\right) + \frac{10}{s}$$
$$\left(\frac{500}{s+500} \cdot \frac{-5}{s}\right) + \frac{10}{s}$$
$$F(s) = \frac{-2500}{s \cdot (s+500)} = \frac{A_{1}}{s} + \frac{A_{2}}{s+500}$$

10/s is easy so do it separately

Coverup rule for A1

$$\frac{-2500 \cdot (s+500)}{s \cdot (s+500)} = \frac{-2500}{s} \text{ at } s=-500 \qquad \text{Agg} := \frac{-2500}{-500}$$

 $A_2 = 5$ 

$$V_{C}(s) = \frac{-5}{s} + \frac{5}{s+500} + \frac{10}{s}$$

$$V_{C}(t) = -5 + 10 + 5 \cdot e^{-500t}$$

$$V_{C}(t) = 5 + 5 \cdot e^{-500t}$$