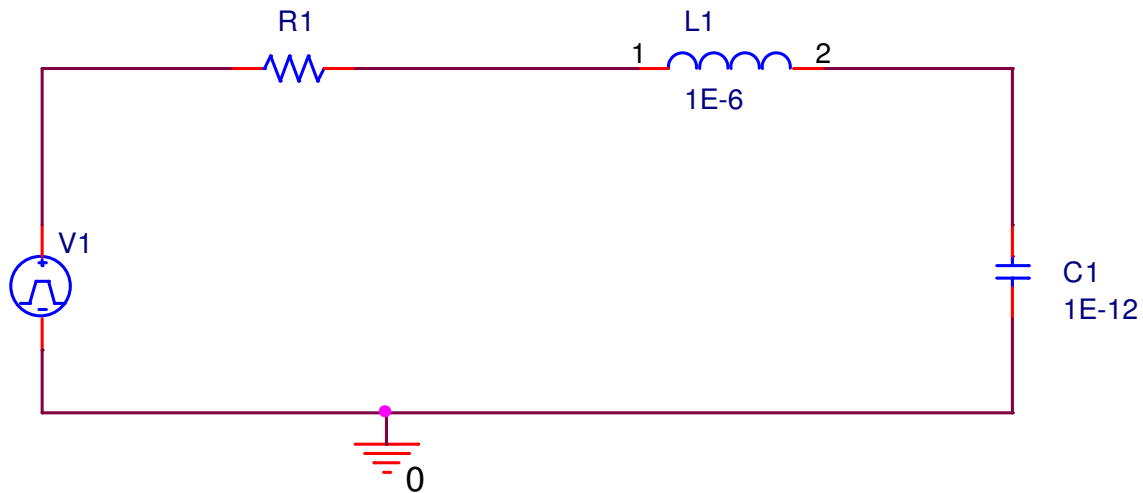


S-domain analysis with initial conditions



$$L_1 := 1 \cdot 10^{-6} \text{ H} \quad C_1 := 1 \cdot 10^{-12} \text{ F} \quad V_{1t0+} := 10\text{V} \quad V_{1t0-} := 5\text{V}$$

In the circuit above, the voltage source is 5V for  $t < 0$  and 10 V for  $t > 0$ .

a. Draw the s-domain equivalent circuit. Include the initial conditions in your s-domain circuit. Label your component values using symbolic notation (i.e. sL1).

b. Using impedances, determine the transfer function for the voltage across  $C1$ . Use symbolic numbers in your expression.

c. Using your result from part b., determine the transfer function for the current through the capacitor.

d. Using the transfer function from part c. for  $R1 = 5k\Omega$ , determine the current through the capacitor as a function of time for  $t > 0$ .