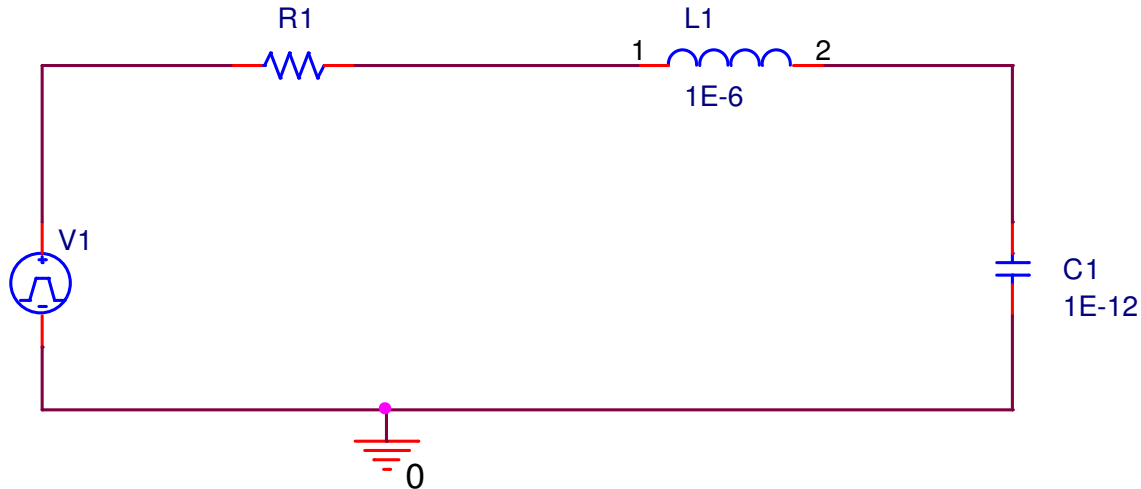


S-domain analysis with initial conditions


The method of analysis is the same as circuits with no initial conditions. At some point, you'll need to substitute in the correct s-domain values for the initial condition sources. These are DC sources that appear at the time of a switch, like a step function, so they should be N/s . Therefore, you'll need to account for another s (or more than one s) in your ratio. See example below.



$$L_1 := 1 \cdot 10^{-6} \text{ H} \quad C_1 := 1 \cdot 10^{-12} \text{ F} \quad V_{1t0+} := 10\text{V} \quad V_{1t0-} := 5\text{V}$$

In the circuit above, the voltage source is 5V for $t < 0$ and 10 V for $t > 0$.

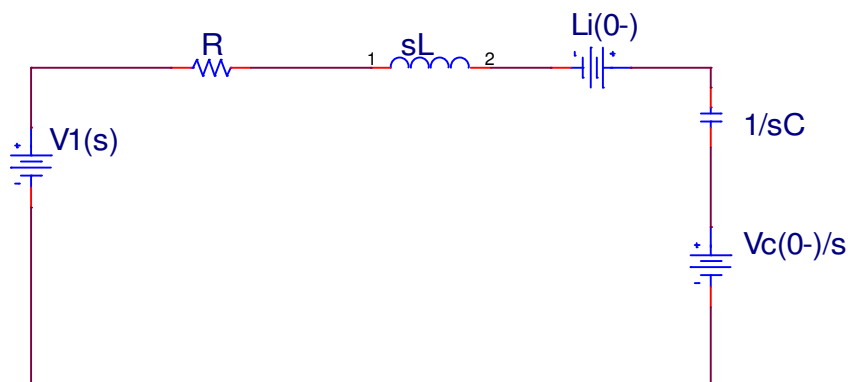
a. Draw the s-domain equivalent circuit. Include the initial conditions in your s-domain circuit. Label your component values using symbolic notation (i.e. sL_1).



$$I_L(0-) = I_L(0+) = 0 \quad \text{DC steady state for components so capacitor is open so the current in series circuit is 0.}$$

$$v_C(0^-) = v_C(0^+) = 5\text{V}$$

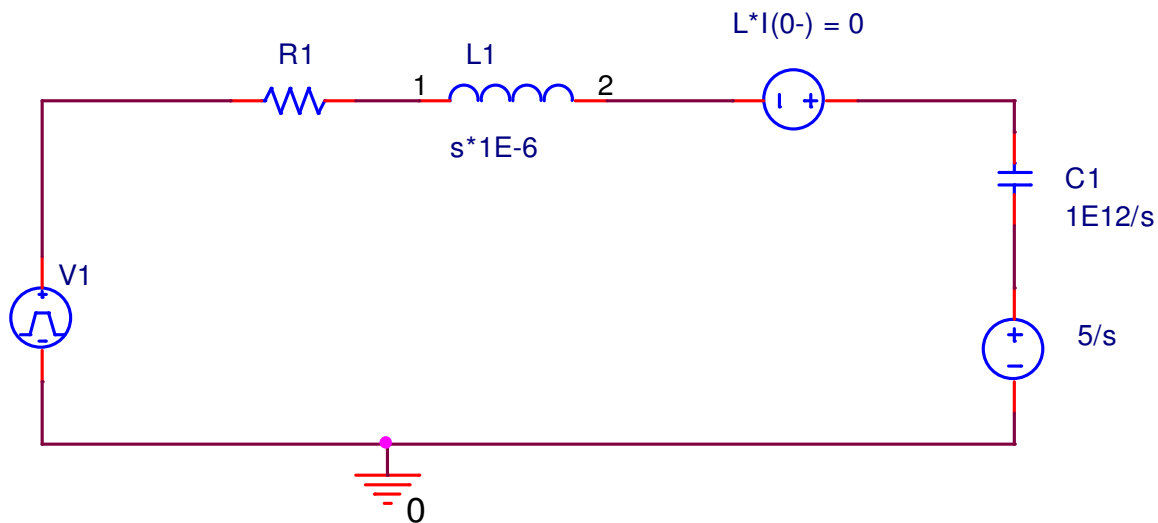The voltage across the capacitor must be 5V, the value of the source at $t < 0$.



b. Using impedances, determine the transfer function for the voltage across C1. Use symbolic numbers in your expression.

$$V_C(s) = \frac{\frac{1}{sC_1}}{R_1 + \frac{1}{sC_1} + \frac{1}{sL_1}} \cdot \left(V_1(s) + L \cdot I(0^-) - \frac{v_C(0^-)}{s} \right) + \frac{v_C(0^-)}{s}$$

*This is a voltage divider.
The voltage sources must be accounted for.*

$$V_C(s) = \frac{\frac{1}{L_1 \cdot C_1}}{s^2 + \frac{R_1}{L_1} \cdot s + \frac{1}{L_1 \cdot C_1}} \cdot \left(V_1(s) + L \cdot I(0^-) - \frac{v_C(0^-)}{s} \right) + \frac{v_C(0^-)}{s}$$

You can insert initial conditions s-domain values here. If we were looking for the $V_C(t)$, then you'd do partial fraction expansion and the inverse laplace transform after the following.

$$V_C(s) = \frac{\frac{1}{L_1 \cdot C_1}}{s^2 + \frac{R_1}{L_1} \cdot s + \frac{1}{L_1 \cdot C_1}} \cdot \left(\frac{10}{s} + 0 - \frac{5}{s} \right) + \frac{5}{s}$$

$$V_C(s) = \frac{\frac{1}{L_1 \cdot C_1}}{s^2 + \frac{R_1}{L_1} \cdot s + \frac{1}{L_1 \cdot C_1}} \cdot \left(\frac{5}{s} \right) + \frac{5}{s}$$

c. Using your result from part b., determine the transfer function for the current through the capacitor.

$$I_C(s) = \frac{V_C(s) - \frac{V_C(0-)}{s}}{\frac{1}{sC_1}}$$

Using ohm's law where current is related to capacitor impedance $Z_c = 1/sC$ by $V_c = Z_c I_c$

The voltage source is subtracted from V_c to measure current through capacitor and use ohm's law.

$$I_C(s) = \frac{\frac{s}{L_1}}{s^2 + \frac{R_1}{L_1} \cdot s + \frac{1}{L_1 \cdot C_1}} \cdot \left(V_1(s) + L_1 \cdot I(0-) - \frac{V_C(0-)}{s} \right)$$

You can insert initial condition values here.

$$I_C(s) = \frac{\frac{s}{L_1}}{s^2 + \frac{R_1}{L_1} \cdot s + \frac{1}{L_1 \cdot C_1}} \cdot \left(\frac{10}{s} + 0 - \frac{5}{s} \right)$$

$$I_C(s) = \frac{\frac{s}{L_1}}{s^2 + \frac{R_1}{L_1} \cdot s + \frac{1}{L_1 \cdot C_1}} \cdot \left(\frac{5}{s} \right)$$

$$I_C(s) = \frac{\frac{5}{L_1}}{s^2 + \frac{R_1}{L_1} \cdot s + \frac{1}{L_1 \cdot C_1}}$$

d. Using the transfer function from part c. for $R_1 = 5k\Omega$, determine the current through the capacitor as a function of time for $t > 0$.

$$I_C(s) = \frac{5 \cdot 10^6}{\left(s^2 + 5 \cdot 10^9 s + 10^{18}\right)}$$

$$R_1 := 5k\Omega$$

$$\frac{1}{L_1 \cdot C_1} = 1 \times 10^{18} \frac{1}{s^2}$$

$$s^2 + 5 \cdot 10^9 s + 10^{18} = 0$$

$$\frac{5}{L_1} = 5 \times 10^6 \frac{1}{H}$$

$$5000000000 \cdot \sqrt{21} - 25000000000 = -2.087 \times 10^8$$

$$-5000000000 \cdot \sqrt{21} - 25000000000 = -4.791 \times 10^9$$

$$\frac{R_1}{L_1} = 5 \times 10^9 \frac{1}{s}$$

Partial fraction expansion

$$\frac{5 \cdot 10^6}{(s + 2.09 \cdot 10^8) \cdot (s + 4.8 \cdot 10^9)} = \frac{A_1}{(s + 2.09 \cdot 10^8)} + \frac{A_2}{(s + 4.8 \cdot 10^9)}$$

For A1

For A2

$$\frac{5 \cdot 10^6}{(-2.09 \cdot 10^8 + 4.8 \cdot 10^9)} = 1.089 \times 10^{-3}$$

$$\frac{5 \cdot 10^6}{(-4.8 \cdot 10^9 + 2.09 \cdot 10^8)} = -1.089 \times 10^{-3}$$

$$I_C(s) = \frac{(1.1 \cdot 10^{-3})}{(s + 2.09 \cdot 10^8)} + \frac{(-1.1 \times 10^{-3})}{(s + 4.8 \cdot 10^9)}$$

$$I_C(t) = 1.1 \cdot 10^{-3} \cdot e^{-2.09 \cdot 10^8 t} - 1.1 \cdot 10^{-3} \cdot e^{-4.8 \cdot 10^9 t}$$

