

In the above circuit, a 5V DC source is shown. At t = 0, the switch in series with the capacitor is closed.

a) Draw the s-domain equivalent circuit. Include all initial condition source components.

b) Determine the transfer function for the voltage across the inductor, VL(s) = N(s)/D(s), where N(s) and D(s) are poloynomials.

- c) Apply partial fraction expansion to your above expression
- d) Based on your result in part c), determine the voltage across the inductor as a function of time.



- a) Transform the circuit into the s domain
- b) Find the zero-state and zero-input components of V(s).
- c) Find v(t) for I1 = 1mA, L = 2H, R=1.5k Ω and C = 1/6 µf With source transformation

Node Analysis in the s-domain



- a. Draw the s-domain circuit
- b. Find node equations and put in standard form
- c. Solve the node equations and find the zero-state and zero-input reponses
- d. Solve for the zero state component of the waveforms VA(t) when

 $\mathsf{R}_2\coloneqq 1 \mathsf{k} \Omega \qquad \mathsf{C}_2\coloneqq 0.2 \mu \mathsf{F} \qquad \mathsf{L}_2\coloneqq 500 \mathsf{m} \mathsf{H} \qquad \mathsf{I}_1(\mathsf{t}) = 10 \, \mathsf{u}(\mathsf{t}) \, \mathsf{m} \mathsf{A}$

Review Problems for Test



In the above circuit, the source is 8V for t<0 and 16 V for t>0. Additionally, the switch U1 closes are t = 1 s and switch U2 open at t = 1 s (They close and open at the same time).

a. At t=0+, determine the current through L1

- b. At t=0+ determine the voltage across L1
- c. For t < 1s, determine the differential equation for the current through R1 (Draw the circuit)
- d. For t<1s, is the circuit underdamped, overdamped or critically damped?
- e. Determine the voltage across L1 as a function of time for 0<t<1s
- f. Based on your above expression, dtermine the voltage across the inductor at t =1s
- g. Determine the voltage as a function of time across the inductor for t>1.



In the above circuit, the source current is 20mA for t < 0 and 0 for t > 0 (the source turns off at t = 0).

- a. What is the initial (t=0+) current through the inductor? What is the (t=0+) voltage across the inductor?
- b. What is the DC steady state current through the inductor a t goes to ∞?
- c. Symbolically, what is the differential equation defining the current through the inductor?
- d. For R1 = 100Ω , determine the current through the inductor as a function of time for t>0.
- e. For R1 = 5k Ω ?
- f. For R1 = $100k\Omega$?