

Questions:

Circuit Analysis: Phasor Math

What is admittance?

How do bridge circuits behave with complex impedances?


How does the total impedance of a series RLC circuit behave with frequency?

How does the total impedance of a parallel RLC circuit behave with frequency?

Complex Power


- What is instantaneous power?
- What is real power?
- What is reactive power?
- What is total power?
- What is rms voltage? rms current?
- How do we determine total power produced by a source?
- What is the power factor?
- What does it mean if the power factor is 'leading'? 'lagging'?

1) Bridge circuits

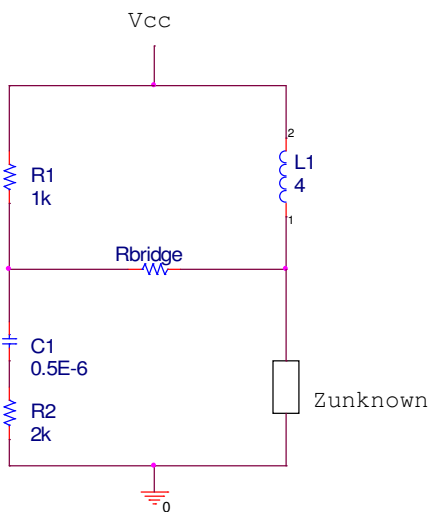

- a) What value of Zunknown balances the bridge (no current through R3) when  $\omega=1000$  rad/s?

2) Phasor KCL/KVL

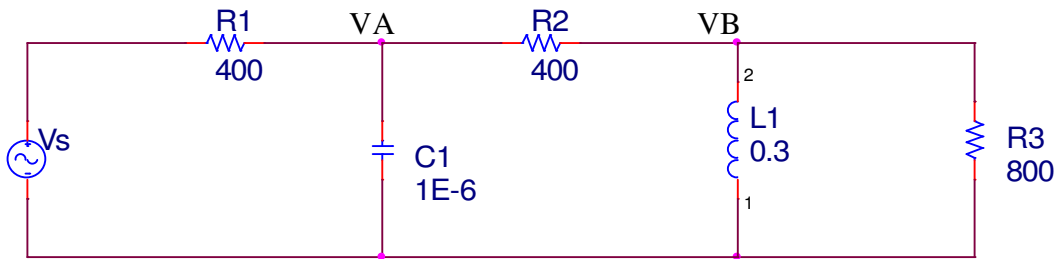

The source in the above circuit is  $20\cos(2000t)$

a. Determine the voltage across the capacitor using node analysis. TEAM ASSIGNMENT

b. Determine the voltage across the capacitor using mesh analysis.

