Lecture 22 questions

How does the orientation of the inductors affect transformer characteristics? What is mutual inductance? What is the coupling coefficient, k? What is the Tee model of mutual inductance? How do real transformers behave?

Review 2)



Determine IR4.

V.s has a 10 V amplitude, and 60 Hz frequency

$$\omega = 2\pi 60 = 377 \frac{\text{rad}}{\text{s}}$$
 N<sub>2</sub> := 5  
 $\frac{1}{377 \cdot 1.3 \cdot 10^{-4}} = 20.404$   
Z<sub>C</sub> = -j20

Refer primary to secondary



To find I2 get ZEQ for the entire circuit which is the Resistor Capacitor and Load Resistor in series

$$500 - 500j$$

$$\sqrt{500^2 + (-500)^2} = 707.107 \quad \text{also by inspection} \quad 500\sqrt{2} < -45 \text{deg}$$

$$\tan\left(\frac{-500}{500}\right) = -45 \cdot \text{deg}$$

$$Z_{\text{EQ}} = 707.1 < -45 \text{deg}$$
So I2 or IR4 is
$$\frac{50 < 0}{707.1 < -45} = 0.071 < 45 \text{deg}$$

$$\frac{50}{707.1} = 0.071 \qquad \frac{1}{10 \cdot \sqrt{2}} = 0.071$$

In the time domain:  $I_{R4} = 0$ 

 $I_{R4} = 0.071 \cdot \cos(377t + 45 \text{deg})$ 

Problem 1)



## Refer primary to secondary

Note: The middle is the secondary for the first part and the primary for the second part.

$$V_{SEQ2} := N_{3a} \cdot 15$$

$$V_{SEQ2} = 75$$

$$Z_{SR} := N_{3a}^{2} \cdot 4$$

$$Z_{SR} = 100$$

Can do Thevenin equivalent, make the load the inductor, so take it out and measure vout..



Refer to primary to secondary with thevenin equivalent attached to a step down transformer

$$V_{SEQ3} := N_{3b} \cdot 37.5$$
  
 $V_{SEQ3} = 18.75$   
 $Z_{SR2} := N_{3b}^{2} \cdot 150 = 37.5$ 

Using the voltage divider

 $\frac{18.75}{37.5 + 18.75} = 0.333$ 

$$V_{R9} \coloneqq 18.75 \cdot \frac{18.75}{37.5 + 18.75}$$

## $V_{R9} = 6.25 \quad \bullet < 0 deg$

## Problem 2) Impedance Matching



a. Determine the winding ratio and the impedance Z such that the power delivered to the load is maximized relative to the source power.

 $\omega := 2 \cdot \pi \cdot 60$  $\omega = 376.991$  $Z_{L3} = 377 \cdot 0.25 \cdot j$ 

$$Z_{I,3} = 94.25j$$

Referring the secondary to the primary, the equivalent circuit is



The power is maximized when ZS=ZL\* where Zunknow is imaginary

Considering the real parts of Zs and ZL

$$\frac{125}{N^2} = 5$$
 N = 5

Considering the imaginary parts of ZS and ZI and the winding ratio

$$\frac{-94.25j}{N^2} = Z_{unknown} \qquad \qquad Z_{unknown} = -3.77j\Omega$$

Problem 3) Tee Model



Draw the tee model equivalent for the circuit above.



 $M_1 := 0.005 M_2 := 0.01 L_3 := 0.04 L_2 := 0.01 L_4 := 0.1 L_4 L_4 := 0.1 L_4 := 0.1 L_4 := 0.1 L_4 := 0.1 L_4 L_4 L_4 := 0.1 L_4 L_$ 

$$L_3 - M_1 = 0.035$$
  
 $L_1 - M_1 = 5 \times 10^{-3}$   
 $L_2 - M_2 = 0$   
 $L_4 - M_2 = 0.09$ 

