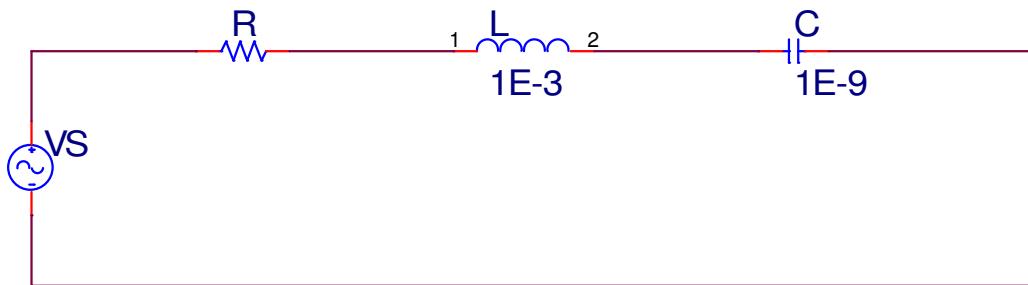


What is the damping ratio, ζ ?


How do overdamped, critically damped, and underdamped circuits behave?

Review

1) Second order circuits



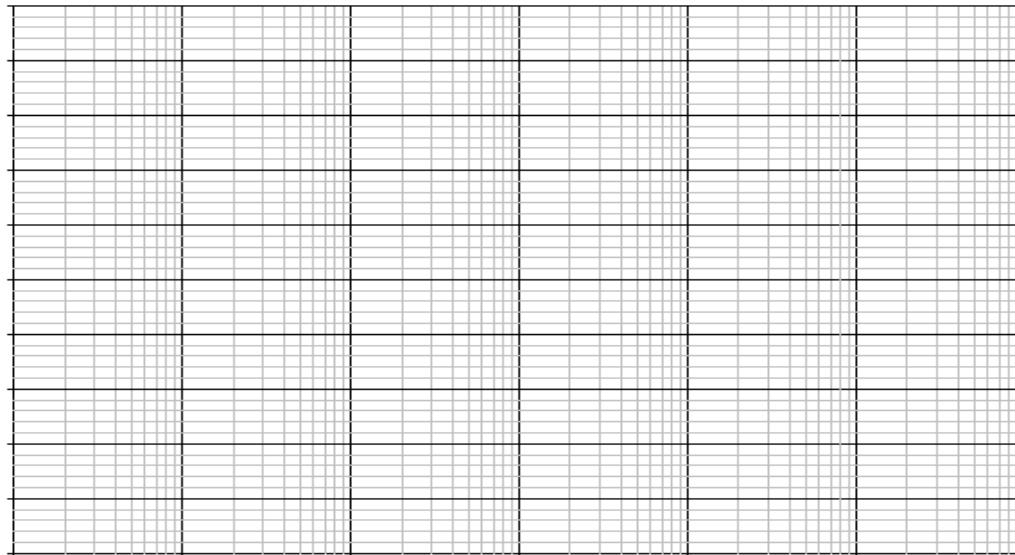a) $H(s) = V_C(s)/V(s)$ when $R=10.1\text{k}\Omega$



$$H(s) = \frac{V_C(s)}{V_T(s)} = \frac{\frac{1}{sC}}{R_T + sL + \frac{1}{sC}} = \frac{1}{sCR_T + sC \cdot sL + \frac{sC}{sC}} = \frac{1}{s^2 \cdot LC + sCR_T + 1}$$

divide top and bottom by LC

$$H(s) = \frac{1}{\frac{LC}{s^2 + \frac{R_T}{L}s + \frac{1}{LC}}}$$

Also can write (will use later)

as

$$H(s) = \frac{\omega_0^2}{s^2 + 2\zeta\omega_0 s + \omega_0^2}$$

$$2\zeta\omega_0 = \frac{R_T}{L}$$

$$\omega_0 = \sqrt{\frac{1}{LC}}$$

$$\zeta = \frac{R_T}{2} \cdot \sqrt{\frac{C}{L}}$$

damping ratio

$$\zeta = \frac{\alpha}{\omega_0}$$

$\zeta > 1$	overdamped case	real poles	two different real poles
-------------	-----------------	------------	--------------------------

$\zeta = 1$	critically damped	double pole	-6db at ω_c	attenuation of gain!
-------------	-------------------	-------------	--------------------	----------------------

$\zeta < 1$	underdamped	complex pole	can get resonance!
-------------	-------------	--------------	--------------------

$$H(s) \text{ as } s \text{ goes to } 0 \quad \frac{1}{LC} = 1 \quad H(j\omega) = \frac{1}{\frac{1}{LC}} = 1$$

$$H(s) \text{ as } s \text{ goes to } \infty \quad \frac{1}{s^2} \text{ goes to } 0 \quad H(j\omega) = \frac{1}{\frac{1}{\omega^2}} \text{ goes to } 0$$

This is a low pass filter and a rolloff of 40db
pole ω^2 or $s^2 = 2 * 20 \log()$

also known as the slope of the stopband at the

RLC series vout = Vc second order low pass filter

$$\text{If } R_1 := 10.1k\Omega \quad L_1 := 1mH \quad C_1 := 1nF \quad \frac{1}{L_1 \cdot C_1} = 1 \times 10^{12} \frac{1}{s^2}$$

$$H(s) = \frac{10^{12}}{s^2 + 1.01 \cdot 10^7 s + 10^{12}}$$

$$\alpha := \frac{1.01 \cdot 10^7}{2} = 5.05 \times 10^6$$

$$\omega_0 := \sqrt{\frac{1}{L_1 \cdot C_1}} = 1 \times 10^6 \frac{1}{s}$$

$$\zeta := \frac{\alpha}{\omega_0} = 5.05 \text{ s} \quad \text{This is } > 1 \text{ so OVERDAMPED}$$

$$H(s) = \frac{10^{12}}{(s + 10^5)(s + 10^7)}$$

zero: none
pole $10^5, 10^7$

$$H(j\omega) = \frac{10^{12}}{10^5 \cdot 10^7} \cdot \frac{1}{\left(1 + \frac{j\omega}{10^5}\right) \cdot \left(1 + \frac{j\omega}{10^7}\right)}$$


$$s < 10^5 \quad \frac{10^{12}}{(10^5)(10^7)} = 1 \quad \omega < 10^5 \quad 1 \quad 20 \cdot \log(1) = 0$$

$$10^5 < s < 10^7 \quad \frac{10^{12}}{(s)(10^7)} \quad \frac{10^5}{s} \quad 10^5 < \omega < 10^7 \quad \frac{1}{\frac{\omega}{10^5}} \quad -20 \frac{\text{db}}{\text{dec}}$$


$$s > 10^7 \quad \frac{10^{12}}{(s) \cdot (s)} \quad \frac{10^{12}}{s^2} \quad \omega > 10^7 \quad \frac{1}{\frac{\omega^2}{10^5 \cdot 10^7}} \quad -40 \frac{\text{db}}{\text{dec}}$$

Overdamped case: two different real poles

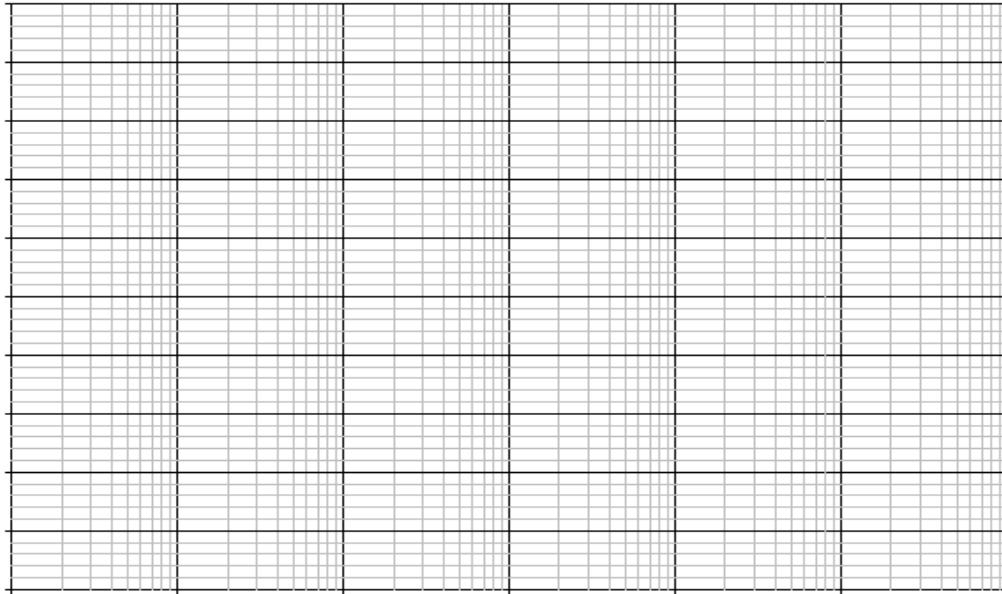
b) $H(s) = VL(s)/V(s)$ when
 $R=10.1k\Omega$



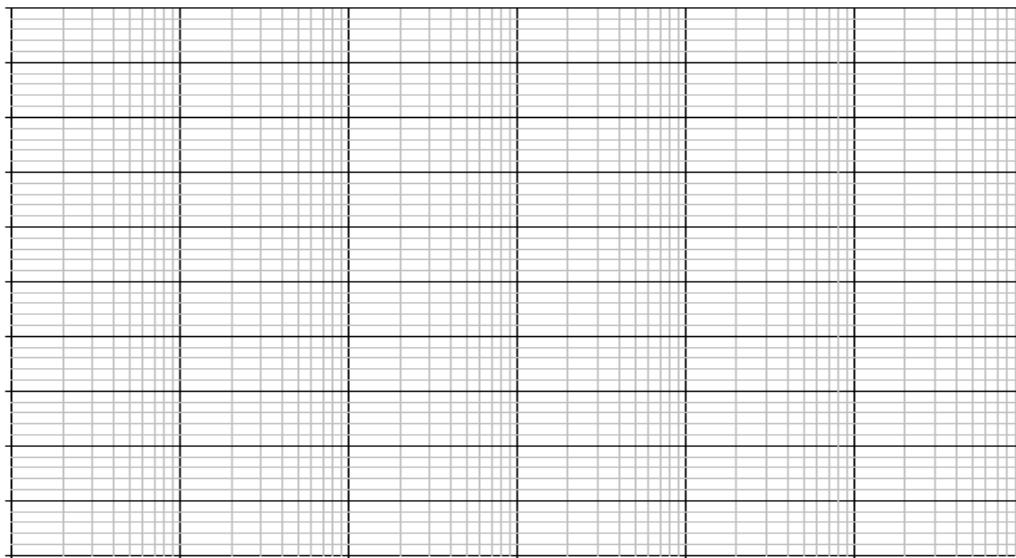
c) $H(s) = VR(s)/V(s)$ when $R = 10.1k\Omega$




2) Second order circuits TEAM ASSIGNMENT

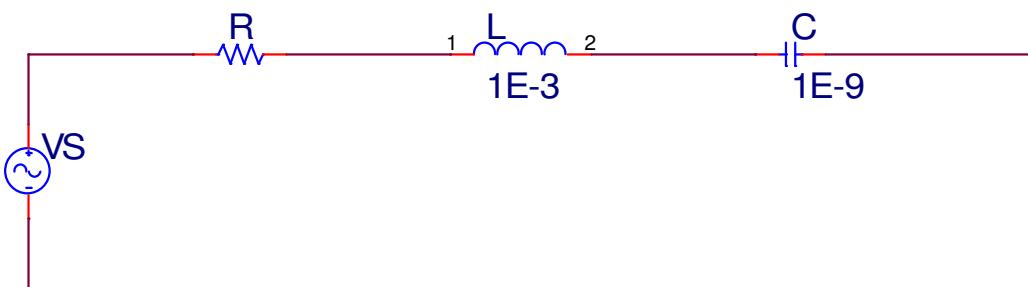

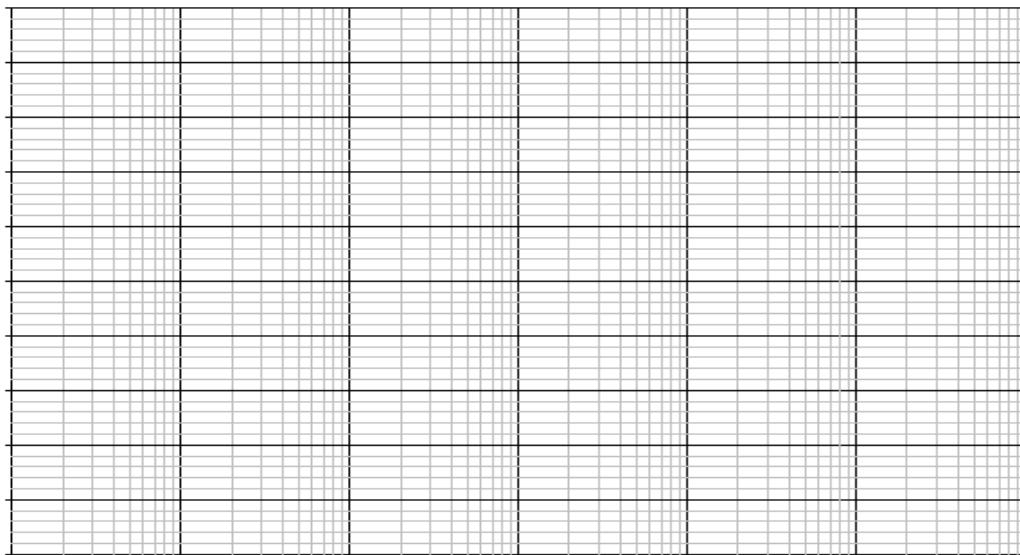
a. $H(s) = VC(s)/V(s)$ **when $R=2k\Omega$**



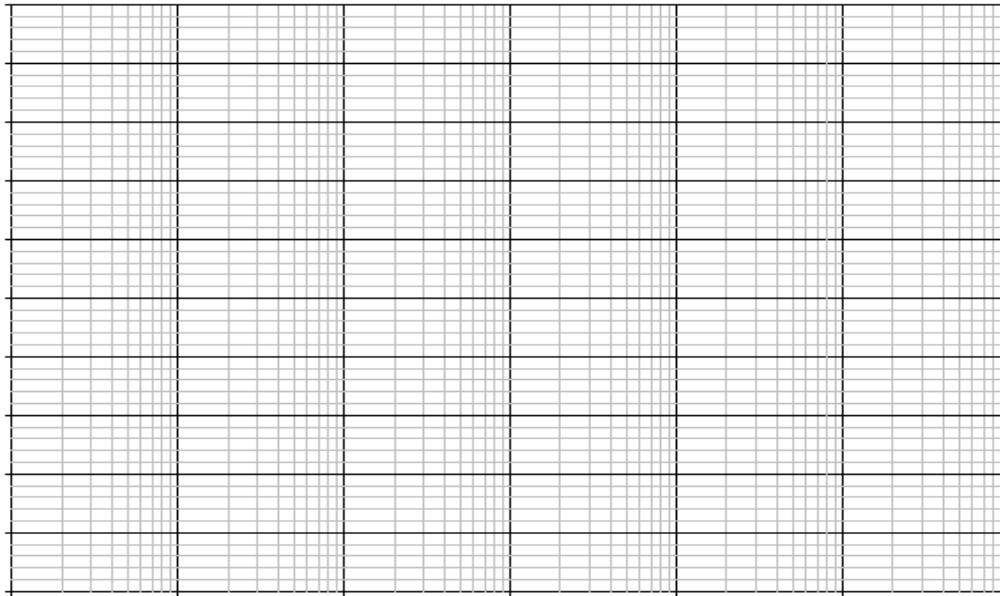
b. $H(s) = VL(s)/V(s)$ when $R = 2k\Omega$



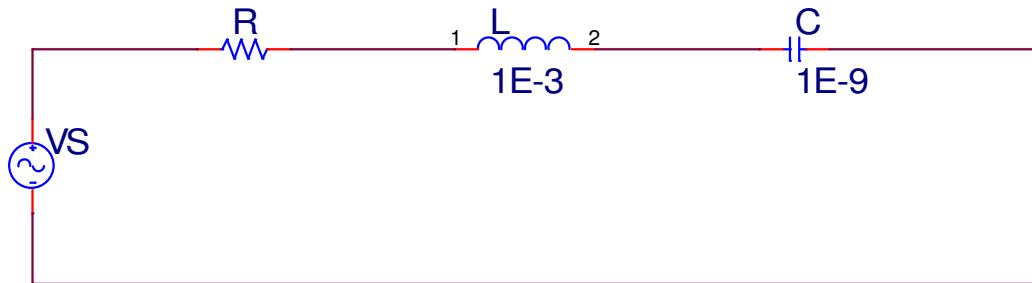
3) Underdamped cases of the RLC series circuit



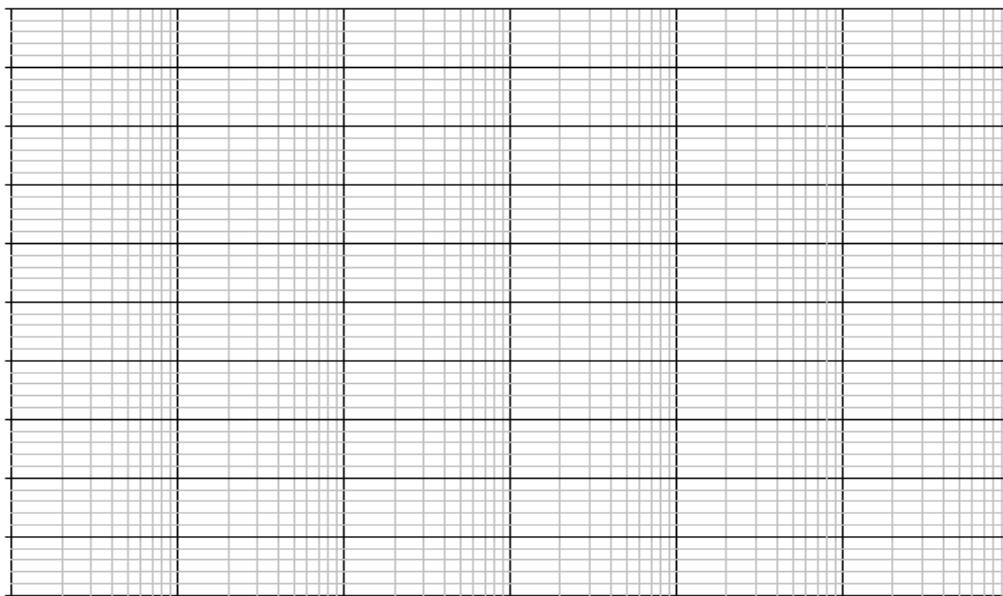a.) $H(s) = VC(s)/V(s)$ when $R = 1\text{k}\Omega$



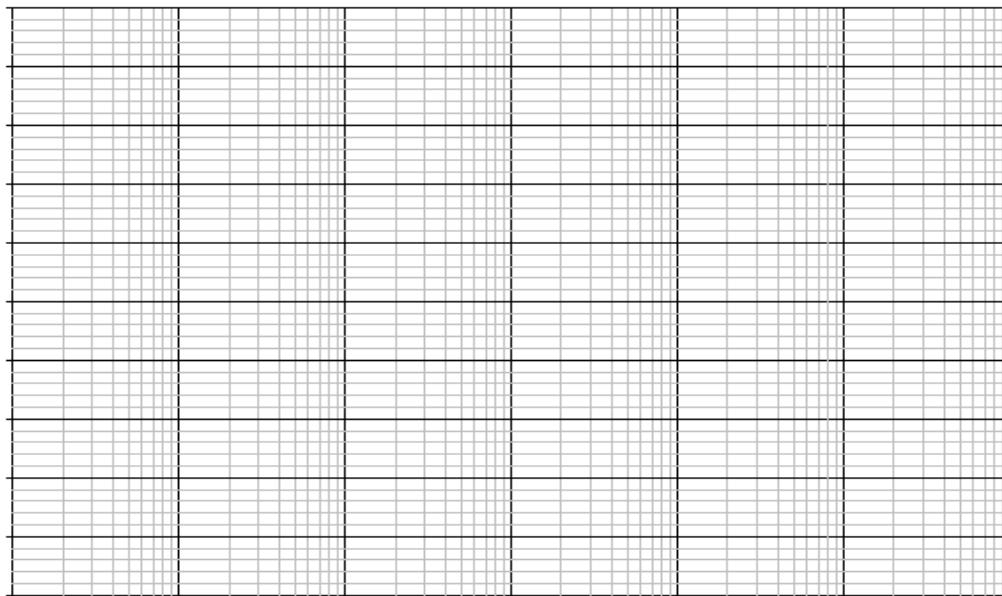b.) $H(s) = VC(s)/V(s)$ when $R = 1.41k\Omega$



c.) $H(s) = VC(s)/V(s)$ when $R = 100\Omega$

