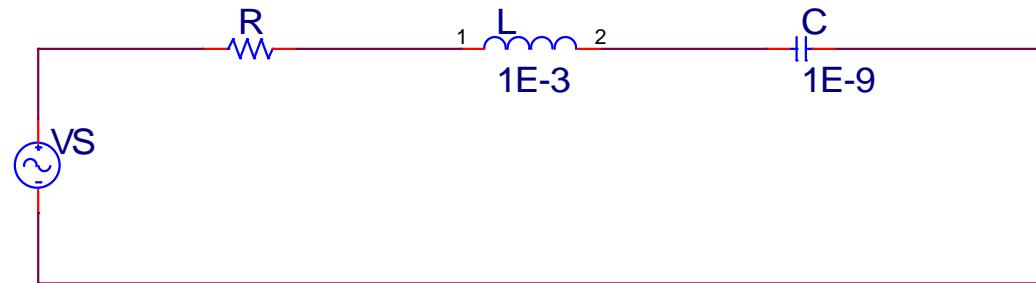


What is the damping ratio,  $\zeta$ ?


How do overdamped, critically damped, and underdamped circuits behave?

Review 1)

1) Second order circuits



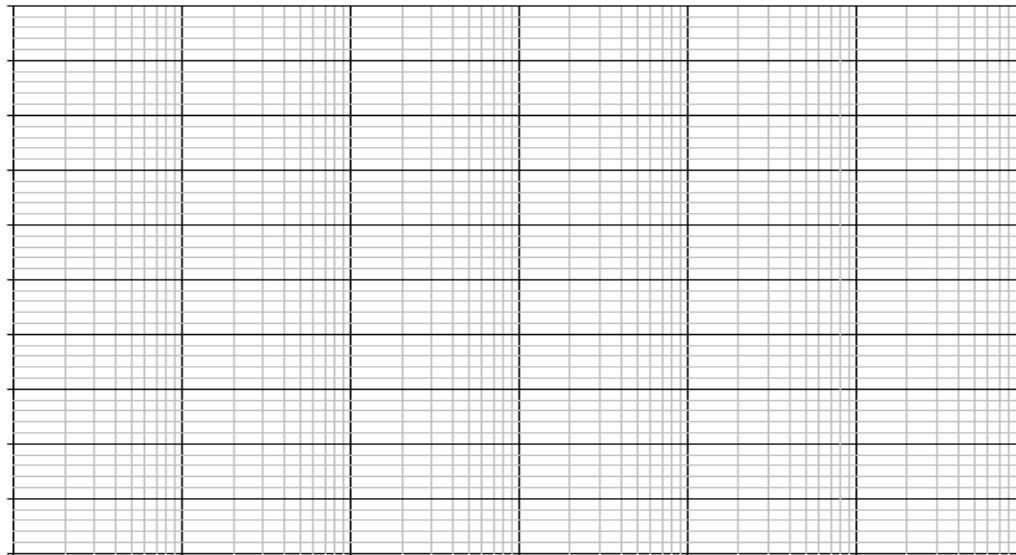a)  $H(s) = V_C(s)/V(s)$  when  $R=10.1\text{k}\Omega$



$$H(s) = \frac{V_C(s)}{V_T(s)} = \frac{\frac{1}{sC}}{R_T + sL + \frac{1}{sC}} = \frac{1}{sCR_T + sC \cdot sL + \frac{1}{sC}} = \frac{1}{s^2 \cdot LC + sCR_T + 1}$$

divide top and bottom by LC

$$H(s) = \frac{1}{\frac{s^2 + \frac{R_T}{L}s + \frac{1}{LC}}{LC}}$$

Also can write as (will use later)

$$H(s) = \frac{\omega_0^2}{s^2 + 2\zeta\omega_0 s + \omega_0^2} \quad 2\zeta\omega_0 = \frac{R_T}{L} \quad \omega_0 = \sqrt{\frac{1}{LC}}$$

$$\zeta = \frac{R_T}{2} \cdot \sqrt{\frac{C}{L}} \quad \text{damping ratio} \quad \zeta = \frac{\alpha}{\omega_0}$$

$\zeta > 1$  overdamped case real poles two different real poles

$\zeta = 1$  critically damped double pole -6db at  $\omega_c$  attenuation of gain!

$\zeta < 1$  underdamped complex pole can get resonance!

$$H(s) \text{ as } s \text{ goes to } 0 \quad \frac{1}{\frac{1}{LC}} = 1 \quad H(j\omega) = \frac{1}{\frac{1}{LC}} = 1$$

$$H(s) \text{ as } s \text{ goes to } \infty \quad \frac{\frac{1}{LC}}{s^2} \text{ goes to } 0 \quad H(j\omega) = \frac{1}{\frac{1}{LC}} \text{ goes to } 0$$

**This is a low pass filter** and a rolloff of 40db also known as the slope of the stopband at the pole  $\omega^2$  or  $s^2 = 2 * 20 \log()$

RLC series  $v_{out} = V_C$  second order low pass filter

$$\text{If } R_1 := 10.1k\Omega \quad L_1 := 1mH \quad C_1 := 1nF \quad \frac{1}{L_1 \cdot C_1} = 1 \times 10^{12} \frac{1}{s^2}$$

$$H(s) = \frac{10^{12}}{s^2 + 1.01 \cdot 10^7 s + 10^{12}} \quad \alpha := \frac{1.01 \cdot 10^7}{2} = 5.05 \times 10^6$$

$$\omega_0 := \sqrt{\frac{1}{L_1 \cdot C_1}} = 1 \times 10^6 \frac{1}{s}$$

$$\zeta := \frac{\alpha}{\omega_0} = 5.05 \text{ s} \quad \text{This is } > 1 \text{ so OVERDAMPED}$$

$$H(s) = \frac{10^{12}}{(s + 10^5) \cdot (s + 10^7)}$$

zero: none  
pole  $10^5, 10^7$

$$H(j\omega) = \frac{10^{12}}{10^5 \cdot 10^7} \cdot \frac{1}{\left(1 + \frac{j\omega}{10^5}\right) \cdot \left(1 + \frac{j\omega}{10^7}\right)}$$


$$s < 10^5 \quad \frac{10^{12}}{(10^5) \cdot (10^7)} = 1 \quad \omega < 10^5 \quad 1 \quad 20 \cdot \log(1) = 0$$

$$10^5 < s < 10^7 \quad \frac{10^{12}}{(s) \cdot (10^7)} \quad \frac{10^5}{s} \quad 10^5 < \omega < 10^7 \quad \frac{1}{\frac{\omega}{10^5}} \quad -20 \frac{\text{db}}{\text{dec}}$$

$$s > 10^7 \quad \frac{10^{12}}{(s) \cdot (s)} \quad \frac{10^{12}}{s^2} \quad \omega > 10^7 \quad \frac{1}{\frac{\omega^2}{10^5 \cdot 10^7}} \quad -40 \frac{\text{db}}{\text{dec}}$$

**Overdamped case: two different real poles**

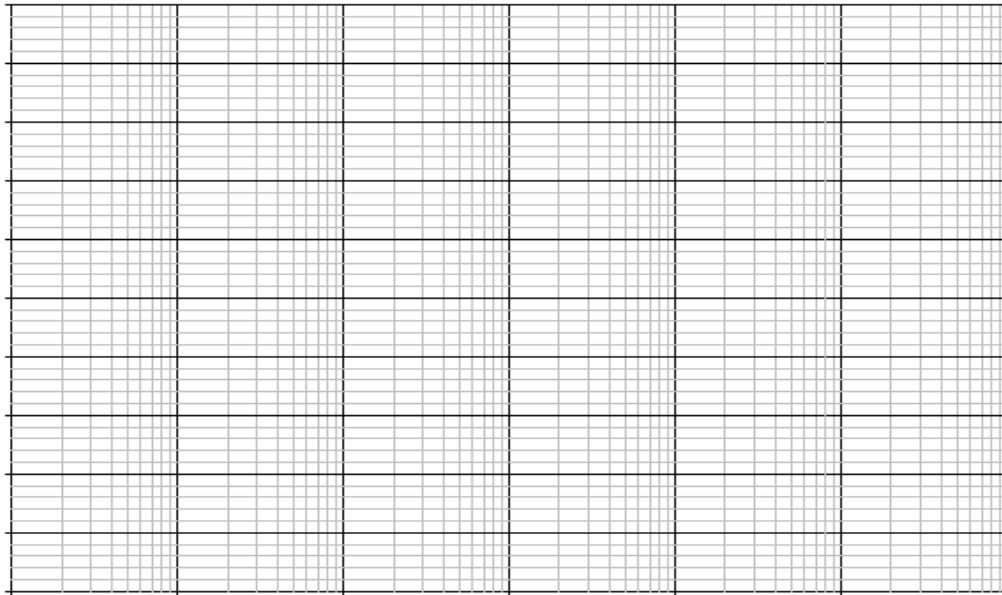b)  $H(s) = VL(s)/V(s)$  when  $R=10.1\text{k}\Omega$



$$H(s) = \frac{s^2}{s^2 + \frac{R}{L} \cdot s + \frac{1}{LC}}$$

$$H(j\omega) = \frac{(j\omega)^2}{\left(1 + \frac{j\omega}{10^5}\right) \cdot \left(1 + \frac{j\omega}{10^7}\right)}$$

$$\begin{aligned} H(s) \text{ when } s \text{ goes to } 0 \\ \frac{s^2}{\frac{1}{LC}} = 0 \end{aligned}$$

$$\begin{aligned} H(s) \text{ when } s \text{ goes to } \infty \\ \frac{\frac{s^2}{2}}{s^2} = 1 \end{aligned}$$

***This is an overdamped, second order high pass filter***

$$\text{If } R_1 := 10.1\text{k}\Omega \quad L_1 := 1\text{mH} \quad C_1 := 1\text{nF} \quad \frac{1}{L_1 \cdot C_1} = 1 \times 10^{12} \frac{1}{\text{s}^2}$$

$$H(s) = \frac{s^2}{s^2 + 1.01 \cdot 10^7 s + 10^{12}}$$

$$H(s) = \frac{s^2}{(s + 10^5) \cdot (s + 10^7)}$$

zero: double 0  
pole  $10^5, 10^7$

$$H(j\omega) = \frac{1}{10^5 \cdot 10^7} \cdot \frac{(j\omega)^2}{\left(1 + \frac{j\omega}{10^5}\right) \cdot \left(1 + \frac{j\omega}{10^7}\right)}$$

$$\frac{(10^5)^2}{10^5 \cdot 10^7} = 0.01$$

$$s < 10^5 \quad \frac{s^2}{(10^5) \cdot (10^7)} \quad \omega < 10^5 \quad \frac{\omega^2}{10^5 \cdot 10^7} \quad 40 \frac{\text{db}}{\text{dec}} \quad 20 \log(0.01) = -40$$


$$10^5 < s < 10^7 \quad \frac{s^2}{(s) \cdot (10^7)} \quad \frac{s}{10^7} \quad 10^5 < \omega < 10^7 \quad \frac{1}{10^5 \cdot 10^7} \cdot \frac{\omega^2}{\frac{\omega}{10^5}} = \frac{\omega}{10^7} \quad 20 \frac{\text{db}}{\text{dec}}$$

$$\frac{10^5}{10^7} = 0.01 \quad 20 \log(0.01) = -40$$

$$s > 10^7 \quad \frac{s^2}{(s) \cdot (s)} = 1 \quad \omega > 10^7 \quad \frac{1}{10^5 \cdot 10^7} \cdot \frac{\omega^2}{\frac{\omega^2}{10^5 \cdot 10^7}} \quad 0 \text{ db}$$

Overdamped high pass filter, two different real poles

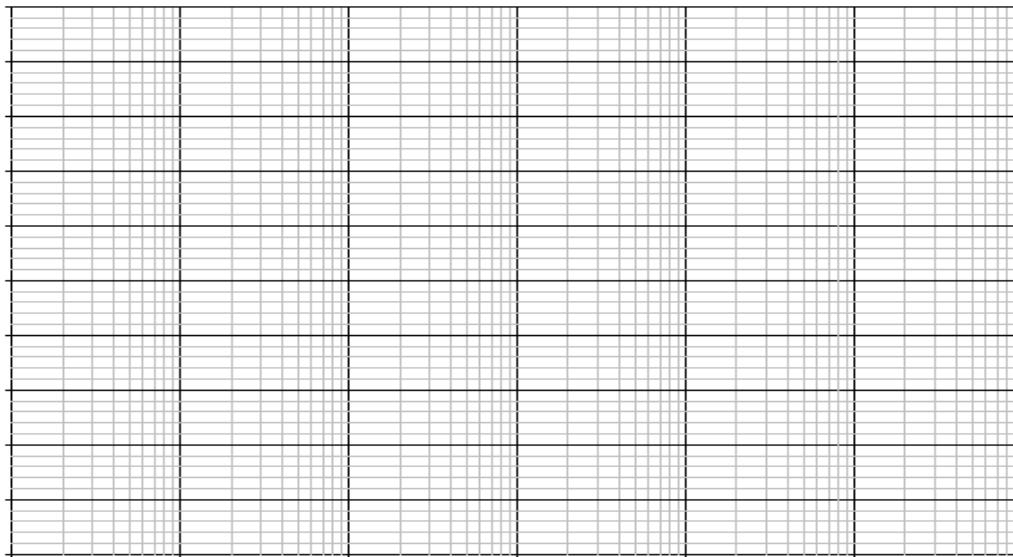c)  $H(s) = VR(s)/V(s)$  when  $R=10.1\text{k}\Omega$



$$V_{out} = V_R$$

$$H(s) = \frac{\frac{R}{L}s}{s^2 + \frac{R}{L} \cdot s + \frac{1}{LC}}$$

$$H(s) \text{ as } s \text{ goes to } 0 \quad H(s) = \frac{\frac{R}{L} \cdot s}{\frac{1}{LC}} = 0$$

$$H(s) \text{ as } s \text{ goes to } \infty \quad \frac{\frac{R}{L}s}{s^2} = 0$$

$$\text{Check the "middle"} \quad \text{rewrite as} \quad \frac{2\alpha s}{s^2 + 2\alpha s + \omega_0^2} \quad \text{where}$$

$$2\alpha = \frac{R}{L}$$

$$\text{Look at resonant frequency} \quad \omega_0 = \frac{1}{LC}$$

$$H(s) \text{ as } s \text{ goes to } j\omega_0$$

$$\frac{2\alpha \cdot (j\omega_0)}{-\omega_0^2 + 2\alpha(j\omega_0) + \omega_0^2} = 1 \quad \text{At the resonant frequency}$$

**Second order bandpass filter where  $\omega_0$  is the resonant frequency**

$$\text{If } R_L := 10.1\text{k}\Omega \quad L_L := 1\text{mH} \quad C_L := 1\text{nF} \quad \frac{1}{L_1 \cdot C_1} = 1 \times 10^{12} \frac{1}{\text{s}^2}$$

$$H(s) = \frac{2\alpha s}{s^2 + 2\alpha s + \omega_0^2}$$

$$H(s) = \frac{1.01 \cdot 10^7 s}{s^2 + 1.01 \cdot 10^7 s + 1 \cdot 10^{12}}$$

$$H(s) = \frac{1.01 \cdot 10^7 s}{(s + 10^5)(s + 10^7)}$$

$$H(s) = \frac{1.01 \cdot 10^7 s}{(s + 10^5) \cdot (s + 10^7)}$$

$$H(j\omega) = \frac{1.01 \cdot 10^7}{10^5 \cdot 10^7} \cdot \frac{j\omega}{\left(1 + \frac{j\omega}{10^5}\right) \cdot \left(1 + \frac{j\omega}{10^7}\right)}$$


zero: 0  
pole  $10^5, 10^7$

$$s < 10^5 \quad 1.01 \cdot 10^7 \cdot \frac{s}{(10^5) \cdot (10^7)} \quad \omega < 10^5 \quad 1.01 \cdot 10^{-5} \cdot \frac{\omega}{1 \cdot 1} \quad 20 \frac{\text{dB}}{\text{dec}} \quad 20 \log(1) = 0$$


$$10^5 < s < 10^7 \quad 1.01 \cdot 10^7 \cdot \frac{s}{(s) \cdot (10^7)} \quad \frac{1.01 \cdot 10^7}{10^7} \quad 10^5 < \omega < 10^7 \quad \frac{1.01 \cdot 10^{-5} \cdot \frac{\omega}{\omega}}{10^5} = 1.01 \cdot 10^{-5} \cdot 1.01 \cdot 10^5$$

constant

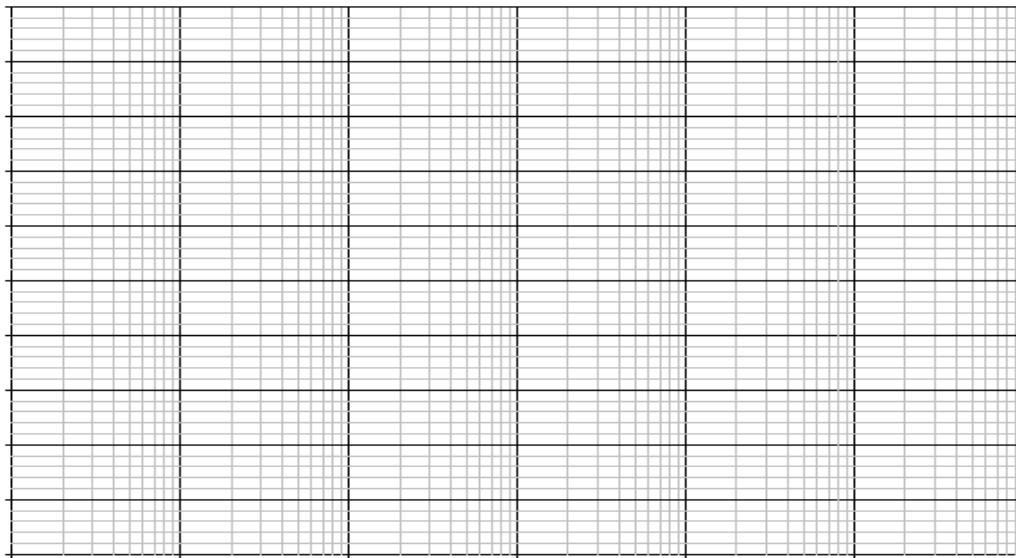
$$s > 10^7 \quad 1.01 \cdot 10^7 \cdot \frac{s}{(s) \cdot (s)} = \frac{1.01 \cdot 10^7}{s} \quad \omega > 10^7 \quad \frac{1.01 \cdot 10^{-5} \cdot \frac{\omega}{\omega^2}}{10^5 \cdot 10^7} \quad -20 \frac{\text{dB}}{\text{dec}}$$




Overdamped, bandpass filter

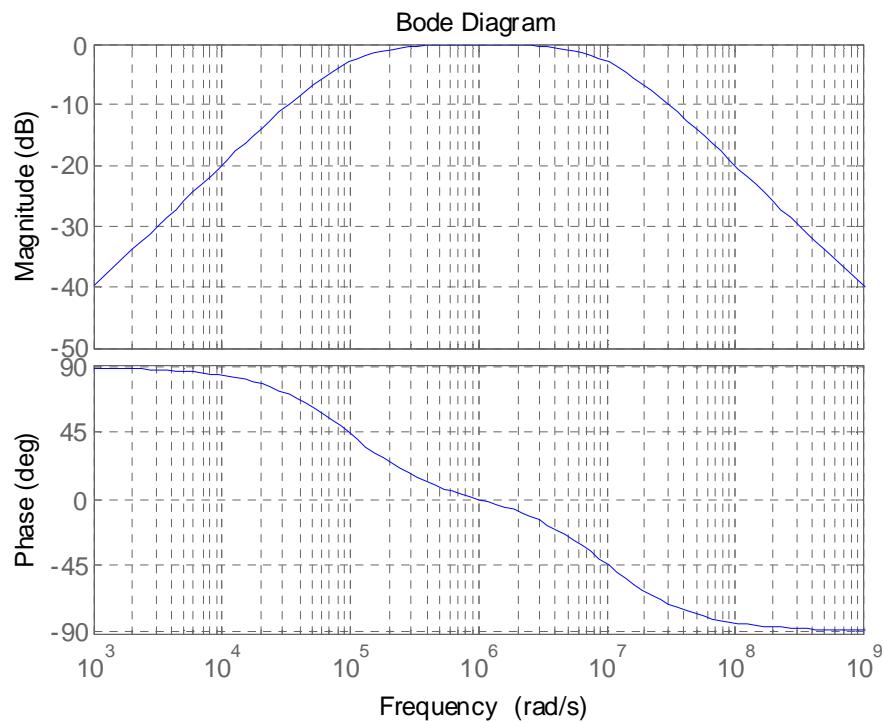
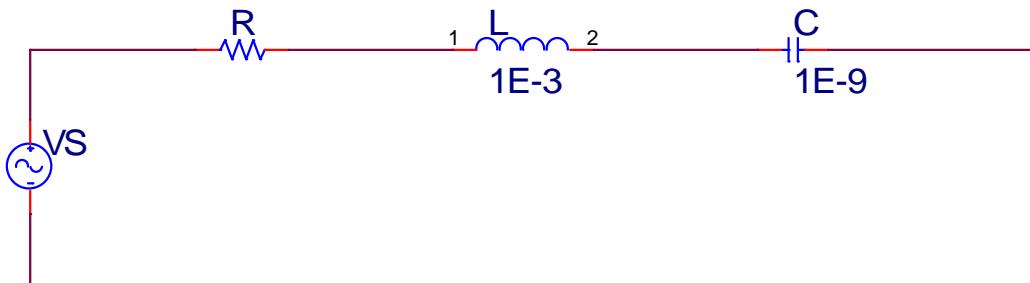
## 2) Second order circuits TEAM ASSIGNMENT



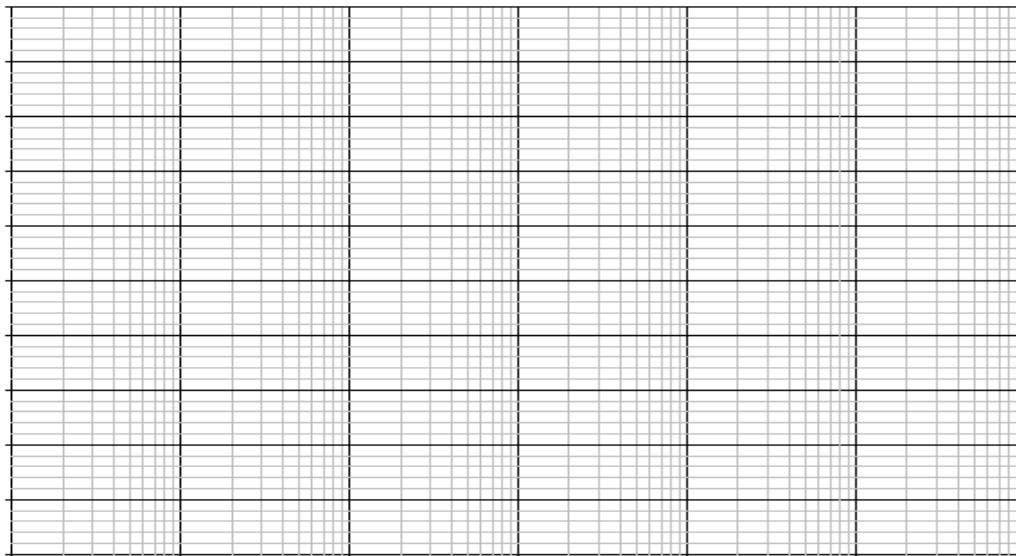a.  $H(s) = VC(s)/V(s)$  when  $R=2\text{k}\Omega$



$$R_{2a} := 2\text{k}\Omega$$

$$H(s) = \frac{\frac{1}{LC}}{s^2 + \frac{R_T}{L}s + \frac{1}{LC}}$$
$$\frac{1}{L_1 \cdot C_1} = 1 \times 10^{12} \frac{1}{\text{s}^2}$$
$$\frac{R_{2a}}{L_1} = 2 \times 10^6 \frac{1}{\text{s}}$$

$$H(s) = \frac{10^{12}}{s^2 + 2 \cdot 10^6 + 10^{12}}$$

$$H(s) = \left( \frac{10^6}{s + 10^6} \right)^2$$

$$H(s) = \left( \frac{10^6}{s + 10^6} \right) \left( \frac{10^6}{s + 10^6} \right)$$

equivalent to two cascaded first order filters

Zeros: none  
Poles 10^6 double

This is a critically damped second order circuit

critically damped low pass filter

If  $R_1 := 2k\Omega$        $L_1 := 1mH$        $C_1 := 1nF$        $\frac{1}{L_1 \cdot C_1} = 1 \times 10^{12} \frac{1}{s^2}$

$$H(s) = \frac{10^{12}}{s^2 + 2 \cdot 10^6 s + 10^{12}}$$

$$\alpha := \frac{2 \cdot 10^6}{2} = 1 \times 10^6$$

$$\omega_0 := \sqrt{\frac{1}{L_1 \cdot C_1}} = 1 \times 10^6 \frac{1}{s}$$

$$\zeta := \frac{\alpha}{\omega_0} = 1s \quad \text{This is = 1 critically damped}$$

$$H(s) = \frac{10^{12}}{(s + 10^6)^2}$$

$$H(j\omega) = \frac{10^{12}}{10^{12}} \cdot \frac{1}{\left(1 + \frac{j\omega}{10^6}\right)^2}$$

zero: none  
pole: double 10^6


$$s < 10^6 \quad \frac{10^{12}}{(10^6)^2} = 1 \quad \omega < 10^6 \quad 1 \quad 20 \cdot \log(1) = 0$$

$$s > 10^6 \quad \frac{10^{12}}{(s^2)} \quad \frac{10^{12}}{s^2} \quad \omega > 10^7 \quad \frac{1}{\omega^2} \quad -40 \frac{db}{dec}$$

correction -6 db

Critically damped case: double poles, Low pass filter

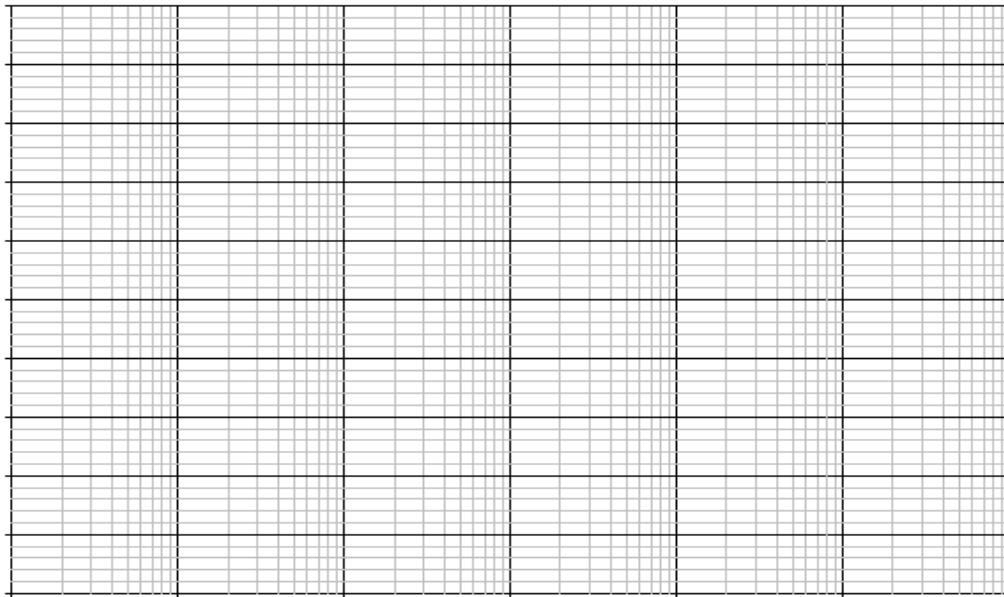b.  $H(s) = VL(s)/V(s)$  when  $R = 2k\Omega$



$$H(s) = \frac{s^2}{s^2 + \frac{R}{L} \cdot s + \frac{1}{LC}}$$

$$H(j\omega) = \frac{(j\omega)^2}{\left(1 + \frac{j\omega}{10^5}\right) \cdot \left(1 + \frac{j\omega}{10^7}\right)}$$

$$\text{If } R_1 := 2k\Omega \quad L_1 := 1mH \quad C_1 := 1nF \quad \frac{1}{L_1 \cdot C_1} = 1 \times 10^{12} \frac{1}{s^2}$$

$$H(s) = \frac{s^2}{s^2 + 2 \cdot 10^6 s + 10^{12}}$$

$$H(s) = \frac{s^2}{(s + 10^6)^2}$$

$$H(j\omega) = 10^{12} \cdot \frac{(j\omega)^2}{\left(1 + \frac{j\omega}{10^6}\right)^2}$$

zero: double 0  
pole: double pole  $10^6$

$$s < 10^6 \quad \frac{s^2}{(10^6)^2} \quad \omega < 10^6 \quad \frac{1}{10^{12}} \frac{\omega^2}{1} \quad 40 \frac{\text{dB}}{\text{dec}} \quad 20 \log(1) = 0$$


ends at

$$s > 10^6 \quad \frac{s^2}{2} = 1 \quad \omega > 10^6 \quad \frac{1}{10^{12}} \cdot \left[ \frac{\omega^2}{\frac{\omega^2}{(10^6)^2}} \right] \quad \text{constant} \quad 0 \text{ dB}$$

correction -6 dB

### Critically damped case: double poles, high pass filter

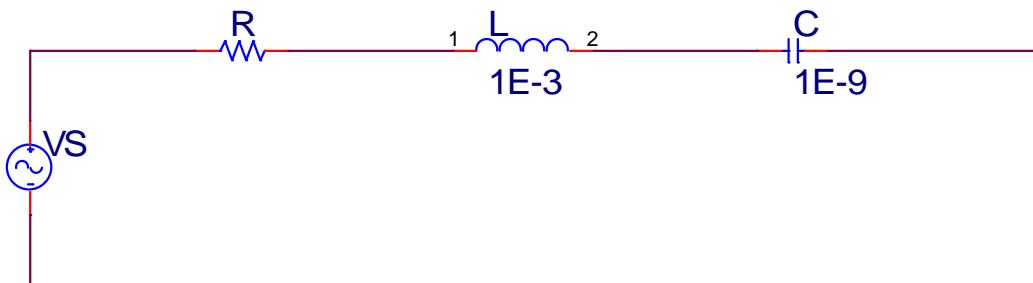3) Underdamped cases of the RLC series circuit



a.)  $H(s) = VC(s)/V(s)$  when  $R = 1\text{k}\Omega$

$$H(s) = \frac{1}{\frac{1}{LC} + \frac{R}{L}s + \frac{1}{LC}}$$

If  $R_{1k} := 1\text{k}\Omega$        $L_1 := 1\text{mH}$        $C_1 := 1 \cdot 10^{-9}\text{F}$

$$\frac{R_1}{L_1} = 1 \times 10^6 \frac{1}{\text{s}}$$

$$\frac{1}{L_1 \cdot C_1} = 1 \times 10^{12} \frac{1}{\text{s}^2}$$

$$H(s) = \frac{10^{12}}{s^2 + 10^6 s + 10^{12}}$$

$$\alpha := \frac{10^6}{2} = 5 \times 10^5$$

$$\omega_0 := \sqrt{\frac{1}{L_1 \cdot C_1}} = 1 \times 10^6 \frac{1}{\text{s}}$$

This is the resonant frequency

$$\zeta := \frac{\alpha}{\omega_0} = 0.5 \text{s}$$

***This is < 1 this is a very specific case of underdamped***

$$\begin{array}{lll} H(s) & s \text{ goes to } 0 & \text{goes to } 1 \\ & & \text{Still a low pass filter} \\ H(s) & \text{so goes to infinity} & \text{goes to } 0 \quad \frac{10^{12}}{s^2} \quad -40 \frac{\text{db}}{\text{dec}} \end{array}$$

**At the limits** you can start like a critically damped bode plot.

Critically damped  $\omega_0 = \omega_{\text{cutoff}}$  (were the same)

$$\begin{array}{lll} \text{At } \omega_0 \text{ evaluate } |H(j\omega_0)| & \text{so our } H(s) \text{ convert to } H(j\omega) & H(s) = \frac{1}{LC} = \frac{1}{s^2 + \frac{R}{L}s + \frac{1}{LC}} = \frac{1}{(j\omega)^2 + 2\alpha \cdot j \omega + \frac{1}{LC}} \\ \text{remember } \omega_0^2 = \frac{1}{LC} & & \end{array}$$

$$\frac{\omega_0^2}{-\omega_0^2 + 2\alpha j\omega_0 + \omega_0^2} = \frac{\omega_0^2}{2\alpha\omega_0 \cdot j} \quad \text{remember} \quad 0.5 = \frac{\alpha}{\omega_0} \quad \text{so} \quad \alpha = 0.5\omega_0$$

$$|H(j\omega_0)| = \frac{\omega_0}{2 \times 0.5\omega_0 \cdot j} = \frac{1}{j} \quad -j \quad \sqrt{-1^2}$$

$$|H(j\omega_0)| = 1$$

$$20 \log(|H(j\omega_0)|) = 0 \text{db} \quad \text{so we have a known point at } \omega_0 \text{ and we ELIMINATED the correction or gain loss so we have a better passband. It was -6dB}$$

Damping ratio of 0.5 gives you a flat passband with a 40 db rolloff, better than cascaded first order filter  
 b.)  $H(s) = VC(s)/V(s)$  when  $R = 1.41 k\Omega$

$$H(s) = \frac{1}{\frac{LC}{s^2 + \frac{R}{L}s + \frac{1}{LC}}}$$

If  $R_1 := 1.41\text{k}\Omega$        $L_1 := 1\text{mH}$        $C_1 := 1 \cdot 10^{-9}\text{F}$

$$\frac{R_1}{L_1} = 1.41 \times 10^6 \frac{1}{\text{s}}$$

$$\frac{1}{L_1 \cdot C_1} = 1 \times 10^{12} \frac{1}{\text{s}^2}$$

$$\alpha := \frac{1.41 \times 10^6}{2} = 7.05 \times 10^5$$

$$\omega_0 := \sqrt{\frac{1}{L_1 \cdot C_1}} = 1 \times 10^6 \frac{1}{\text{s}}$$

This is the resonant frequency

$$\zeta := \frac{\alpha}{\omega_0} = 0.705 \text{ s} \quad \frac{1}{\sqrt{2}}$$

**This is < 1 this is less underdamped than the previous**

$H(s)$   $s$  goes to 0    goes to 1

Still a low pass filter

$H(s)$   $s$  goes to infinity    goes to 0

$$|H(j\omega_0)| = \frac{1}{\sqrt{2}}$$

$$\frac{\omega_0^2}{-\omega_0^2 + 2\alpha j\omega_0 + \omega_0^2} = \frac{\omega_0^2}{2\alpha\omega_0 j}$$

$$20 \log\left(\frac{1}{\sqrt{2}}\right) = -3.01 \text{ dB}$$

So now this point is -3dB at  $\omega_0$

now       $\alpha = \frac{1}{\sqrt{2}}\omega_0$        $\frac{\omega_0}{2 \cdot \frac{1}{\sqrt{2}}\omega_{0j}}$

$$\frac{\sqrt{2}}{2} j \quad \left(\sqrt{\frac{\sqrt{2}}{2}}\right)^2 = 0.707 \quad \frac{1}{\sqrt{2}}$$

c.)  $H(s) = VC(s)/V(s)$  when  $R = 1.41\text{k}\Omega$

$$H(s) = \frac{1}{\frac{LC}{s^2 + \frac{R}{L}s + \frac{1}{LC}}}$$

If  $R_1 := 100\Omega$        $L_1 := 1\text{mH}$        $C_1 := 1 \cdot 10^{-9}\text{F}$

$$\frac{R_1}{L_1} = 1 \times 10^5 \frac{1}{\text{s}}$$

$$\frac{1}{L_1 \cdot C_1} = 1 \times 10^{12} \frac{1}{\text{s}^2}$$

$$\alpha := \frac{R_1}{2L_1} = 5 \times 10^4 \frac{1}{\text{s}}$$

$$\omega_0 := \sqrt{\frac{1}{L_1 \cdot C_1}} = 1 \times 10^6 \frac{1}{\text{s}}$$

This is the resonant frequency

$$\zeta := \frac{\alpha}{\omega_0} = 0.05$$

**This is << 1 this is very underdamped**

H(s) s goes to 0 goes to 1  
H(s) so goes to infinity goes to 0  $-40 \frac{db}{dc}$  Still a low pass filter

$$|H(j\omega_0)| = 10$$

$$\frac{\omega_0^2}{-\omega_0^2 + 2\alpha j\omega_0 + \omega_0^2} = \frac{\omega_0^2}{2\alpha\omega_0 j}$$

$$20\log(10) = 20 \text{ dB}$$

So now this point is 20dB at  $\omega_0$

$$\text{now } \alpha = 0.05\omega_0 \quad \frac{\omega_0}{2 \cdot 0.05\omega_0 j} = \frac{1}{0.1j}$$

$$2 \cdot 0.05 = 0.1$$

This creates a peak, a large one  
and is not necessarily a good low pass filter  
A flat passband is ideal remember.

$$-10j \quad \sqrt{(-10)^2} = 10$$

Basic process summary for second order circuits:

Overdamped

Bode plots

Critically damped

Find real poles, regions, analyze

Underdamped

Use critically damped approximation at the limits

Find correction at  $\omega_0$

$$1 > \zeta > 0.5$$

Correction is a -db of some value

$$\zeta = 0.5$$

Correction is 0db

$$\zeta < 0.5$$

Correction is positive db (Strongly underdamped which means there is a peak)