

## 1) Bode plots/Transfer functions

a. Draw magnitude and phase bode plots for the transfer function

$$H(s) = 0.01 \cdot \frac{s \cdot (s + 100)}{(s + 1E4)}$$

In your magnitude plot, indicate corrections at the poles and zeros.

Step 1: Find poles, zeros

Zeros: 0, 100

Poles: 1E4

Step 2: Define regions and find either  $H(j\omega)$  or  $H(s)$ 

$$\frac{100 \cdot 0.01}{1 \cdot 10^4} = 1 \times 10^{-4}$$

$s < 100$

$$H(s) = \frac{0.01 \cdot s \cdot 100}{1 \cdot 10^4} = 1 \cdot 10^{-4} s$$

+20db/dec slope

$$100 \cdot 1 \cdot 10^{-4} = 0.01$$

slope ends at  $20 \cdot \log(0.01) = -40$

$$100 < s < 10^4$$

$$H(s) = \frac{0.01 \cdot s \cdot s}{1 \cdot 10^4} = 1 \cdot 10^{-6} s^2$$

+40 db/dec slope

$$\frac{0.01}{1 \cdot 10^4} = 1 \times 10^{-6}$$

$$20 \log \left[ 10^{-6} \cdot (1 \cdot 10^4)^2 \right] = 40$$

$$s > 10^4$$

$$H(s) = \frac{0.01 \cdot s \cdot s}{s} = 0.01 s$$


+20db/dec slope

Step 3: Make corrections

Correction at 100 is +3db because it is a ZERO^1!

Correction at 10^4 is -3db because it is a POLE^1!
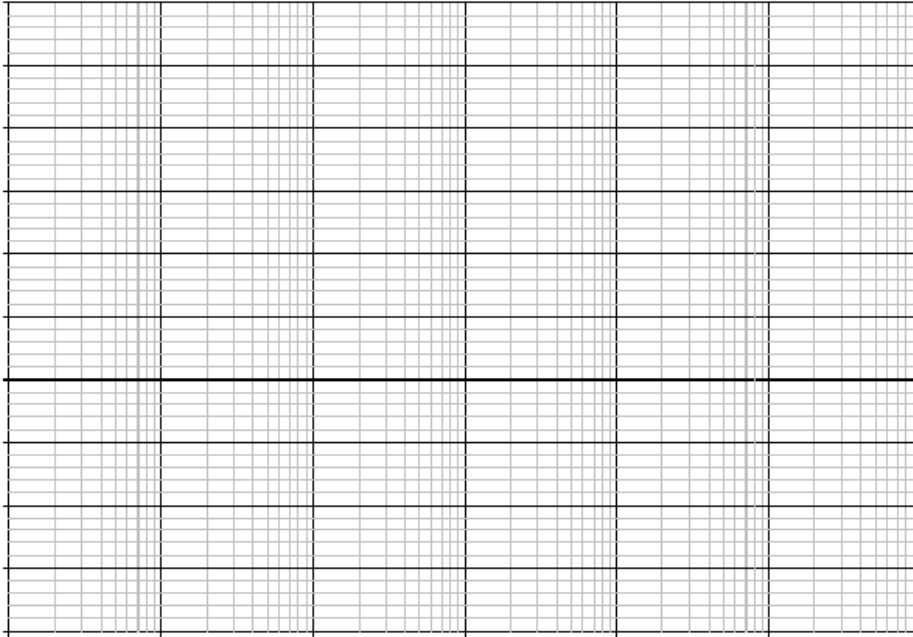
$$H(s) = 10 \frac{s^2}{(s+100)(s+10000)}$$



Phase plots

$$0.1\omega_{c1} = 10$$

$$\omega = 10$$

$$\angle H(j10) = 0.01 \cdot \frac{j10 \cdot (j10 + 100)}{(10j + 1E4)} \quad \frac{\angle 0 \cdot (\angle 90)(\angle 0)}{\angle 0} \quad \angle 90$$

$$\angle 0 + \angle 90 + \angle 0 - \angle 0$$

$$10 \cdot \omega_{c1} = 10^3$$

$$\omega = 10^3$$

$$\angle H(j10^3) = 0.01 \cdot \frac{j10^3 \cdot (j10^3 + 100)}{(10^3j + 1E4)} \quad \frac{\angle 0 \cdot (\angle 90)(\angle 90)}{\angle 0} \quad \angle 180$$

$$\angle 0 + \angle 90 + \angle 90 - \angle 0$$

$$180 - 45 = 135$$

$$\omega = 100 \quad \angle 135$$

$$0.1\omega_{c2} = 10^3 \quad \text{already done} \quad \angle 180$$

$$10\omega_{c2} = 10^5$$


$$\angle H(j10^5) = 0.01 \cdot \frac{j10^5 \cdot (j10^5 + 100)}{(10^5 j + 1E4)} \quad \frac{\angle 0 \cdot (\angle 90)(\angle 90)}{\angle 90} \quad \angle 90$$

$$\angle 0 + \angle 90 + \angle 90 - \angle 90$$


$$\omega = 10^4$$

$$\angle H(j10^4) = 0.01 \cdot \frac{j10^4 \cdot (j10^4 + 100)}{(10^4 j + 1E4)} \quad \frac{\angle 0 \cdot (\angle 90)(\angle 90)}{\angle 45} \quad \angle 135$$
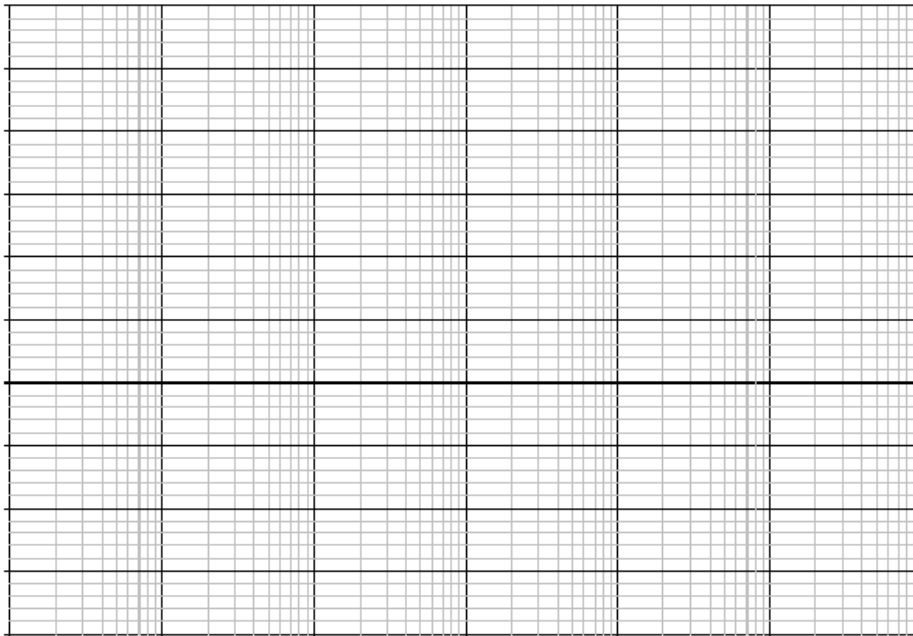
$$H(s) = 10 \frac{s^2}{(s+100)(s+10000)} \quad \angle 0 + \angle 90 + \angle 90 - \angle 45 \quad 180 - 45 = 135$$



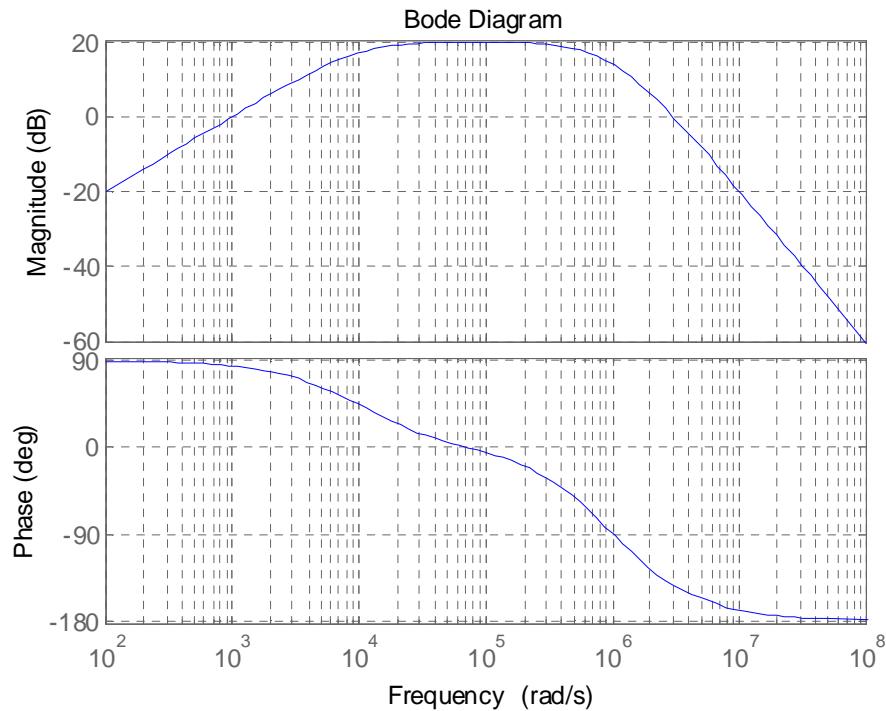b. Determine the transfer function for the following magnitude and phase Bode plots (the plots are for the same circuit).



1. We have a 20 db pass band so

$$20 \log(K) = 20 \text{ dB} \quad \frac{20}{20} = 1 \quad 10^1 = 10$$

$$K = 10$$

2. We have 40 db rolloff on the right where  $\omega_o = 1 \text{E}6$  rad/s, critically damped low pass filter, double pole there

$$\frac{(10^6)^2}{(s + 10^6)^2} = \left( \frac{\omega_o}{s + \omega_o} \right)^2$$


3. 1st order high pass filter, 20db rolloff,  $\omega_o = 10^4$  rad/s

$$\frac{s}{s + 10^4} = \frac{s}{s + \omega_o}$$

Put all together

$$H(s) = 10 \cdot \frac{10^{12}}{(s + 10^6)^2} \cdot \frac{s}{(s + 10^4)} = \frac{10 \cdot 10^{12} s}{(s + 10^4)(s + 10^6)^2}$$

## 2) 2nd order Bandpass Bode plots

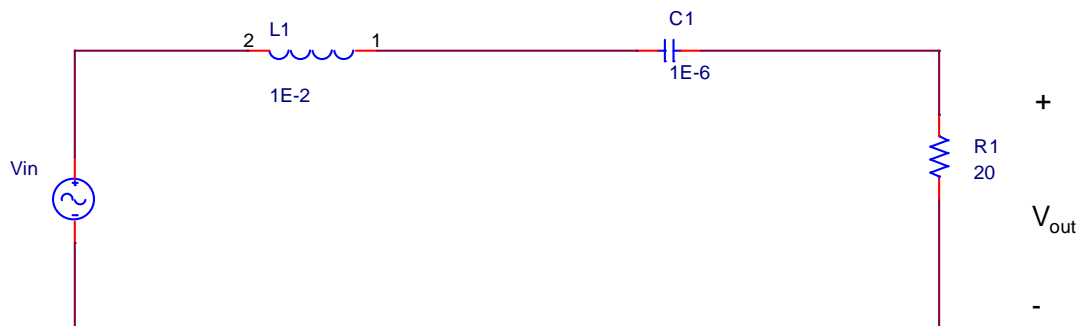

a. Determine the transfer function for the above circuit  $H(s) = \frac{V_R(s)}{V_{in}(s)}$

$$H(s) = \frac{2\alpha s}{s^2 + 2\alpha s + \omega_0^2} = \frac{\frac{R}{L} \cdot s}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$$R_2 := 20 \quad L_2 := 1 \cdot 10^{-2} \quad C_2 := 1 \cdot 10^{-6}$$

b. Determine  $\alpha$ ,  $\omega_0$ , and  $\zeta$  (damping ratio).

$$\frac{R_2}{L_2} = 2 \times 10^3 \quad \text{b) Band pass filter}$$

$$\alpha := 1000$$

$$\omega_0 := \sqrt{\frac{1}{L_2 \cdot C_2}} \quad 0\text{db}$$

$$\omega_0 = 1 \times 10^4$$

$$\zeta := \frac{\alpha}{\omega_0} \quad \zeta = 0.1$$

1. Asymptotes take the form of an inverted V
2. Each has a 20 db rolloff
3. At  $\omega_0$ ,  $20 \log \text{abs}(H(j\omega)) = 0\text{db}$  always
4. The point of the inverted V is  $20 \log \text{abs}(H(j\omega_0))$  away from  
 $20 \log(2\zeta)$  Narrow or wide?

c. Draw the Bode-magnitude plot. Indicate the magnitude (dB) of the transfer function at the resonant frequency.


Remember peak must always be at 0db at  $\omega_0$ , we have to figure out where the asymptotes will be +, - 20db/dec.

$$H(s) \quad s \text{ goes to } 0 \quad H(s) = \frac{2\alpha s}{\frac{1}{LC}} \quad +20\text{db/dec}$$

$$H(s) \quad s \text{ goes to } \infty \quad H(s) = \frac{2\alpha s}{s^2} \quad -20\text{db/dec}$$

$$H(j\omega_0) = \frac{2\alpha j\omega_0}{-\omega_0^2 + 2\alpha j\omega_0 + \omega_0^2} = 1 \quad \text{always! at } \omega_0 \quad 2 \cdot \zeta \cdot \omega_0^2 j$$

$$H(s) = \frac{s^2}{(s+100)(s+10000)}$$

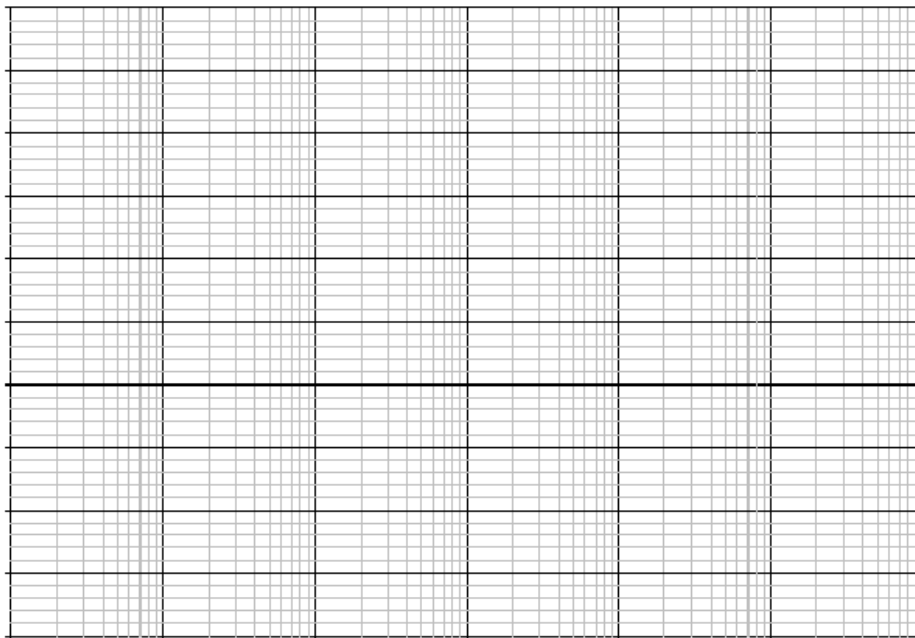

## 4) Design problems-Multiple Stages

Using only first order filters and opamp circuits for each stage, design a filter that meets the specifications below. You need to pick values for any resistors, capacitors or inductors in your circuit. Your circuit must consist of at least one inductor and at least one capacitor.

- Lowpass filter with a cutoff frequency of 1 MHz (Note: this value is given in Hz).
- In the passband, the gain must be >10dB
- The asymptotic slope of the stopbands should be -60dB/decade
- Your circuit must contain at least one inductor and at least one capacitor.

$$\omega_c := 2 \cdot \pi \cdot 1\text{MHz}$$

$$\omega_c = 6.283 \times 10^6 \frac{\text{rad}}{\text{s}}$$

$$\text{Gain} \quad 20\log|K| > 10\text{dB}$$

Slope indicates a triple pole

$$R_1 := 1.59\text{k}\Omega \quad C_1 := 1 \cdot 10^{-10}$$

$$R_3 := 6.28\text{k}\Omega$$

$$L_1 := 1 \cdot 10^{-3}\text{H}$$

Remember  $\omega_c = \frac{R}{L}$  for inductor/resistor across resistor

$$\frac{R_3}{L_1} = 6.28 \times 10^6 \frac{1}{\text{s}}$$

$\omega_c = \frac{1}{RC}$  for capacitor/resistor across capacitor

$$\frac{1}{R_1 \cdot C_1} = 6.289 \times 10^6 \frac{1}{\Omega}$$

$$R_4 := 90\text{k}\Omega \quad R_5 := 10\text{k}\Omega$$

Gain

$$\text{Amplifier} \quad \left( 1 + \frac{R_4}{R_5} \right) = 10$$

Note: Need to overcome the -9 dB loss at corner frequency to get >10 dB to meet spec. So that is ~20dB needed

$$20\log(10) = 20$$

Also need to isolate first order filters

use buffer

Solution 1:

Lowpass filter

Cutoff frequency of  $6.28\text{E}6 \text{ rad/s}$

Rolloff of 60dB/decade indicates a triple pole.

Three first order filters with amplifier stages for isolation.

-9dB point relative to the passband at  $6.28\text{E}6 \text{ rad/s}$

Passband gain of 20dB to meet spec,  $20\log|K|=20 \rightarrow K=10$



$$H(s) = K \left( \frac{\omega_c}{s + \omega_c} \right)^3$$

LPF stage, RL circuit: Choose an RL circuit,  $R = 6.28\text{k}$ ,  $L = 1\text{E}-3$

LPF stage, RC circuit: Choose an RC circuit,  $R = 1.59\text{k}$ ,  $C = 1\text{E}-10$

Amplifier stage: Choose a non-inverting amplifier,  $R_2=90\text{k}$ ,  $R_1=10\text{k}$

Isolation amplifier stage: unity gain

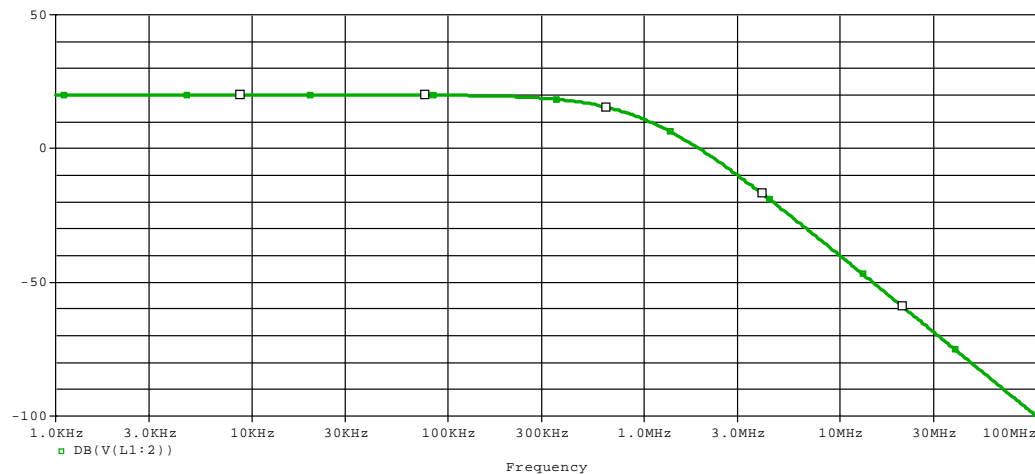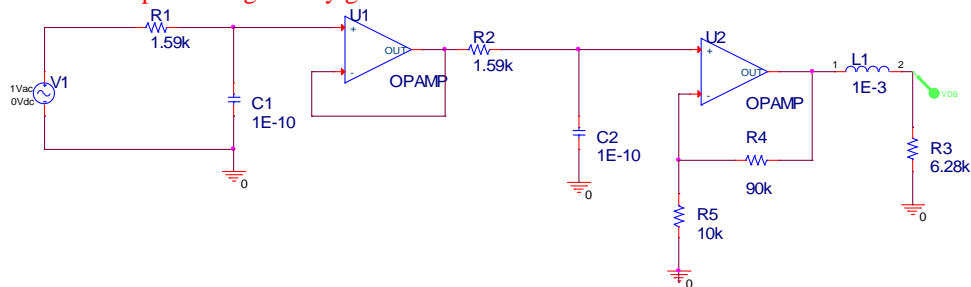



If restriction of only first order filter was lifted....you could also do....


### Solution 2:

Second order LPF cascaded with a first order LPF

Use an underdamped circuit with a damping ratio of 0.5.

The gain term then needs to be 13dB to satisfy the passband requirements, giving

$20\log|K|=13\text{dB}$ ,  $K=4.4$

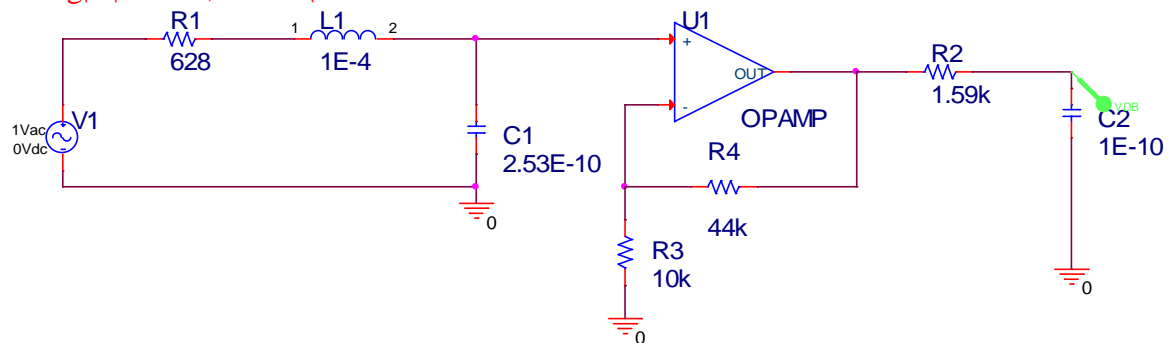

$$H(s) = \frac{1}{LC} \cdot \frac{1}{s^2 + \frac{R_T}{L}s + \frac{1}{LC}}$$

$$\omega_0 = \omega_c = 6.283 \times 10^6 \frac{\text{rad}}{\text{s}}$$

$$\omega_0 = \sqrt{\frac{1}{L_1 \cdot C_1}}$$

need **at least a** critically damped circuit, should use underdamped

choose  $L_1$  first if you like

$$L_{1b} := 1 \cdot 10^{-4}$$

$$\frac{1}{(\omega_0^2 \cdot L_1)} = C_1$$

$$\frac{1}{\left[ (6.283 \times 10^6)^2 \cdot L_{1b} \right]} = 2.533 \times 10^{-10}$$

$$\sqrt{\frac{1}{1 \cdot 10^{-4} \cdot 2.53 \cdot 10^{-10}}} = 6.287 \times 10^6$$

$$\zeta = \frac{\alpha}{\omega_0} \quad \text{For better filter make } \zeta=0.5$$

$$\alpha_b := 0.5 \cdot (6.283 \times 10^6)$$

$$2\alpha = \frac{R}{L}$$

$$R_{1b} := 2 \cdot \alpha_b \cdot L_{1b}$$

$$R_{1b} = 628.3$$

This gives -40 db roll off, with  $\omega_0$  at  $6.23 \cdot 10^6$  and a very flat passband

Still need another -20 db roll off so you can use a first order filter (like previous) which has -3dB rolloff

Gain

For this circuit we need over only overcome -3dB so that means a total of 13 dB

$$20 \log |K| = 13$$

$$\frac{13}{20} = 0.65$$


$$10^{0.65} = 4.467$$

Can use a non inverting amplifier with a gain of 4.5

$$R_{4b} := 35k\Omega$$

$$R_{3b} := 10k\Omega$$
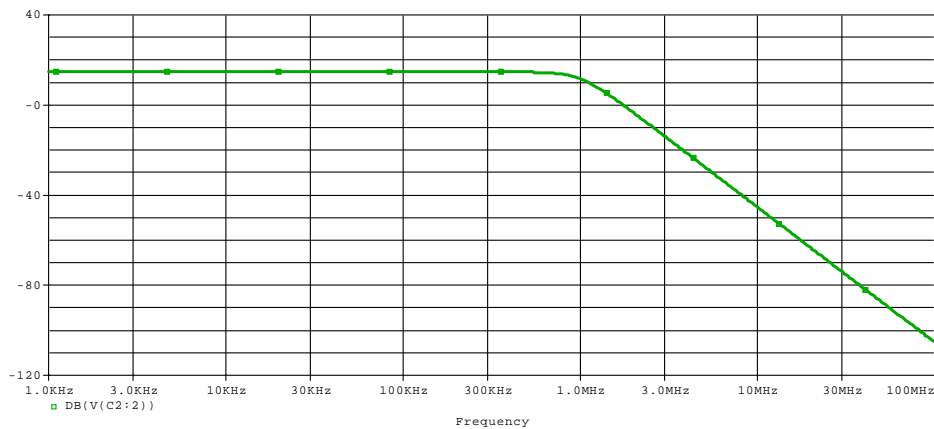
$$\left( 1 + \frac{R_{4b}}{R_{3b}} \right) = 4.5$$



## 5) Design Problem

Design a bandpass filter with the following specifications. Show your work and justify your calculations. Include a schematic of your circuit.

- The passband is  $1\text{E}4 < \omega < 1\text{E}6$
- The passband gain should be 5dB
- The low frequency stopband rolloff should be 20dB/decade
- The high frequency stopband rolloff should be 60 dB/decade
- The low frequency cutoff frequency,  $1\text{E}4$  [rad/s] should be -3dB relative to the passband.
- The high frequency cutoff frequency,  $1\text{E}6$  [rad/s], should be -3dB relative to the passband.
- You cannot use any first order circuit stages

Build the circuit using BPF LPF

BPF	$\omega_{c\text{Low}} = 10^4$	$\omega_{c\text{High}} = 10^6$	2nd order overdamped circuit measured across the resistor
	-3 corrections $20 \frac{\text{dB}}{\text{dec}}$	-3 corrections $20 \frac{\text{dB}}{\text{dec}}$	R must give $\zeta > 1$
LPF	$\omega_c = 10^6$ (double)		
	need 0dB correction at $10^6$	2nd order underdamped $\zeta = 0.5$	
	$40 \frac{\text{dB}}{\text{dec}}$ rolloff		

pass band gain

$$20 \log(K) = 5 \text{ dB}$$

$$K = 1.77$$

Non inverting amp

choose R1

$$R_1 = 1\text{k}$$

$$R_2 = 0.77\text{k}$$

$$\left(1 + \frac{0.77\text{k}\Omega}{1\text{k}\Omega}\right) = 1.77$$

$$\left(1 + \frac{R_2}{R_1}\right)$$

BPF

$$H(s) = \frac{2\alpha s}{s^2 + 2\alpha s + \omega_0^2}$$

you know that  
denominator must  
be

$$(s + 10^4)(s + 10^6)$$

expand and  $2\alpha$  in  
numerator can be  
given by doing so

$$s^2 + 1010000 \cdot s + 10000000000$$

$$H(s) = \frac{1.01 \cdot 10^6 s}{(s + 10^4)(s + 10^6)}$$

Now find R/L you can pick R or L

$$L = 10^{-3}$$

$$R = 10^{-3} \cdot 1.01 \cdot 10^6 \quad 10^{-3} \cdot 1.01 \cdot 10^6 = 1.01 \times 10^3$$

$$R = 1.01k$$

$$C = 1 \cdot 10^{-7}$$

$$\omega_0^2 = \frac{1}{LC}$$

$$\frac{1}{10^{10} \cdot 1 \cdot 10^{-3}} = 1 \times 10^{-7}$$

LPF

$$H(s) = \frac{\omega_0^2}{s^2 + 2\alpha s + \omega_0^2}$$

you know that denominator  
must be

$$\frac{1}{(s + 10^6)^2} \quad \omega_c = \omega_0$$

$$\omega_0 = 10^6$$

$$\alpha = 0.5 \cdot \omega_0 \quad \text{this is the underdamped condition where correction is 0dB}$$

$$\alpha = 5 \cdot 10^5$$

pick  $L = 1 \cdot 10^{-3}$

$$\omega_0^2 = \frac{1}{LC}$$

$$C = \frac{1}{10^{12} \cdot 1 \cdot 10^{-3}}$$

$$\frac{1}{10^{12} \cdot 1 \cdot 10^{-3}} = 1 \times 10^{-9}$$

$$C = 1 \cdot 10^{-9}$$

$$2\alpha = \frac{R}{L}$$

$$2 \cdot 5 \cdot 10^5 \cdot 1 \cdot 10^{-3} = 1 \times 10^3$$

$$R = 1k$$

