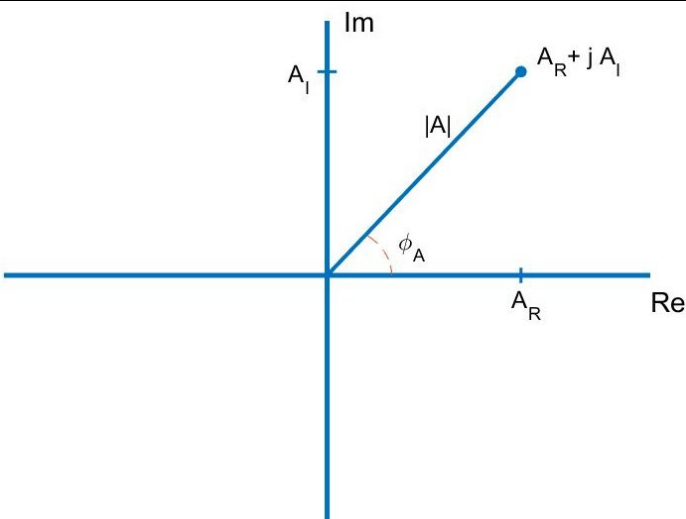



Exam 3 Crib Sheet

Complex Numbers		
	<p>Rectangular form: $A = A_R + jA_I$</p> <p>Polar form: $A \angle \varphi_A$</p> <p>Rectangular to polar $A = \sqrt{(A_R)^2 + (A_I)^2}$ $\varphi_A = \tan^{-1} \left(\frac{A_I}{A_R} \right)$</p> <p>Polar to rectangular $A_R = A \cos(\varphi_A)$ $A_I = A \sin(\varphi_A)$</p>	
Euler's Law: $e^{j\theta} = \cos(\theta) + j \sin(\theta)$		
Mathematics with complex number		
<p>Addition/Subtraction – Rectangular form $A + B = (A_R + B_R) + j(A_I + B_I)$ $A - B = (A_R - B_R) + j(A_I - B_I)$</p> <p>Complex conjugate $A = A_R + jA_I \quad A^* = A_R - jA_I$</p>	<p>Multiplication/Division – Rectangular form $AB = A B \angle (\varphi_A + \varphi_B)$ $\frac{A}{B} = \frac{ A }{ B } \angle (\varphi_A - \varphi_B)$</p> <p>Complex conjugate $A = A \angle \varphi_A \quad A^* = A \angle -\varphi_A$</p>	
AC Steady State signals		
<p>Time domain signals $F(t) = A_o \cos(\omega t + \theta)$ A_o – amplitude ω – radial frequency, $2\pi f$ Θ – phase</p>	<p>Phasor signals $\tilde{F} = A_o \angle \theta$ A_o – amplitude Θ – phase</p>	
<p>(Rectangular form) $F(t) = A_o \cos(\omega t + \theta) \leftrightarrow A_o \Re\{e^{j(\omega t + \theta)}\} \leftrightarrow A_o e^{j\theta} \leftrightarrow A_o \angle \theta$ (Phasor form)</p>		
Impedances – Laplace domain (zero initial conditions)		
$Z_R = R$	$Z_L = sL$	$Z_C = \frac{1}{sC}$
Impedances – AC steady state		
$Z_R = R$ $Z_R = R \angle 0^\circ$	$Z_L = j\omega L$ $Z_L = \omega L \angle 90^\circ$	$Z_C = \frac{1}{j\omega C}$ $Z_C = \frac{1}{\omega C} \angle -90^\circ$
<p><i>Impedance, $Z [\Omega]$, properties have the same characteristics as resistance</i></p> <p><i>In series add, $Z_{EQ} = Z_1 + Z_2$ In parallel, inverse relationship, $Z_{EQ} = \left(\frac{1}{Z_1} + \frac{1}{Z_2}\right)^{-1} = \frac{Z_1 Z_2}{Z_1 + Z_2}$</i></p>		
<p><i>Admittance, $Y [mho]$, properties have characteristics that are the 'inverse' of impedance</i></p> <p><i>In parallel, add, $Y_{EQ} = Y_1 + Y_2$ In series, inverse relationship, $Y_{EQ} = \left(\frac{1}{Y_1} + \frac{1}{Y_2}\right)^{-1} = \frac{Y_1 Y_2}{Y_1 + Y_2}$</i></p>		
AC Steady State Power		
<p style="text-align: center;">$S = P + jQ$</p> <p>S – Complex power</p>	<p>Using Ohm's Law relationships for impedances (Z)</p>	


Exam 3 Crib Sheet

<p>P – Real power, [W] Q – Reactive power, [VAR] S – Apparent Power, [VA]</p>	$P = I_{RMS}^2 Z \cos \theta$ $= I_{RMS}^2 R(\omega)$ $= V_{RMS} I_{RMS} \cos \theta$ <p style="text-align: right;">{ Equivalent ways of expressing Real Power [Watts]</p> $Q = I_{RMS}^2 Z \sin \theta$ $= I_{RMS}^2 X(\omega)$ $= V_{RMS} I_{RMS} \sin \theta$ <p style="text-align: right;">{ Equivalent ways of expressing Reactive Power [VAR's]</p> <p>If using V_{RMS}^2 version of equations also divide by Z (phasor form) *cos or sin θ OR must use complex conjugate of Z (rectangular form)</p>
<p>Capacitive reactance is negative ($Q < 0$)</p> <p>Inductive reactance is positive ($Q > 0$)</p> <p>Power produced by the source(s) is equal to the sum of the power produced/stored for each impedance in the circuit</p>	<p>Power factor – a metric over how efficient power consumption/production appears to be</p> <p style="text-align: center;">$0 < \text{power factor} < 1$</p> <p style="text-align: center;">Power factor = $\frac{P}{ S } = \cos(\phi_S)$</p>

Power Triangle

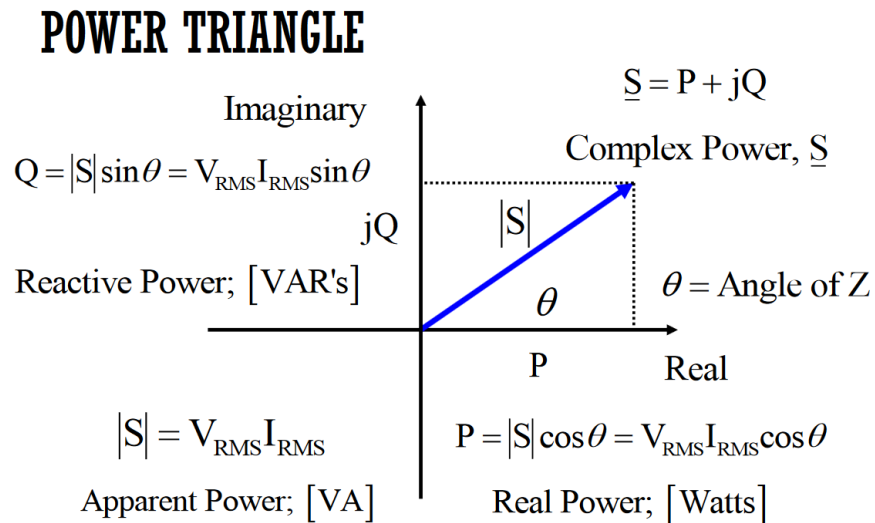


Ideal Transformers

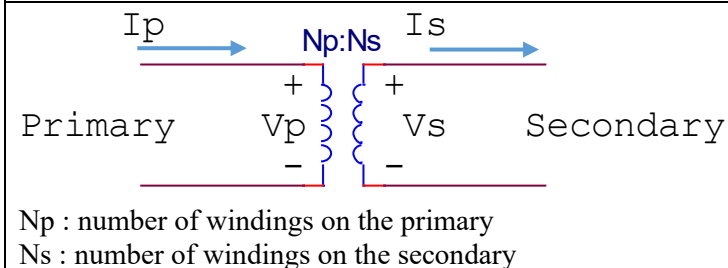


Primary: source side of the transformer
Secondary: load side of the transformer
The winding ratio, $N = \frac{N_s}{N_p}$
Voltage relationship, $V_s = N V_p$
Current relationship, $I_s = \frac{I_p}{N}$

Exam 3 Crib Sheet

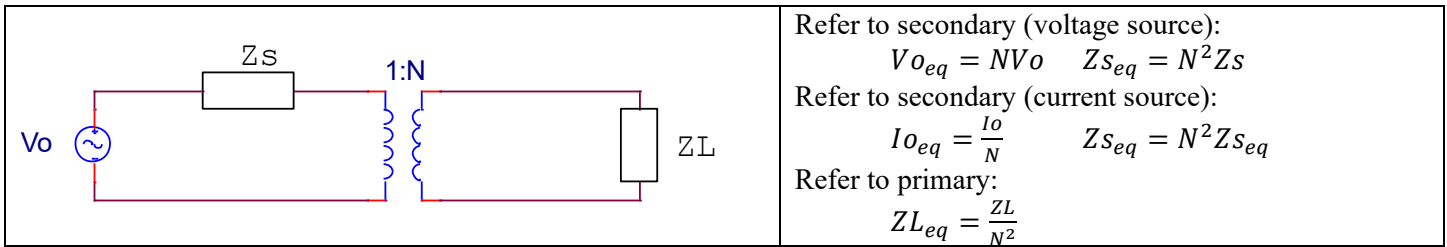


Mutual Inductance

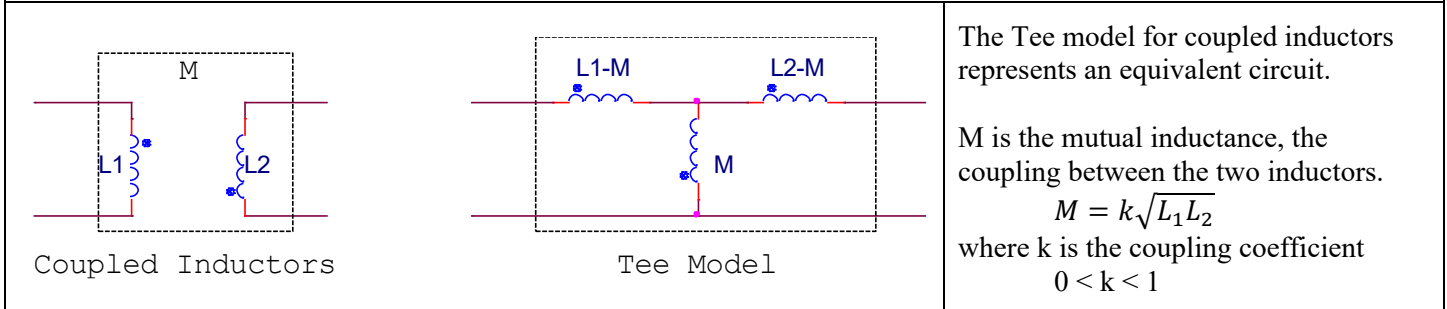


Student Requested Add-ons

REFERRAL TO PRIMARY

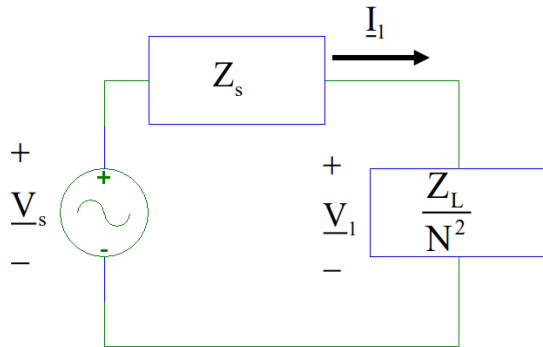

REFERRAL TO SECONDARY

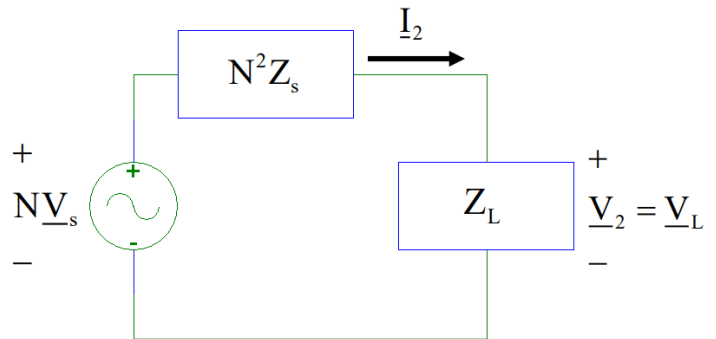

<i>Complex Power</i>	
$P = I_{RMS}^2 Z \cos\theta$	$Q = I_{RMS}^2 Z \sin\theta$
$P = I_{RMS}^2 R(\omega)$	$Q = I_{RMS}^2 X(\omega)$
$P = V_{RMS} I_{RMS} \cos\theta$	$Q = V_{RMS} I_{RMS} \sin\theta$
<i>Notes</i>	
$R(\omega) = Z_{REAL}$	$X(\omega) = Z_{IMG}$
$\theta = \text{Angle of Impedance}$	$\theta = \tan^{-1}\left(\frac{Z_{IMG}}{Z_{REAL}}\right)$
$\theta > 0 \Rightarrow I \text{ lags } V \text{ (Ind.)}$	$\theta < 0 \Rightarrow I \text{ leads } V \text{ (Cap.)}$