

Circuits

Exam 3

Fall 2020

1.	/30
2.	/70
Total	/100

Name _____


Notes:

- 1) If you are stuck on one part of the problem, choose ‘reasonable’ values on the following parts to receive partial credit
- 2) You don’t need to simplify all your numerical calculations. For example, you can leave square root terms in radical form.

Sorry that I forgot to integrity statement. I will use you name placed anywhere on your papers as your signature!

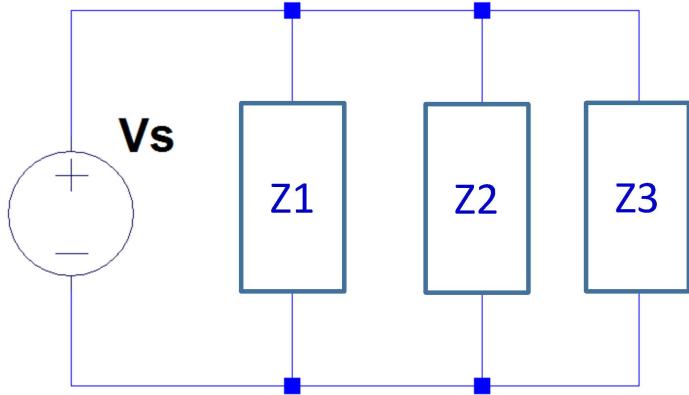1) Power Circuits (30 points)

In this circuit, the total source power, S , is 50,000 VA with a 60 Hz, 1,000 VRMS voltage. The power factor for the entire parallel load is 0.74 lagging. The loads are described below:



Z1: Capacitive load with value you specify ____ μF

Z2: Inductive load $L = 0.2 \text{ H}$ with real loss, $R = \text{____} \Omega$,

Z3: Unknown load (value(s) depend on your choices above)

1.1: (28 pts) Determine the values in the table below. Please show all work for full credit! Every box is worth 2 points. Partial credit is not given for wrong answers in boxes.

	P[W]	Q [VAR]	S [VA]	power factor
Load 1				0
Load 2				
Load 3				
Source				0.74 lagging

$$S_{\text{Totalabs}} := 50000 = 5 \times 10^4$$

$$\text{pf} := 0.74$$

$$\theta := \text{acos(pf)}$$

$$S_{\text{Total}} = P_{\text{Total}} + j \cdot Q_{\text{Total}}$$

$$\theta = 42.269 \cdot \text{deg}$$

$$P_{\text{Total}} := \text{pf} \cdot S_{\text{Totalabs}}$$

$$Q_{\text{Total}} := S_{\text{Totalabs}} \cdot \sin(\theta)$$

$$P_{\text{Total}} = 3.7 \times 10^4$$

$$Q_{\text{Total}} = 3.363 \times 10^4 \text{ VARs}$$

*lagging means
QTotal is positive*

$$|S| = \text{check}$$

$$\sqrt{P_{\text{Total}}^2 + (Q_{\text{Total}})^2} = 5 \times 10^4 \text{ VA}$$

Load 1: Capacitive element

$$f_1 := 60\text{Hz}$$

$$\omega_1 := 2 \cdot \pi \cdot f_1 = 376.991 \frac{1}{\text{s}}$$

1st way to solve:

Can use source voltage

$$V_{\text{RMS}} := 1000\text{V} \quad C_1 := 2.3\mu\text{F}$$

$$Z_{C1} := \frac{-j}{C_1 \cdot \omega_1} = -1.153i \times 10^3 \Omega$$

Another way to solve:

$$Z_{C1} = 1.153 \cdot 10^3 \angle -90^\circ$$

$$Z_{C1\text{mag}} := 1.153 \cdot 10^3 \quad \theta_{C1\text{phase}} := -90\text{deg}$$

note: θ is 0 degrees because it is purely resistive. There is not j or imaginary part in for a purely resistive load.

$$S_1 = \frac{(|V_{\text{RMS}}|)^2}{Z_{C1\text{mag}}} \cdot \cos(\theta_{C1\text{phase}}) + j \cdot \frac{(|V_{\text{RMS}}|)^2}{Z_{C1\text{mag}}} \cdot \sin(\theta_{C1\text{phase}})$$

$$S_1 := \left[\frac{(|V_{\text{RMS}}|)^2}{Z_{C1\text{mag}}} \cdot \cos(\theta_{C1\text{phase}}) + \frac{(|V_{\text{RMS}}|)^2}{Z_{C1\text{mag}}} j \cdot \sin(\theta_{C1\text{phase}}) \right] \quad \cos(\theta_{C1\text{phase}}) = 0$$

$$P_1 := \frac{(|V_{\text{RMS}}|)^2}{Z_{C1\text{mag}}} \cdot 0 = 0$$

$$Q_1 := \frac{(|V_{\text{RMS}}|)^2}{Z_{C1\text{mag}}} \cdot \sin(\theta_{C1\text{phase}}) = -867.303 \text{ V}^2$$

$$S_1 = 0 - j867$$

$$P_1 = 0 \quad \text{W}$$

$$Q_1 := -867 \quad \text{VAR}$$

$$|S_1| = 867 \text{ VA}$$

$$\text{pf}_1 := \frac{P_1}{|S_1|} = 0$$

Load 2: Inductive element with real loss, R=5.7Ω, L=0.2H

$$Z_2 = Z_{R2} + Z_{L2} \quad \text{Now there is a real AND imaginary part to the load.}$$

$$Z_{R2} = 5.7\Omega$$

$$L_2 := 0.2\text{H}$$

$$\omega_1 := 2 \cdot \pi \cdot 60 = 376.991$$

$$Z_{L2} := L_2 \cdot \omega_1 \cdot j = 75.398i\text{H}$$

Mathcad turns j into i

$$Z_2 = 5.7 + j \cdot 75.4 = 75.43 \angle 85.7^\circ = |Z_{2\text{mag}}| \cdot \angle \theta_{Z2}$$

$$\sqrt{5.7^2 + (75.4)^2} = 75.615$$

$$V_{RMS} = 1000 \quad \text{Given}$$

$$Z_{2\text{mag}} := 75.615 \quad \theta_{Z2} := 85.689\text{deg}$$

$$\tan\left(\frac{75.62}{5.7}\right) = 85.689\cdot\text{deg}$$

$$S_2 = \frac{(|V_{RMS}|)^2}{Z_{2\text{mag}}} \cdot \cos\theta_{Z2} + j \frac{(|V_{RMS}|)^2}{Z_{2\text{mag}}} \cdot \sin\theta_{Z2}$$

$$S_2 = 994.117 + 1.319 \times 10^4 j$$

$$\frac{V_{RMS}^2}{Z_{2\text{mag}}} \cdot \cos(\theta_{Z2}) = 994.117 V^2$$

$$\frac{V_{RMS}^2}{Z_{2\text{mag}}} \cdot \sin(\theta_{Z2}) = 1.319 \times 10^4 V^2$$

$$P_2 := 994.117$$

$$Q_2 := 1.319 \times 10^4$$

$$S_{2\text{abs}} := \sqrt{P_2^2 + Q_2^2} = 1.323 \times 10^4$$

$$pf_{\text{Load2}} := \frac{P_2}{S_{2\text{abs}}} = 0.075$$

To get the unknown load we need the total power, then we can subtract S1 and S2 from it.

Load 3:

$$S_3 = S_{\text{tot}} - S_1 - S_2 \quad pf_{\text{Tot}} := 0.74$$

$$P_3 := P_{\text{Total}} - P_1 - P_2 = 3.601 \times 10^4$$

$$Q_3 := Q_{\text{Total}} - Q_1 - Q_2 = 2.131 \times 10^4$$

check

$$Q_3 + Q_1 + Q_2 = 3.363 \times 10^4$$

$$Q_{\text{Total}} = 3.363 \times 10^4$$

$$pf_3 := \frac{P_3}{S_{3\text{abs}}} = 0.861$$

1.2: (2 pts) What are the component values for your unknown load? Enter the values that correspond to your circuit. You may leave the component value that doesn't exist in your circuit blank.

$$\cos(\text{pf}_3) = 30.616 \cdot \text{deg}$$

$$\frac{(|V_{RMS}|)^2}{Z_{L3mag}} \cdot \text{pf}_3 = P_3$$

$$Z_{L3mag} := \frac{(|V_{RMS}|)^2}{P_3} \cdot \text{pf}_3 = 23.902 V^2$$

positive because it is leading pf

$$R_3 := 23.902 \cdot \cos(30.616\text{deg}) = 20.57$$

$$X_3 := 23.902 \cdot \sin(30.616\text{deg}) = 12.173$$

$$X_3 = j \cdot L_3 \cdot \omega_1$$

$$L_3 := \frac{X_3}{\omega_1} = 0.032$$

My check

$$Z_{RL3} := 20.57 + 12.173j \quad X_3 = 12.173$$


$$L_3 := 0.032$$

$$R_3 := 20.57$$

$$Z_3 := L_3 \cdot \omega_1 \cdot j = 12.064i$$

$$\sqrt{R_3^2 + (X_3)^2} = 23.902 \quad \text{atan}\left(\frac{X_3}{R_3}\right) = 30.616 \cdot \text{deg}$$

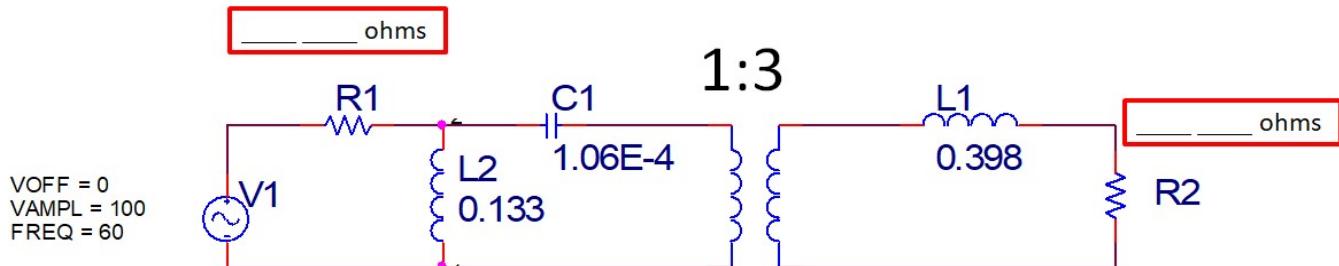Problem 2) Ideal Transformer Circuit (70 pts)



2.1: **30 pts**) Choose the values of R1 and R2. (i.e 15 ohms and 78 ohms. respectively...) **You may use either referral method though one referral method is one less step. (30 pts)**

The above circuit has a 100 V, 60 Hz source.

$$\begin{aligned} V_1 &:= 100\text{V} & R_1 &:= 33\Omega & C_1 &:= 1.06 \cdot 10^{-4}\text{F} & R_2 &:= 55\Omega \\ f &:= 60\text{Hz} & L_2 &:= 0.133\text{H} & L_1 &:= 0.398\text{H} \\ \omega &:= 2 \cdot \pi \cdot f & N_1 &:= 3 & Z_{R2} &:= R_2 \\ \omega &= 376.991 \frac{1}{\text{s}} & \frac{-1}{C_1 \cdot \omega} &= -25.024\Omega & L_1 \cdot \omega &= 150.042\Omega \\ L_2 \cdot \omega &= 50.14\Omega & Z_{L2} &:= 50j\Omega & Z_{C1} &:= -25j\Omega & Z_{L1} &:= 150j\Omega \end{aligned}$$

Convert to thevenin using a voltage divider (for voltage across L2...)

$$V_{Th} := V_1 \cdot \frac{Z_{L2}}{R_1 + Z_{L2}}$$

$$V_{Th} = (69.657 + 45.974i)\text{V}$$

$$\sqrt{70^2 + 46^2} = 83.762$$

$$\text{atan}\left(\frac{46}{70}\right) = 33.311 \cdot \text{deg}$$

$$83.8 < 33\text{deg}$$

Combine secondary impedances


$$Z_{Load} := Z_{L1} + R_2$$

$$Z_{Load} = (55 + 150i)\Omega$$

(recognition and correct use of thevenin 7 pts)
They can leave any value in polar or rectangular form.

Find thevenin impedance by shorting source then combining like resistors
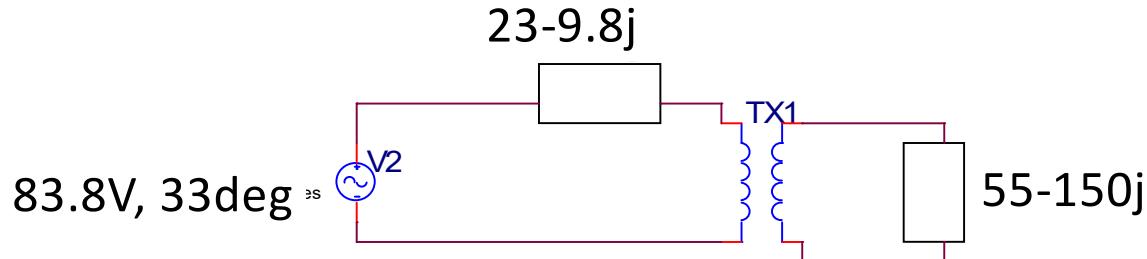
$$Z_{Th} := \frac{R_1 \cdot Z_{L2}}{R_1 + Z_{L2}} + Z_{C1} \quad Z_{Th} = (22.987 - 9.829i) \Omega$$



Equivalent circuit:

1st equivalent circuit: Refer to secondary

$$Z_{sps} := N_1^2 \cdot Z_{Th} \quad Z_{LEQps} := Z_{Load}$$

$$Z_{sps} = (206.882 - 88.458i) \cdot \Omega \quad Z_{LEQps} = (55 + 150i) \Omega$$

$$V_{sps} := N_1 \cdot V_{Th}$$

$$V_{sps} = (208.972 + 137.921i) V$$


$$\sqrt{279^2 + 184^2} = 334.211$$

$$\text{atan}\left(\frac{184}{279}\right) = 33.405 \cdot \text{deg}$$

$$334 < 33\text{deg}$$

This one should be preferred since you are looking for the voltage across R_2 .

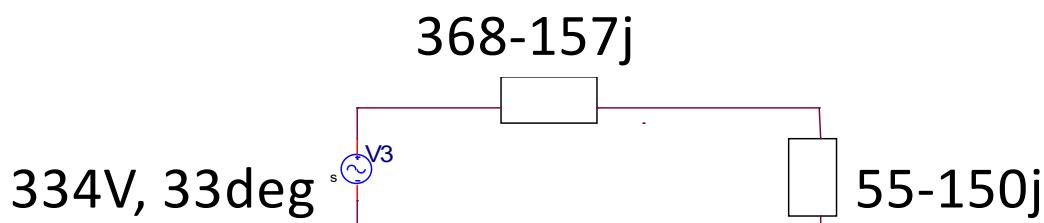Correct referral process (either one) 7 pts
Correct values 1 pt



Use refer to secondary. You can use voltage divider to find it.

$$V_{LEQ} := V_{sps} \cdot \left[\frac{Z_{LEQps}}{(Z_{sps}) + (Z_{LEQps})} \right]$$

$$\frac{Z_{LEQps}}{(Z_{sps}) + (Z_{LEQps})} = 0.327 + 0.496i$$

$$V_{LEQ} = (-0.166 + 148.699i) V$$

$$V_{R2} := V_{LEQ} \cdot \frac{Z_{R2}}{Z_{LEQps}} = (48.042 + 17.676i) V$$

$$\sqrt{(0.124)^2 + 0.357^2} = 0.378$$

$$\text{atan}\left(\frac{0.357}{0.124}\right) = 70.846 \cdot \text{deg}$$


$$\sqrt{35.825^2 + (24.538)^2} = 43.423$$

$$\text{atan}\left(\frac{24.538}{35.825}\right) = 34.409 \cdot \text{deg}$$

$$43.423 < 34.409 \text{deg}$$

R2	
----	--

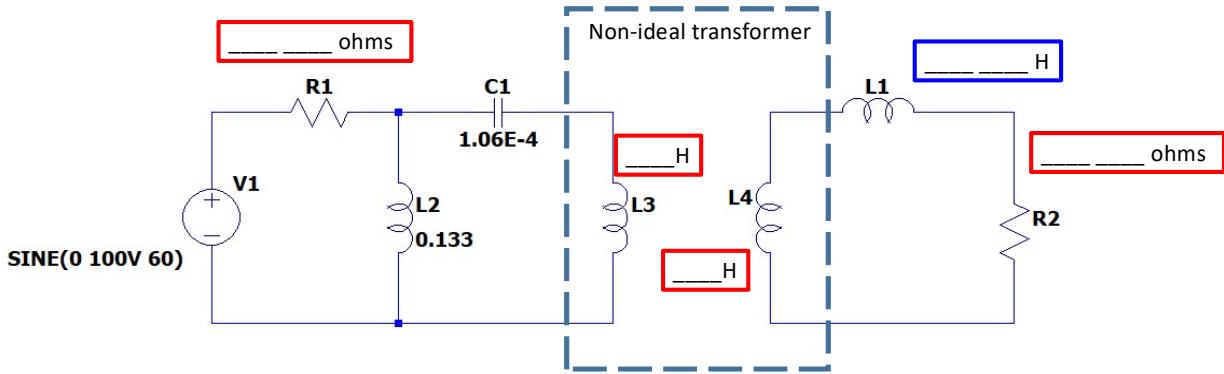2.2: (35 pts) The ideal transformer if 2.1 is now non-ideal. The values of R1 and R2 in 2.1 should be used again. The coupling coefficient is 0.45. Choose values of the transformer self-inductances L3 and L4 between 1 and 5 H. Design your circuit such that your answer for the voltage across R2 in 2.1 matches with this non-ideal transformer. (The easiest way is to adjust the value of L1 at the end if needed which may mean adding resistance or making it a capacitor. If your answer is ridiculous but procedure is right...no problem..you will still get full points!)



$$\omega := 2 \cdot \pi \cdot f$$

$$\omega = 376.991 \frac{1}{\text{s}}$$

$$R_{1v} := 33\Omega$$

$$R_{2v} := 55\Omega$$

$$V_{1v} := 100V$$

$$C_{1v} := 1.06 \cdot 10^{-4} \text{F}$$

$$L_{2v} := 0.133\text{H}$$

$$L_2 \cdot \omega = 50.14 \Omega$$

$$Z_{L2v} := 50j\Omega$$

$$\frac{-1}{C_1 \cdot \omega} = -25.024 \Omega$$

$$Z_{R1} := R_1 = 33 \Omega$$

$$L_{3v} := 2\text{H}$$

$$L_4 := 5\text{H}$$

$$Z_{C1v} := -25j\Omega$$

$$Z_{R2v} := R_2 = 55 \Omega$$

$$k := 0.45$$

$$M := k \cdot \sqrt{L_3 \cdot L_4}$$

$$k = \frac{M}{\sqrt{L_3 \cdot L_4}}$$

$$M = 1.423 \text{H}$$


$$L_3 - M = 0.577 \text{H}$$

$$Z_{L3M} := (L_3 - M)j \cdot \omega = 217.514i\Omega$$

$$L_4 - M = 3.577 \text{H}$$

$$Z_{L4M} := (L_4 - M) \cdot j \cdot \omega = 1.348i \times 10^3 \Omega$$
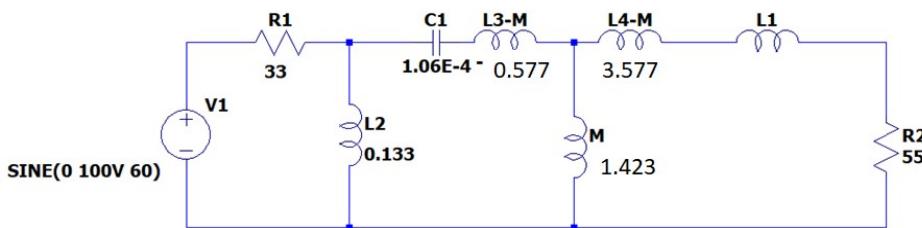
$$Z_M := M \cdot j \cdot \omega = 536.468i\Omega$$



To find VR2...can use circuit reduction and then voltage divider...make equal to find L1

$$L_{\text{L1}} := 0.398 \text{ H}$$

$$L_1 \cdot \omega = 150.042 \Omega$$

using thevenin again before L1...then will make it equal

$$Z_{L1} := 150j\Omega$$

$$Z_M + Z_{L3M} + Z_{C1} = 728.982i\Omega$$

$$Z_{L2C1L3MM} := \frac{(Z_M + Z_{L3M} + Z_{C1}) \cdot Z_{L2}}{Z_{L2} + Z_M + Z_{L3M} + Z_{C1}} = 46.791i\Omega$$

$$V_{ZL2C1L3MM} := V_1 \cdot \frac{Z_{L2C1L3MM}}{Z_{R1} + Z_{L2C1L3MM}} = (66.782 + 47.099i) \text{ V}$$

$$V_M := V_{ZL2C1L3MM} \cdot \frac{Z_M}{Z_M + Z_{L3M} + Z_{C1}} = (49.146 + 34.661i) \text{ V}$$

$$V_{Th2} := V_M \quad \sqrt{42.206^2 + 13.53^2} = 44.322$$

$$Z_{TH} := \frac{\left(\frac{Z_{R1} \cdot Z_{L2}}{Z_{R1} + Z_{L2}} + Z_{C1} + Z_{L3M} \right) \cdot Z_M}{\left(\frac{Z_{R1} \cdot Z_{L2}}{Z_{R1} + Z_{L2}} + Z_{C1} + Z_{L3M} \right) + Z_M} + Z_{L4M} = (11.935 + 1.499i \times 10^3) \Omega$$

$$V_{R2} = (48.042 + 17.676i) \text{ V}$$

$$V_{R2} = V_{Th2} \cdot \frac{Z_{R2}}{Z_{R2} + Z_{L1} + Z_{TH}}$$

$$V_{L1\text{nonideal}} := \frac{V_{Th2} \cdot Z_{R2}}{V_{R2}} - Z_{TH} - Z_{R2} = (-4.52 - 1.482i \times 10^3) \Omega$$

Added resistor

$$R_{ZL1} := -4.52 \Omega$$

$$C_{ZL1} := \frac{-j\Omega}{-1.482 \cdot 10^3 \Omega j \cdot \omega \cdot 1} = 1.79 \times 10^{-6} \text{ s}$$

This is my check of your answers to see if it matches your VR2

$$V_{R2} = (48.042 + 17.676i) V$$

$$Z_{LZL1} := \frac{-j\Omega}{C_{ZL1} \cdot \omega} = -1.482i \times 10^3 \Omega$$

$$Z_{ZL1} := R_{ZL1} + Z_{R2} = 50.48 \Omega \quad \text{These resistances add together...}$$

a couple voltage dividers are done...

$$Z_{L4ML1R2} := Z_{ZL1} + Z_{LZL1} + Z_{L4M} = (50.48 - 133.512i) \Omega$$

$$Z_{ML4ML1R2} := \frac{Z_{L4ML1R2} \cdot Z_M}{Z_{L4ML1R2} + Z_M} = (88.091 - 166.714i) \Omega$$

$$Z_{C1L3MML4ML1R2} := Z_{ML4ML1R2} + Z_{C1} + Z_{L3M} = (88.091 + 25.801i) \Omega$$

$$Z_{L2C1L3MML4ML1R2} := \frac{Z_{C1L3MML4ML1R2} \cdot Z_{L2}}{Z_{C1L3MML4ML1R2} + Z_{L2}} = (16.306 + 35.969i) \Omega$$

$$V_A := V_1 \cdot \frac{Z_{L2C1L3MML4ML1R2}}{Z_{L2C1L3MML4ML1R2} + Z_{R1}} = (56.318 + 31.866i) V$$

$$V_B := \frac{V_A \cdot Z_{ML4ML1R2}}{Z_{ML4ML1R2} + Z_{C1} + Z_{L3M}} = (87.256 - 100.273i) V$$

$$V_{R2check} := \frac{V_B \cdot Z_{R2}}{Z_{L4ML1R2}} = (48.031 + 17.785i) V$$

if VR2check doesn't match VR2 something is wrong...

$$V_{R2} = (48.042 + 17.676i) V$$