

ELECTRIC CIRCUITS

ECSE-2010

Lecture 3.1



LECTURE 3.1 AGENDA

- Introduction to solving tools
- Node voltage analysis basics
- Node voltage analysis examples
- Cramer's Rule

sawyer@rpi.edu

www.rpi.edu/~sawyer



MORE SOLVING TOOLS

- Node Voltage Analysis
 - Systematic method for **solving for all unknown voltages** (and hence all unknown currents) in any circuit
- Mesh Current Analysis
 - Systematic method for **solving for all unknown currents** (and hence all unknown voltages) in any circuit

sawyer@rpi.edu

www.rpi.edu/~sawyer



NODE VOLTAGE ANALYSIS

- A systematic technique for **solving ANY linear circuit**:
 - Will Always Work!
 - Not always the easiest technique
- Will also learn mesh current analysis:
 - Can use either technique; But cannot mix
- These are very powerful techniques!!
 - Will use for rest of course

sawyer@rpi.edu

www.rpi.edu/~sawyer



NODE VOLTAGE ANALYSIS

Procedure:


1. Label all node voltages, known and unknown, identifying variables (v_1 , v_2 , etc.)
 - a. # of Unknown Node Voltages = # of Nodes - # of Voltage Sources - 1 (Reference)
 - b. Example: 4 Nodes - 1 Voltage Source - 1 = 2 Unknown Node Voltages; v_1 , v_2
2. Write a KCL at each unknown node voltage
 - a. Best to use: Sum of currents out of node = 0
 - b. Makes equations "cleaner"
 - c. Express i's in terms of node voltages

sawyer@rpi.edu

www.rpi.edu/~sawyer



EXAMPLE

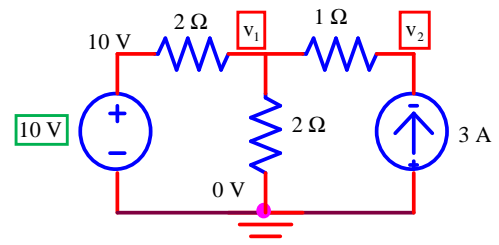


Step 1: Label All Node Voltages
Known and Unknown
2 Unknown Node Voltages, v_1 , v_2

sawyer@rpi.edu

www.rpi.edu/~sawyer



EXAMPLE

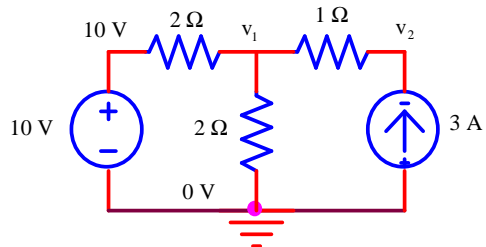


If Find v_1, v_2 , All Voltages and Currents
Can Be Determined

sawyer@rpi.edu

www.rpi.edu/~sawyer



EXAMPLE

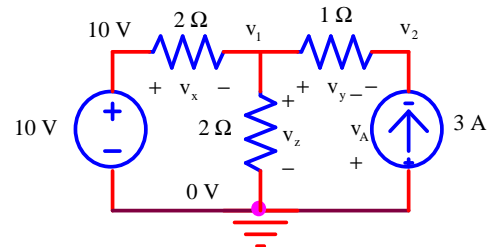

$$v_x = 10 - v_1$$

$$v_z = v_1 - 0 = v_1$$

$$v_y = v_1 - v_2$$


$$v_A = 0 - v_2 = -v_2$$

sawyer@rpi.edu

www.rpi.edu/~sawyer



EXAMPLE

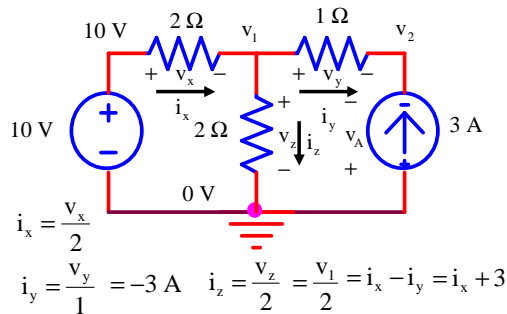

$$i_x = \frac{v_x}{2}$$


$$i_y = \frac{v_y}{1} = -3 \text{ A} \quad i_z = \frac{v_z}{2} = \frac{v_1}{2} = i_x - i_y = i_x + 3$$

sawyer@rpi.edu

www.rpi.edu/~sawyer



EXAMPLE

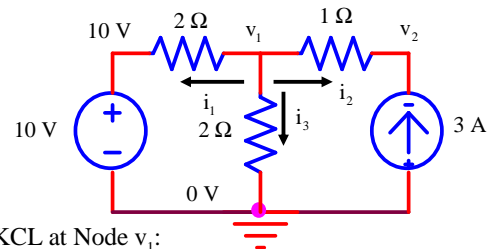

KCL at Node v_1 :


$$i_1 + i_2 + i_3 = 0 \quad \frac{v_1 - 10}{2} + \frac{v_1 - v_2}{1} + \frac{v_1 - 0}{2} = 0$$

sawyer@rpi.edu

www.rpi.edu/~sawyer



EXAMPLE

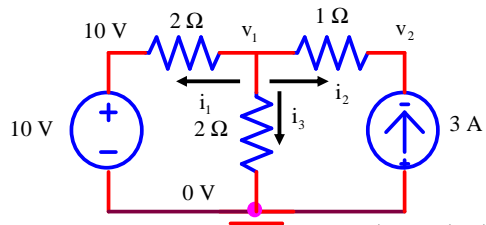

$$\frac{v_1 - 10}{2} + \frac{v_1 - v_2}{1} + \frac{v_1}{2} = 0 \quad v_1 \left(\frac{1}{2} + \frac{1}{1} + \frac{1}{2} \right) + v_2 \left(-\frac{1}{1} \right) = 5$$

1 Equation, 2 Unknowns


$$2v_1 - v_2 = 5$$

sawyer@rpi.edu

www.rpi.edu/~sawyer



EXAMPLE

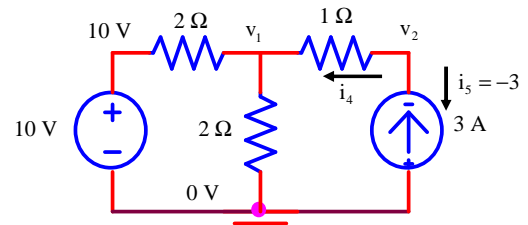

KCL at Node v_2 :

$$i_4 + i_5 = 0 \quad \frac{v_2 - v_1}{1} - 3 = 0 \quad v_1 \left(-\frac{1}{1} \right) + v_2 \left(\frac{1}{1} \right) = 3$$

$$i_4 + (-3) = 0$$

$$-v_1 + v_2 = 3$$

sawyer@rpi.edu

www.rpi.edu/~sawyer



NODE VOLTAGE ANALYSIS

■ Example:

$$\text{KCL at } v_1: \frac{(v_1 - 10)}{2} + \frac{(v_1 - 0)}{2} + \frac{(v_1 - v_2)}{1} = 0$$

$$\Rightarrow 2v_1 - v_2 = 5$$

$$\text{KCL at } v_2: \frac{(v_2 - v_1)}{1} + (-3) = 0$$

$$\Rightarrow (-v_1 + v_2) = 3$$

sawyer@rpi.edu

www.rpi.edu/~sawyer



NODE VOLTAGE ANALYSIS

■ Example:

$$\text{Node } v_1 \Rightarrow 2v_1 - v_2 = 5$$

$$\text{Node } v_2 \Rightarrow -v_1 + v_2 = 3$$

$$\text{Add: } \Rightarrow v_1 = 8 \text{ V}$$

$$\Rightarrow v_2 = 11 \text{ V}$$

Can now Find All Voltages and All Currents

sawyer@rpi.edu

www.rpi.edu/~sawyer



NODE VOLTAGE ANALYSIS

- Writing a KCL at each unknown node voltage will always provide # of linear equations = # Unknowns:

- Can always solve for v_1, v_2, \dots
- Can solve for all currents after solving for all Unknown Node Voltages
- Node Voltage Analysis will ALWAYS work
- If cannot find an easier method \Rightarrow Use Node Voltage Analysis

sawyer@rpi.edu

www.rpi.edu/~sawyer



CRAMER'S RULE

$$\begin{bmatrix} a_1 & b_1 & c_1 \\ a_2 & b_2 & c_2 \\ a_3 & b_3 & c_3 \end{bmatrix} \begin{bmatrix} x \\ y \\ z \end{bmatrix} = \begin{bmatrix} d_1 \\ d_2 \\ d_3 \end{bmatrix}$$

$$\text{Define } \Delta = \begin{vmatrix} a_1 & b_1 & c_1 \\ a_2 & b_2 & c_2 \\ a_3 & b_3 & c_3 \end{vmatrix}$$

sawyer@rpi.edu

www.rpi.edu/~sawyer



CRAMER'S RULE

$$\text{Define } \Delta_1 = \begin{vmatrix} d_1 & b_1 & c_1 \\ d_2 & b_2 & c_2 \\ d_3 & b_3 & c_3 \end{vmatrix};$$

$$\Delta_2 = \begin{vmatrix} a_1 & d_1 & c_1 \\ a_2 & d_2 & c_2 \\ a_3 & d_3 & c_3 \end{vmatrix}; \text{ etc}$$

sawyer@rpi.edu

www.rpi.edu/~sawyer



CRAMER'S RULE

$$x = \frac{\Delta_1}{\Delta}; \quad y = \frac{\Delta_2}{\Delta}; \quad z = \frac{\Delta_3}{\Delta}$$

sawyer@rpi.edu

www.rpi.edu/~sawyer



ELECTRIC CIRCUITS

ECSE-2010

Lecture 3.2



LECTURE 3.2 AGENDA

- Mesh current analysis basics
- Mesh current analysis examples
- Circuit solver

sawyer@rpi.edu

www.rpi.edu/~sawyer



MESH CURRENT ANALYSIS

Procedure:

1. Label and define ALL Mesh Currents
 - a. Unknown Mesh Currents and currents from current sources
 - b. # of Unknown Mesh Currents = # of Meshes - # of Current Sources;
 - c. Example: 2 Meshes - 0 Current Sources = 2 Unknown Mesh Currents; i_1 and i_2
2. Write a KVL around each Unknown Mesh Current
 1. Sum of voltages due to all Mesh Currents = 0
 2. Best to go backwards around current arrow
 3. Express v's in terms of Mesh Currents using Ohm's Law

sawyer@rpi.edu

www.rpi.edu/~sawyer



MESH CURRENT ANALYSIS

What is a mesh and what is a mesh current?


- Mesh = "Window Pane" in Circuit
- Mesh Current = A current defined as flowing all the way around a mesh
 - Some Circuit Elements will have more than 1 Mesh Current flowing in them
 - Mesh Currents must satisfy KCL
- Must define both Unknown Mesh Currents and known currents from current sources
- May choose any direction for Unknown Mesh Current

sawyer@rpi.edu

www.rpi.edu/~sawyer



EXAMPLE

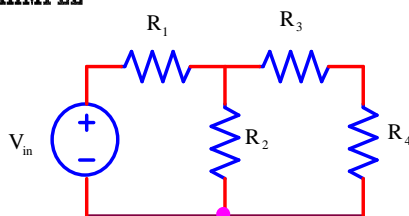

Ladder Circuit:

Could Solve Using Series/Parallel Reduction


Let's Solve Using Mesh Current Analysis

sawyer@rpi.edu

www.rpi.edu/~sawyer



EXAMPLE

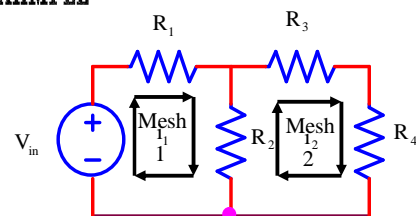

2 "Window Panes" \Rightarrow 2 Meshes

Define Two Mesh Currents, i_1 and i_2


Directions chosen for i_1 and i_2 are arbitrary

sawyer@rpi.edu

www.rpi.edu/~sawyer



EXAMPLE

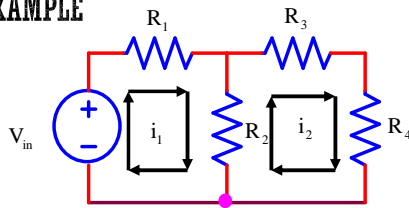


i_1 is the only current in R_1 , V_{in}
 i_2 is the only current in R_3 , R_4
 Both i_1 and i_2 flow in R_2 i_1 flows Down; i_2 flows Up
 Total Current Down $= i_1 - i_2$

sawyer@rpi.edu

www.rpi.edu/~sawyer



EXAMPLE

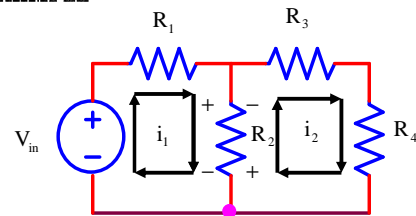

KVL Around Mesh i_1 : $i_1 R_2 - i_2 R_2 + i_1 R_1 - V_{in} = 0$


KVL Around Mesh i_2 : $i_2 R_4 + i_2 R_3 + i_2 R_2 - i_1 R_2 = 0$

sawyer@rpi.edu

www.rpi.edu/~sawyer



EXAMPLE

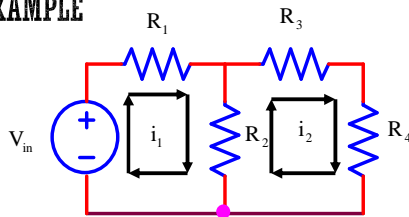

$i_1(R_1 + R_2) + i_2(-R_2) = v_{in}$ 2 Equations, 2 Unknowns
 $i_1(-R_2) + i_2(R_1 + R_2 + R_3) = 0$ Can Solve for i_1 and i_2 :

sawyer@rpi.edu

www.rpi.edu/~sawyer



EXAMPLE

In Matrix Form:

$$\begin{bmatrix} R_1 + R_2 & -R_2 \\ -R_2 & R_2 + R_3 + R_4 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} v_{in} \\ 0 \end{bmatrix}$$

$$[R] [I] = [V_s]$$

ohms amps = volts

sawyer@rpi.edu

www.rpi.edu/~sawyer



EXAMPLE

In Matrix Form:

$$\begin{bmatrix} \sum R_1 + R_2 & -R_2 \\ -R_2 & R_2 + R_3 + R_4 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} v_{in} \\ 0 \end{bmatrix}$$

Annotations:
 - $\sum R_1 + R_2$: Sum of R's Around Mesh 1
 - $-R_2$: Common to Mesh 1 and Mesh 2
 - $R_2 + R_3 + R_4$: Sum of R's Around Mesh 2

sawyer@rpi.edu

www.rpi.edu/~sawyer



EXAMPLE

In Matrix Form:

$$\begin{bmatrix} R_{11} & -R_{12} \\ -R_{21} & R_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} v_{in} \\ 0 \end{bmatrix}$$

Diagonal Terms are ≥ 0

Off-Diagonal Terms are ≤ 0

Matrix is Symmetric ($R_{12} = R_{21}$, etc.)

Only for $\sum v's = 0$
 Backwards Around Arrow

sawyer@rpi.edu

www.rpi.edu/~sawyer



SUMMARY

- **Node Voltage Analysis:**
 - Label All Node Voltages, Known and Unknown, Identifying Variables (v_1 , v_2 , etc.)
 - # of Unknown Node Voltages = # of Nodes - # of Voltage Sources - 1 (Reference)
 - Write a KCL at Each Unknown Node Voltage
 - Best to Use: Sum of Currents Out of Node = 0
 - Express i's in terms of Node Voltages
 - Solve Algebraic Equations for Node Voltages
 - Use MAPLE, MATLAB, Cramer's Rule, etc.
 - Solve for Currents Using Ohm's Law



NODE ANALYSIS -SOLVING PROCEDURE

1. Identify all nodes
2. Choose a reference node (ground)
3. Label the unknown nodes
4. Locate all voltage sources
 1. Determine either absolute or relative voltages based on the voltage sources
5. Write a KCL equation for each node
6. Use Ohm's Law to rewrite the currents as voltage differences over resistance
 1. If a voltage source is on one of the current paths, 'follow' it to the next node to get an expression for current.
7. Set up the linear system
8. Solve the matrix



SUMMARY

- **Mesh Current Analysis:**
 - Label and Define ALL Mesh Currents
 - Unknown Mesh Currents and Currents from Current Sources
 - # of Unknown Mesh Currents = # of Meshes - # of Current Sources;
 - Write a KVL around Each Unknown Mesh Current
 - Sum of Voltages due to All Mesh Currents = 0
 - Best to Go Backwards Around Current Arrow
 - Solve Algebraic Equations for Mesh Currents (Maple, Cramer's Rule, etc.)
 - Solve for Voltages Using Ohms Law



MESH ANALYSIS -SOLVING PROCEDURE

1. Identify all loops
2. Locate all current sources
3. If possible, simplify the problem by redrawing the circuit with current sources on the 'outside'
4. Label the currents in each loop
5. Assign the current directly if a current source is on the 'outside'
6. Assign a relative current expression if the current source is shared by two loops.
7. Write a KVL expression for each loop
 1. If a current source is shared by two loops, combine them to form a larger loop.
8. Use Ohm's Law to write the KVL in terms of currents
9. Set up the linear system
10. Solve the matrix



CIRCUIT SOLVER

sawyes@rpi.edu www.rpi.edu/~sawyes

CIRCUIT SOLVER

- An Interactive Learning Module (ILM) developed by Academy for Electronic Media
- 1 of many ILM's developed at Rensselaer
- Link to Modules on Course WebCT Homepage
- Or via:
 - <http://www.academy.rpi.edu/projects/ccli>
- Click on Circuit Solver
- "2 Mesh" is same as our Example
- We'll do Activity 4-2 using circuit solver (number on ILM is 4-3)

sawyes@rpi.edu www.rpi.edu/~sawyes

