

ELECTRIC CIRCUITS

ECSE-2010

Lecture 4.1



LECTURE 4.1 AGENDA


- Linearity
- Superposition Principle
- Superposition Example
- Dependent Sources

sawyer@rpi.edu

www.rpi.edu/~sawyer



ACTIVITY 5-1A

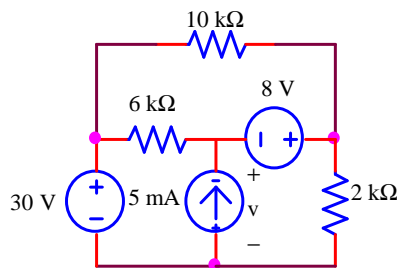

4 Nodes – 2 Voltage Sources – 1 Ref
1 Unknown Node Voltage, v

sawyer@rpi.edu

www.rpi.edu/~sawyer



LINEARITY

- If have multiple inputs
- Input = $x_1 + x_2 + x_3$
- Output must be additive
- $y = k_1x_1 + k_2x_2 + k_3x_3$
- Leads to Superposition Principle
 - Can use only for multiple inputs to a linear circuit

sawyer@rpi.edu

www.rpi.edu/~sawyer



SUPERPOSITION

- Technique to use when there is more than 1 Independent Source in a Linear Circuit:
 - Not always the best technique to use
 - Will learn lots of techniques; Experience helps us learn which technique to choose

sawyer@rpi.edu

www.rpi.edu/~sawyer



SUPERPOSITION

- Find Output due to each independent source with all other independent sources set = 0; then Add to find Total Output:
 - Source of 0 is called a “dead source”
 - “Dead” voltage source = 0 V = Short Circuit
 - “Dead” current source = 0 A = Open Circuit

sawyer@rpi.edu

www.rpi.edu/~sawyer



ELECTRIC CIRCUITS

ECSE-2010

Lecture 4.2



LECTURE 4.2 AGENDA


- Dependent sources overview
- Dependent sources example

sawyes@rpi.edu

www.rpi.edu/~sawyes



ACTIVITY 5-1A

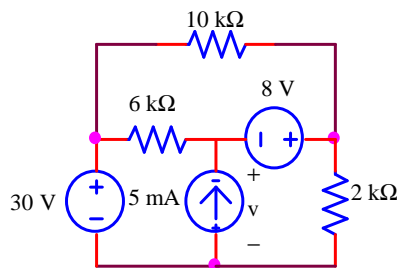

4 Nodes – 2 Voltage Sources – 1 Ref
1 Unknown Node Voltage, v

sawyes@rpi.edu

www.rpi.edu/~sawyes



DEPENDENT SOURCES

- 2 Types of sources for circuit models:
 - Independent Sources
 - Both voltage and current sources
 - Usually model with ideal sources
 - Dependent Sources
 - Also called controlled sources
 - Both voltage and current sources

sawyes@rpi.edu

www.rpi.edu/~sawyes



DEPENDENT SOURCES

- Dependent/Controlled Source:
 - Voltage or current source whose value depends on the v or i at some other point in the circuit
 - Cannot buy a dependent source!
 - Used to model the behavior of electronic devices
 - Almost all interesting or useful circuits contain Dependent Sources

sawyes@rpi.edu

www.rpi.edu/~sawyes



DEPENDENT SOURCES

- Dependent source cannot be the only source of energy in a complete circuit
 - Need an Independent Source to create the controlling current or voltage
- All circuit models for transistors and other electronic devices involve Dependent Sources
 - Whole field of analog electronics is based on dependent sources

sawyes@rpi.edu

www.rpi.edu/~sawyes




EXAMPLE

BJT Transistor

$$i_C = 24i_B$$

$$v_{BE} = 0.6 \text{ V}$$

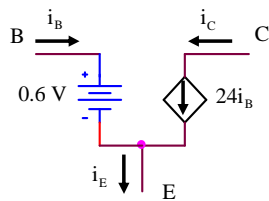

Circuit Model for a BJT



DEPENDENT SOURCES

Symbol:

- Diamond = Symbol for Dependent Source
- Circle = Symbol for Independent Source

4 Types of Dependent Sources

- Voltage Controlled Voltage Source (VCVS), E
- Current Controlled Current Source (CCCS), F
- Voltage Controlled Current Source (VCCS), G
- Current Controlled Voltage Source (CCVS), H


sawyer@rpi.edu

www.rpi.edu/~sawyer



VCVS

Symbol for Dependent Source

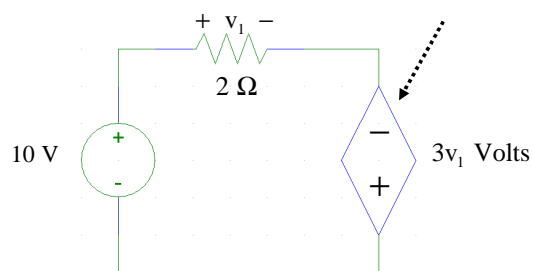

Voltage Controlled Voltage Source (VCVS)


sawyer@rpi.edu

www.rpi.edu/~sawyer



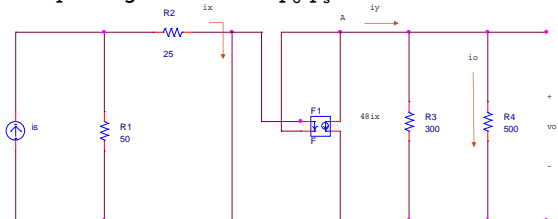EXAMPLE 4-1

- Determine the current, voltage, and power delivered to the 500-ohm output load. Then find the power gain defined as p_o/p_s .



Current Controlled Current Source (CCCS), F


sawyer@rpi.edu

www.rpi.edu/~sawyer



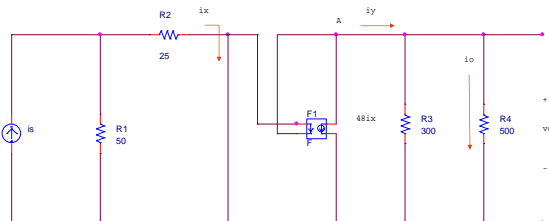EXAMPLE 4-1

Current Controlled Current Source (CCCS), F



sawyer@rpi.edu

www.rpi.edu/~sawyer



SUPERPOSITION


- Total Output = Sum of all Outputs due to each independent source with all other independent sources “dead”:
 - Simply Add them
 - Works only for Linear Circuits; Only kind we will consider

sawyer@rpi.edu

www.rpi.edu/~sawyer



EXAMPLE

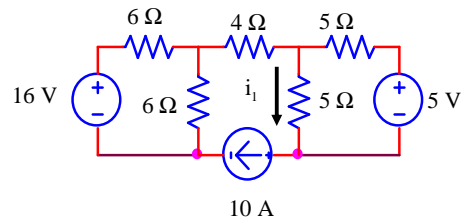

Find i_1 using Superposition


sawyer@rpi.edu

www.rpi.edu/~sawyer



EXAMPLE

Output Due to 16 V Source

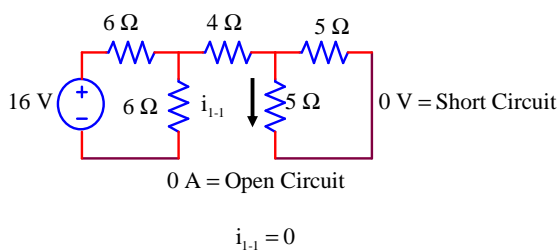


sawyer@rpi.edu

www.rpi.edu/~sawyer



EXAMPLE

Output Due to 10 A Source

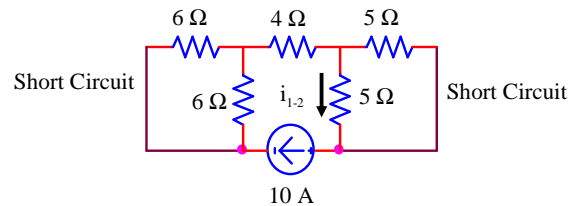


sawyer@rpi.edu

www.rpi.edu/~sawyer



EXAMPLE

Output Due to 10 A Source

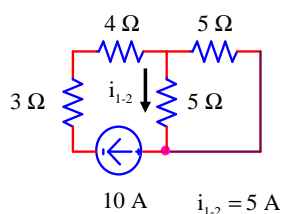


sawyer@rpi.edu

www.rpi.edu/~sawyer



EXAMPLE

Output Due to 5 V Source

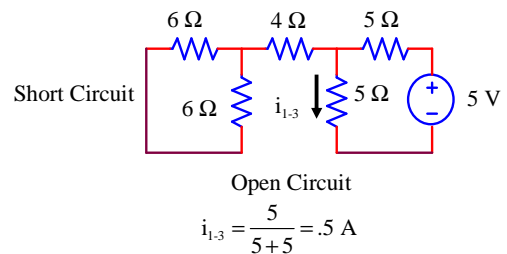


sawyer@rpi.edu

www.rpi.edu/~sawyer



EXAMPLE

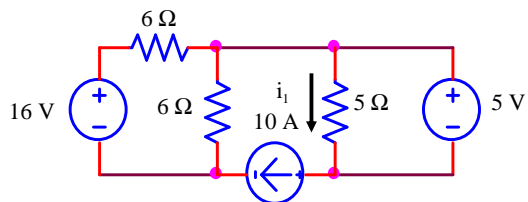


$$i_1 = 0 + 5 + .5 = 5.5 \text{ A}$$

sawyer@rpi.edu

www.rpi.edu/~sawyer



ACTIVITY 5-2

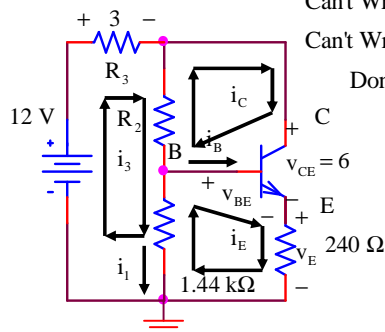

Can't Write KVL around i_3

Can't Write KVL around i_C


Don't know R_2

sawyer@rpi.edu

www.rpi.edu/~sawyer



ACTIVITY 5-2

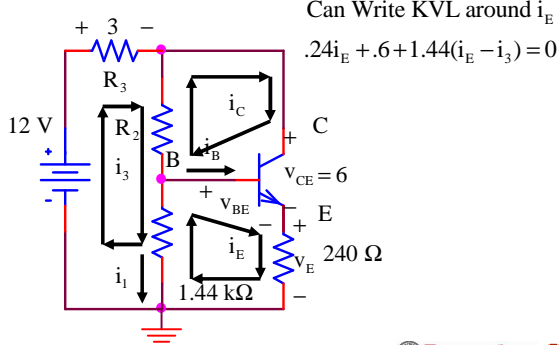

Can Write KVL around i_E


$$.24i_E + .6 + 1.44(i_E - i_3) = 0$$

sawyer@rpi.edu

www.rpi.edu/~sawyer



ACTIVITY 5-2

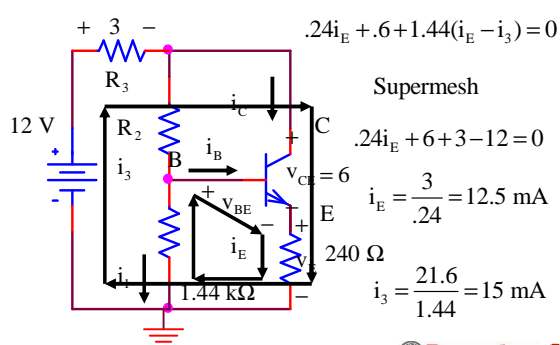

$$.24i_E + .6 + 1.44(i_E - i_3) = 0$$

Supermesh

$$.24i_E + 6 + 3 - 12 = 0$$

$$i_E = \frac{3}{.24} = 12.5 \text{ mA}$$


$$i_3 = \frac{21.6}{1.44} = 15 \text{ mA}$$

sawyer@rpi.edu

www.rpi.edu/~sawyer



ACTIVITY 5-2

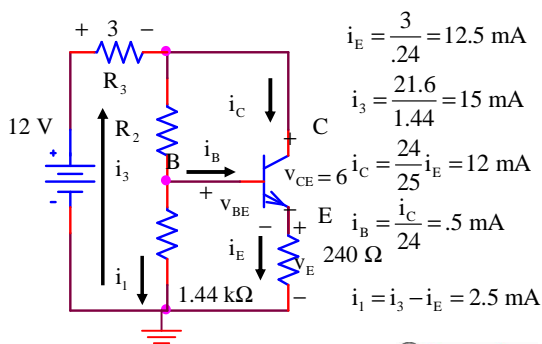

$$i_E = \frac{3}{.24} = 12.5 \text{ mA}$$

$$i_3 = \frac{21.6}{1.44} = 15 \text{ mA}$$

$$i_C = \frac{24}{25} i_E = 12 \text{ mA}$$

$$i_B = \frac{i_C}{24} = .5 \text{ mA}$$


$$i_1 = i_3 - i_E = 2.5 \text{ mA}$$

sawyer@rpi.edu

www.rpi.edu/~sawyer



ACTIVITY 5-2

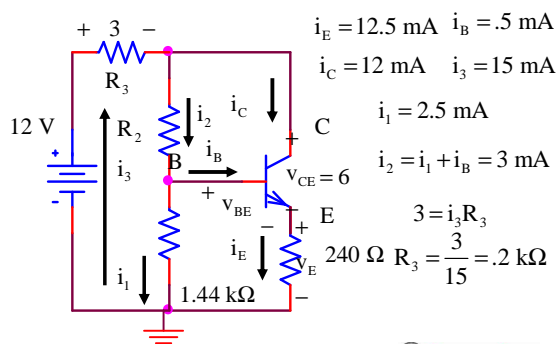

$$i_E = 12.5 \text{ mA} \quad i_B = .5 \text{ mA}$$

$$i_C = 12 \text{ mA} \quad i_3 = 15 \text{ mA}$$

$$i_1 = 2.5 \text{ mA}$$

$$i_2 = i_1 + i_B = 3 \text{ mA}$$

$$3 = i_3 R_3$$


$$R_3 = \frac{3}{15} = .2 \text{ k}\Omega$$

sawyer@rpi.edu

www.rpi.edu/~sawyer



ACTIVITY 5-2

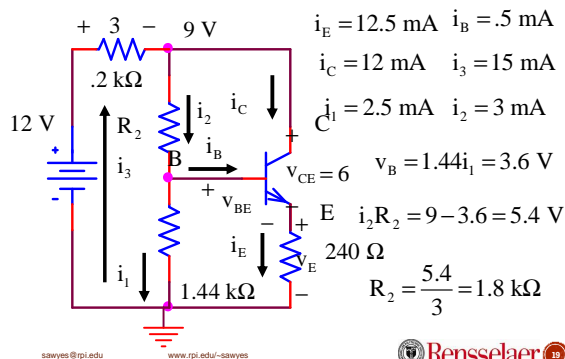

ACTIVITY 5-2

