

ELECTRIC CIRCUITS ECSE-2010

Lecture 6.1

 Rensselaer


LECTURE 6.1 AGENDA

- Amplifier circuit model
- Ideal Operational Amplifiers (Op Amps)

sawyes@rpi.edu www.rpi.edu/~sawyes

 Rensselaer 

VOLTAGE AMPLIFIER

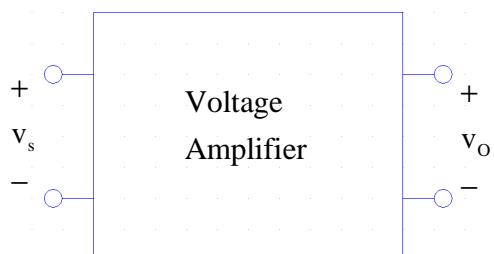

Want $v_o \approx A v_s$; A = Voltage Gain


sawyes@rpi.edu

www.rpi.edu/~sawyes

 Rensselaer 

AMPLIFIER CIRCUIT MODEL

R_i = Input Resistance

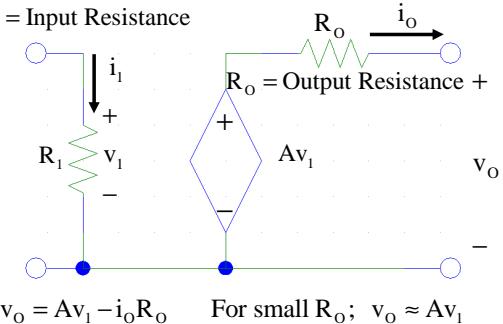

sawyes@rpi.edu

www.rpi.edu/~sawyes

 Rensselaer 

AMPLIFIER CIRCUIT


- Add source network at input:
 - Model with Thevenin Equivalent circuit
 - v_T in series with R_T
- Add load network at output:
 - Model with R_{eq}

sawyes@rpi.edu

www.rpi.edu/~sawyes

 Rensselaer 

AMPLIFIER CIRCUIT

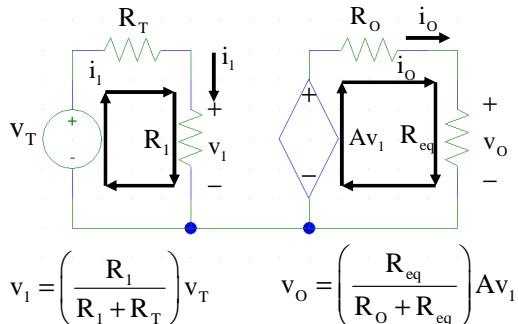

sawyes@rpi.edu

www.rpi.edu/~sawyes

 Rensselaer 

ELECTRIC CIRCUITS


ECSE-2010

Lecture 6.2

 Rensselaer

ZERO CROSSING DETECTOR

No Negative Feedback

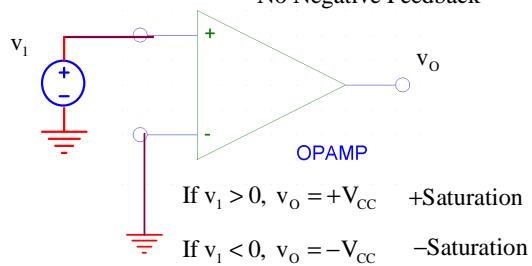

sawyes@rpi.edu

www.rpi.edu/~sawyes

 Rensselaer

LECTURE 6.2 AGENDA


- Op Amps
- Without negative feedback
- With negative feedback (Circuits)
- OP Amp CAD Interactive Learning Module (ILM)

sawyes@rpi.edu www.rpi.edu/~sawyes

 Rensselaer

COMPARATOR

No Negative Feedback

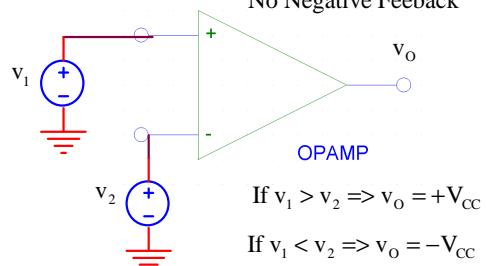

sawyes@rpi.edu www.rpi.edu/~sawyes

 Rensselaer

OP AMP CIRCUITS


- For most Op Amp circuits, we add negative feedback:
 - Circuit connection between v_o and v_N
 - Helps to keep Op Amp in Linear Range
 - This will help keep $v_p = v_N$
 - Output, $v_o = A(v_p - v_N)$, will be finite, as long as its magnitude is less than V_{cc}
 - Output can never be greater than $\pm V_{cc}$

sawyes@rpi.edu

www.rpi.edu/~sawyes

 Rensselaer

VOLTAGE FOLLOWER

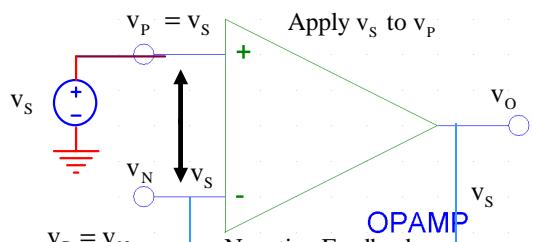


Draws No Current from Source
Buffer, or Isolation Amplifier


sawyes@rpi.edu www.rpi.edu/~sawyes

 Rensselaer


INVERTING AMPLIFIER

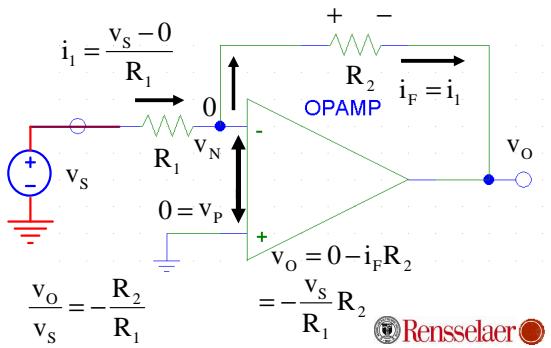


NON-INVERTING AMPLIFIER

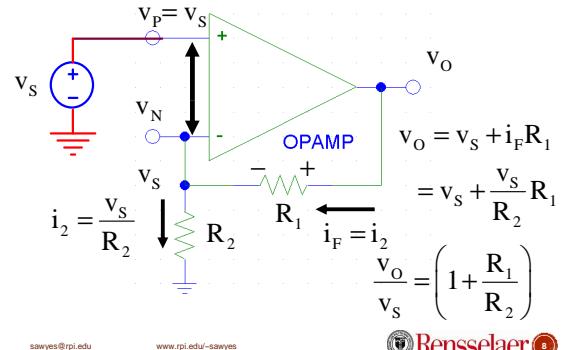


NON-INVERTING AMPLIFIER

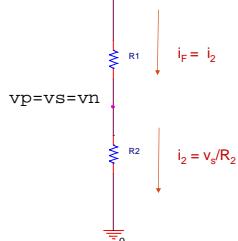


SUMMER

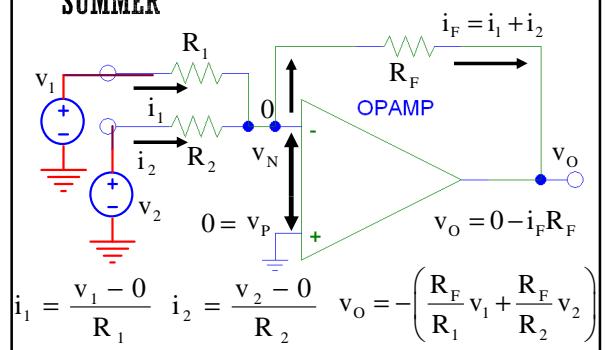

SUMMING AMPLIFIER

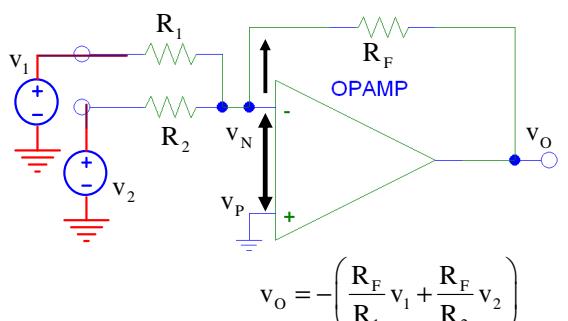

DIFFERENTIAL AMP

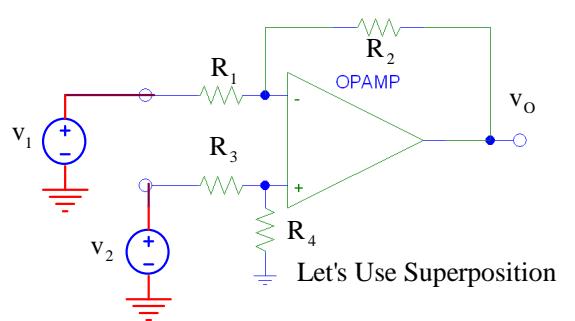

OP AMP CAD ILM

- Go to WebCT Site, Click on Modules
- Click on Op Amp CAD Module
- Move top slider to choose type of circuit
- Inverting, Non-Inverting Amplifier
- Differential Amplifier, Comparator
- Integrator, Differentiator (Later in Course)

http://www.academy.rpi.edu/projects/ccli/module_display.php?ModuleID=11

sawyes@rpi.edu

www.rpi.edu/~sawyes



13

OP AMP CAD ILM

- Move slider to Inverting Amplifier
- Change R_F from 1k to 4k
- => Observe Clipping
- Change R_F from 4k to 10k
- => Observe \approx Square Wave
- Change f from 1 kHz to 5 kHz

sawyes@rpi.edu

www.rpi.edu/~sawyes



14

OP AMP CAD MODULE

- Move slider to Non-Inverting Amplifier
- Change V_{DC} to +5, -5 V
- => Observe Clipping
- Change f from 1 kHz to 5 kHz
- Same effect as changing Gain

sawyes@rpi.edu

www.rpi.edu/~sawyes



15

OP AMP CAD MODULE

- Move slider to Differential Amplifier
- Change R_F , R_1 , R_2 , f
- Observe what happens
- Will Discuss Differential Amplifiers
More Next Class


sawyes@rpi.edu

www.rpi.edu/~sawyes



16

AMPLIFIER CIRCUIT

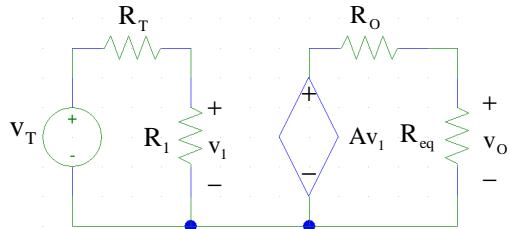

$$v_1 = \left(\frac{R_1}{R_1 + R_T} \right) v_T \quad \text{If: } R_1 \gg R_T \quad v_1 \approx v_T$$


Want Input Resistance \square Large



sawyes@rpi.edu

www.rpi.edu/~sawyes

AMPLIFIER CIRCUIT

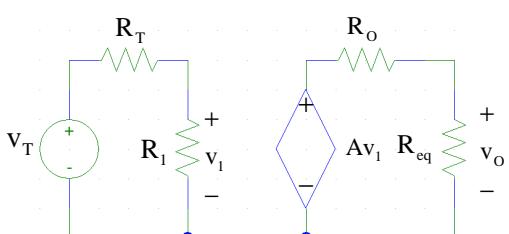

$$v_o = \left(\frac{R_{eq}}{R_o + R_{eq}} \right) Av_1 \quad \text{If: } R_{eq} \gg R_o \quad v_o \approx Av_1$$


Want Output Resistance Small



sawyes@rpi.edu

www.rpi.edu/~sawyes

AMPLIFIER CIRCUIT

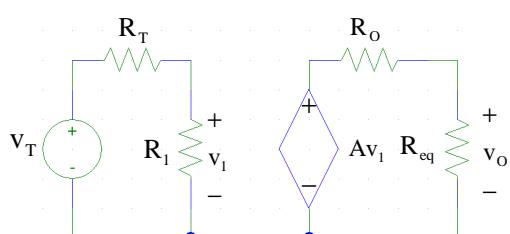

$$\text{If: } R_1 \gg R_T \Rightarrow \frac{v_o}{v_T} = \text{Voltage Gain } \approx A$$

$$R_{eq} \gg R_o \quad \text{Design Challenge}$$



sawyes@rpi.edu

www.rpi.edu/~sawyes

OPERATIONAL AMPLIFIERS

- An Operational Amplifier is a **High Gain Voltage Amplifier that can be used to perform Mathematical Operations:**

- Addition and Subtraction
- Differentiation and Integration
- Other Functions as Well

- Op Amps are the building blocks for many, many electronic circuits



sawyes@rpi.edu

www.rpi.edu/~sawyes

OPERATIONAL AMPLIFIERS


- Op Amps have existed since 1947:
 - First made with vacuum tubes
 - Then with discrete transistors
 - Now with Integrated Circuits
- Op Amps are complex arrays of transistors, diodes, resistors and capacitors – All on a chip:
 - But can be modeled quite simply







sawyes@rpi.edu

www.rpi.edu/~sawyes




TYPICAL 741 OP AMP CIRCUIT

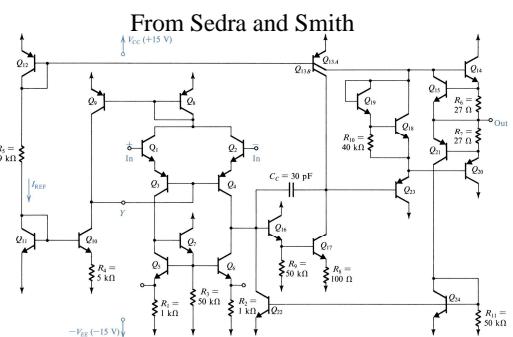

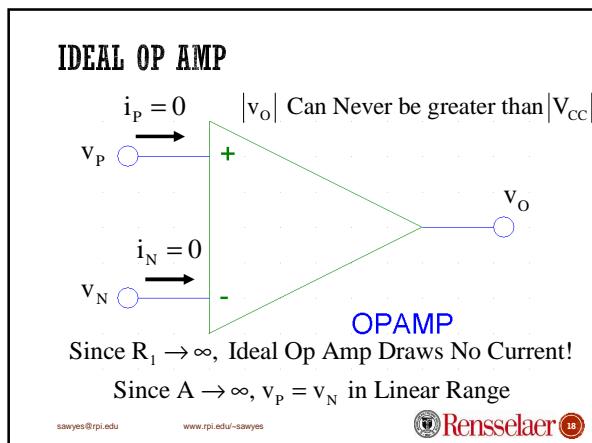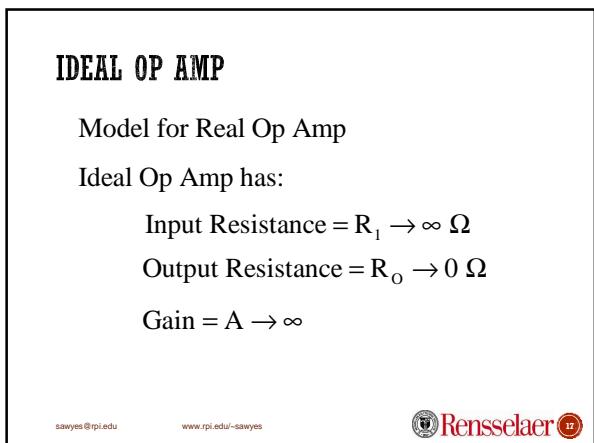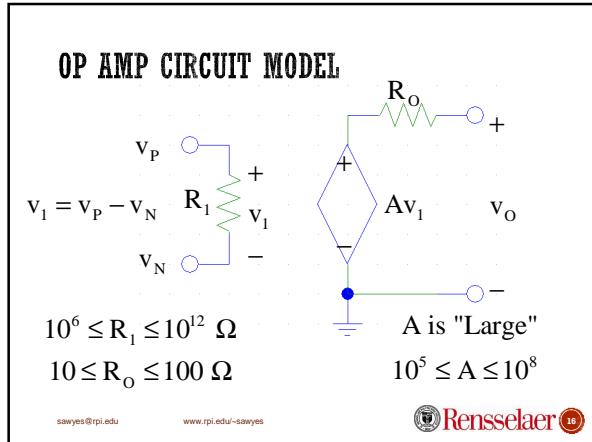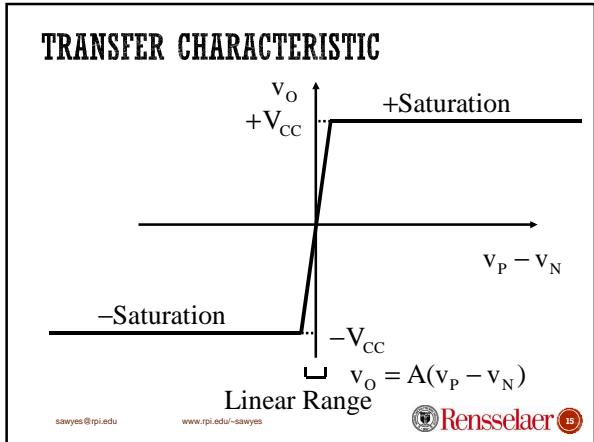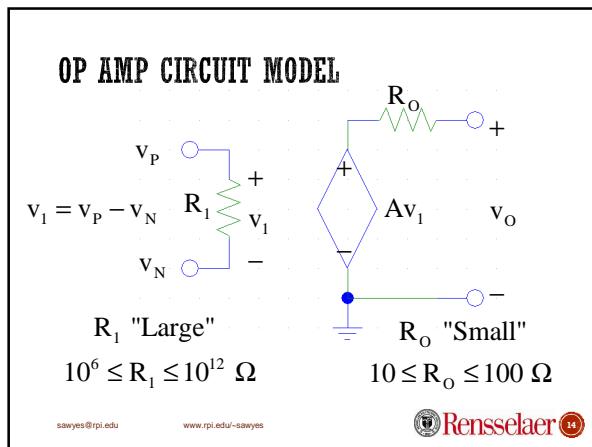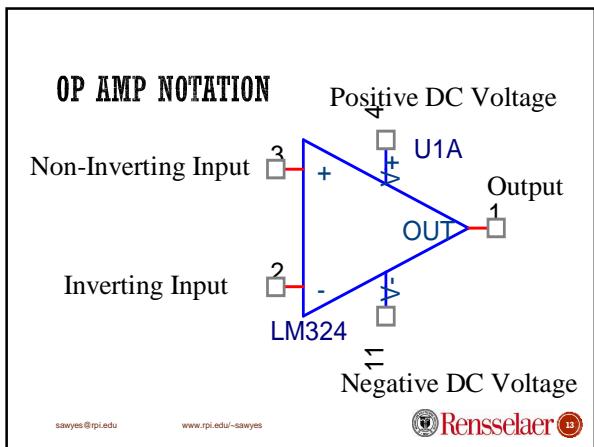

IDEAL OP AMP

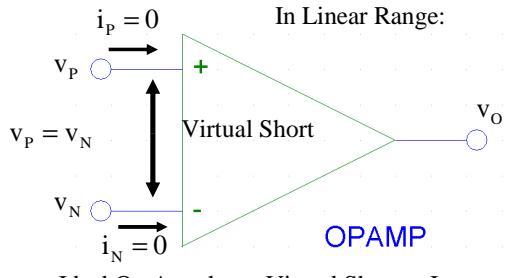

Ideal Op Amp has a Virtual Short at Input

$$v_p = v_n; i_p = i_n = 0$$

sawyes@rpi.edu

Rensselaer 19