

ELECTRIC CIRCUITS ECSE-2010

Lecture 14.1



CIRCUITS WITH LAPLACE

- Will Do in 2 Steps:
- Method 1
 - First find differential equation
 - Transform to an algebraic equation
 - Take inverse laplace to find $y(t)$
- Method 2
 - Define s-domain circuits
 - No more differential equations!




LECTURE 14.1 AGENDA

- Example Problems
- Initial and final values
- Circuit elements in the S-domain

sawyes@rpi.edu www.rpi.edu/~sawyes



ACTIVITY 20-1

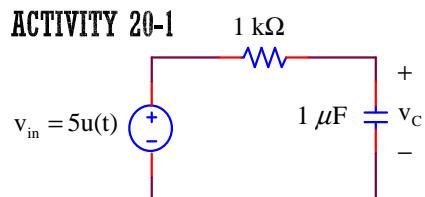

First Order Circuit

$$v_{C0} = 0 \text{ V} \quad v_{CSS} = 5 \text{ V}$$


Switched DC Input

$$v_C(t) = v_{CSS} + (v_{C0} - v_{CSS})e^{-(t-t_0)/\tau}$$

$$\tau = RC = 1 \text{ msec} \quad v_C(t) = 5(1 - e^{-t/\tau}) \quad t \geq 0$$




ACTIVITY 20-1

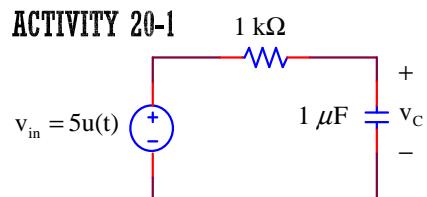

Find Differential Equation
Relating $v_C(t)$ to v_{in}



ACTIVITY 20-1

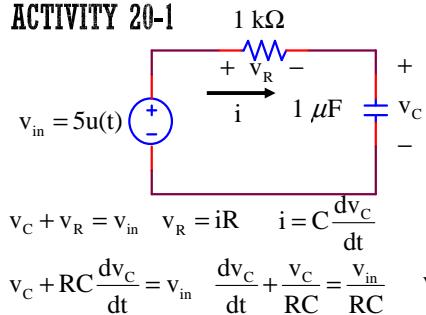

Rensselaer

ACTIVITY 20-1

$$\frac{dv_C}{dt} + \frac{v_C}{RC} = \frac{v_{in}}{RC} \quad v_{in} = 5u(t)$$

$$L \left\{ \frac{dv_C}{dt} + \frac{v_C}{RC} \right\} = L \left\{ \frac{5u(t)}{RC} \right\}$$

$$(sV_C(s) - v_C(0^-)) + \frac{V_C(s)}{RC} = \frac{5}{RC} \frac{1}{s}$$

$$(sV_C(s) - v_{C0}) + \frac{V_C(s)}{RC} = \frac{5}{sRC}$$

Algebraic Equation

Rensselaer

ACTIVITY 20-1

$$(sV_C(s) - v_{C0}) + \frac{V_C(s)}{RC} = \frac{5}{sRC}$$

$$V_C(s) \left(s + \frac{1}{RC} \right) = \frac{5}{sRC} + v_{C0}$$

$$V_C(s) = \frac{5/RC}{s(s+1/RC)} + \frac{v_{C0}}{(s+1/RC)}$$

Rensselaer

ACTIVITY 20-1

$$V_C(s) = \frac{5/RC}{s(s+1/RC)} + \frac{v_{C0}}{(s+1/RC)}$$

$$\frac{5/RC}{s(s+1/RC)} = \frac{A_1}{s} + \frac{A_2}{(s+1/RC)}$$

$$A_1 = \left. \frac{5/RC}{(s+1/RC)} \right|_{s=0} = 5$$

$$A_2 = \left. \frac{5/RC}{s} \right|_{s=-\frac{1}{RC}} = -5$$

Rensselaer

ACTIVITY 20-1

$$V_C(s) = \frac{5}{s} + \frac{-5}{s+1/RC} + \frac{v_{C0}}{(s+1/RC)}$$

$$v_C(t) = 5 - 5e^{-t/RC} + v_{C0}e^{-t/RC}$$


$$v_C(t) = 5 + (v_{C0} - 5)e^{-t/RC}$$

$$v_{C0} = 0; \quad RC = \tau$$

$$v_C(t) = 5(1 - e^{-t/\tau}) \text{ volts} \quad t \geq 0$$

Same as Before Rensselaer

ACTIVITY 20-2

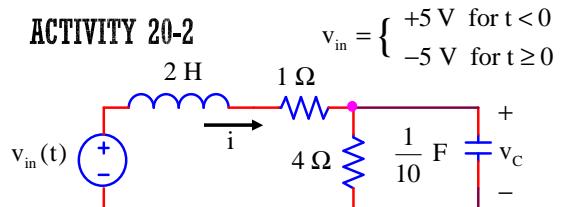


Find $I(s), V_C(s)$

You do have to find $v_C(t)$

(e.g. if you like, use Maple or other methods)

Rensselaer

ACTIVITY 20-2

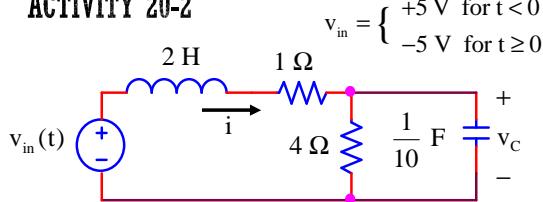

First: Find $i_L(0^-)$, $v_c(0^-)$ Initial Conditions


Second: Find Differential Equation for v_c

Third: Solve for $V_c(s)$, $I(s)$



ACTIVITY 20-2

$t = 0^-$

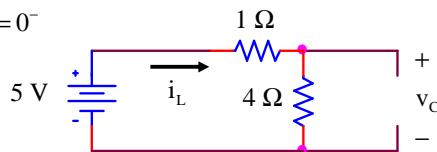

$$i_L(0^-) = 1 \text{ A}$$


$$i_c(0^-) = 0 = \frac{1}{10} \frac{dv_c}{dt}(0^-)$$

$$v_c(0^-) = 4 \text{ V}$$

$$\Rightarrow \frac{dv_c}{dt}(0^-) = 0$$



ACTIVITY 20-2

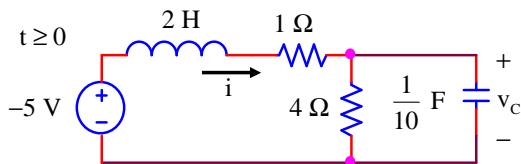

$$\text{KVL: } v_c + 1(i) + 2 \frac{di}{dt} = -5 \quad \text{KCL: } i = \frac{v_c}{4} + \frac{1}{10} \frac{dv_c}{dt}$$

$$v_c + \left(\frac{v_c}{4} + \frac{1}{10} \frac{dv_c}{dt} \right) + 2 \left(\frac{1}{4} \frac{dv_c}{dt} + \frac{1}{10} \frac{d^2v_c}{dt^2} \right) = -5$$



ACTIVITY 20-2

$$v_c + \left(\frac{v_c}{4} + \frac{1}{10} \frac{dv_c}{dt} \right) + 2 \left(\frac{1}{4} \frac{dv_c}{dt} + \frac{1}{10} \frac{d^2v_c}{dt^2} \right) = -5$$

$$\frac{1}{5} \frac{d^2v_c}{dt^2} + \frac{6}{10} \frac{dv_c}{dt} + \frac{5}{4} v_c = -5$$

$$\frac{d^2v_c}{dt^2} + 3 \frac{dv_c}{dt} + \frac{25}{4} v_c = -25$$

$$4 \frac{d^2v_c}{dt^2} + 12 \frac{dv_c}{dt} + 25v_c = -100$$



ACTIVITY 20-2

$$4 \frac{d^2v_c}{dt^2} + 12 \frac{dv_c}{dt} + 25v_c = -100$$

$$L \left(\frac{d^2v_c}{dt^2} \right) = s^2 V_c(s) - sv_c(0^-) - \frac{dv_c}{dt}(0^-)$$

↓

4s

↓

0

$$4(s^2 V_c(s) - 4s) + 12(s V_c(s) - 4) + 25V_c(s) = -\frac{100}{s}$$



ACTIVITY 20-2

$$4(s^2 V_c(s) - 4s) + 12(s V_c(s) - 4) + 25V_c(s) = -\frac{100}{s}$$

$$V_c(s)(4s^2 + 12s + 25) = -\frac{100}{s} + 16s + 48$$

$$V_c(s)(4s^2 + 12s + 25) = \frac{-100 + 16s^2 + 48s}{s}$$

$$V_c(s) = \frac{16s^2 + 48s - 100}{s(4s^2 + 12s + 25)}$$



ACTIVITY 20-2

$$V_C(s) = \frac{16s^2 + 48s - 100}{s(4s^2 + 12s + 25)}$$

$$\text{KCL: } i = \frac{v_c}{4} + \frac{1}{10} \frac{dv_c}{dt}$$

$$L(i) = L\left(\frac{v_c}{4} + \frac{1}{10} \frac{dv_c}{dt}\right)$$

$$I(s) = \frac{V_C(s)}{4} + \frac{1}{10}(sV_C(s) - 4)$$



ACTIVITY 20-2

$$I(s) = \frac{V_C(s)}{4} + \frac{1}{10}(sV_C(s) - 4)$$

Lots of Algebra Later...

$$I(s) = \frac{4s^2 - 8s - 25}{4s^3 + 12s^2 + 25s}$$



INITIAL AND FINAL VALUES

- Once we have found $F(s)$, the initial and final values of $f(t)$ can often be found without finding the inverse laplace transform:
 - Initial Value Theorem
 - Final Value Theorem



INITIAL VALUE THEOREM

$$f(t = 0^+) = f_0 = \lim_{s \rightarrow \infty} sF(s)$$

=> Can Find Initial Value Directly from $F(s)$

$F(s)$ must be a Proper Rational Fraction

$$(m < n)$$



INITIAL VALUE THEOREM

Example:

$$F(s) = \frac{2s}{(s^2 + 7s + 12)}$$

$$\Rightarrow f(0^+) = f_0 = \lim_{s \rightarrow \infty} sF(s)$$

$$\Rightarrow f(0^+) = \lim_{s \rightarrow \infty} \frac{2s^2}{(s^2 + 7s + 12)} = 2$$



FINAL VALUE THEOREM

$$f(t \rightarrow \infty) = f_{ss} = \lim_{s \rightarrow 0} sF(s)$$

=> Can Find Final Value Directly from $Y(s)$

Limit Must Exist

=> Cannot Use When:

Multiple Poles at $s = 0$

Poles on Imaginary Axis

Poles in Right Half of s-plane



FINAL VALUE THEOREM

Example:

$$F(s) = \frac{2s}{(s^2 + 7s + 12)}$$

$$\Rightarrow f(t \rightarrow \infty) = f_{ss}$$

$$\Rightarrow f(t \rightarrow \infty) = \lim_{s \rightarrow 0} sF(s) = \lim_{s \rightarrow 0} \frac{2s^2}{(s^2 + 7s + 12)} = 0$$



CIRCUIT ELEMENTS IN S-DOMAIN

- Time Domain:

$$v_R(t) = i_R(t)R; \text{ Algebraic Equation}$$

- s-Domain:


$$L\{v_R(t)\} = L\{i_R(t)R\}$$

$V_R(s) = I_R(s) R \Rightarrow$ Still Algebraic

\Rightarrow Resistor still looks like a Resistor


\Rightarrow Resistor has an "Impedance"

of $R \Omega$ in s-Domain

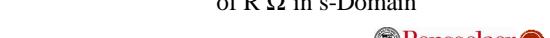

CIRCUIT ELEMENTS IN S-DOMAIN

- Impedance:

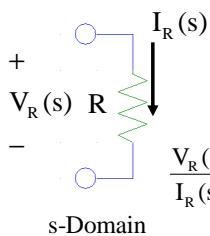

$$V_R(s) = I_R(s) R$$

$\frac{V_R(s)}{I_R(s)}$ has units of Ohms

$$\frac{V_R(s)}{I_R(s)} = Z_R(s) = \text{Impedance of Resistor}$$

$$Z_R(s) = R \Omega$$



CIRCUIT ELEMENTS IN S-DOMAIN

- Time Domain:

$$v_L = L \frac{di_L}{dt}; \text{ Differential Equation}$$

- s-Domain:

$$L(v_L) = L(L \frac{di_L}{dt})$$

$$\Rightarrow V_L(s) = L\{sI_L(s) - i_L(0^-)\}$$

\Rightarrow Algebraic Equation



CIRCUIT ELEMENTS IN S-DOMAIN

$$V_L(s) = sL I_L(s) - Li_L(0^-)$$

In s-Domain:

Inductor looks like an "Impedance"


of value $sL \Omega$ in Series with

a Voltage Source of $-Li_L(0^-)$ Volts



CIRCUIT ELEMENTS IN S-DOMAIN

Model for L in s-Domain

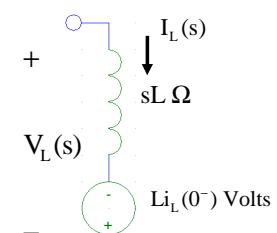


$$V_L(s) = sL I_L(s) - Li_L(0^-)$$



CIRCUIT ELEMENTS IN S-DOMAIN

Time Domain

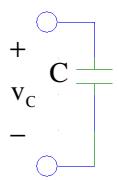

• Time Domain:

$$i_c = C \frac{dv_c}{dt}; \text{ Differential Equation}$$

• s-Domain:

$$L(i_c) = L(C \frac{dv_c}{dt})$$

$$\Rightarrow I_c(s) = C \{sV_c(s) - v_c(0^-)\}$$

$$\Rightarrow V_c(s) = \frac{I_c(s)}{sC} + \frac{v_c(0^-)}{s}$$

⇒ Algebraic Equation



CIRCUIT ELEMENTS IN S-DOMAIN

$$V_c(s) = \frac{I_c(s)}{sC} + \frac{v_c(0^-)}{s}$$

In s-Domain:

Capacitor looks like an "Impedance"


of value $\frac{1}{sC} \Omega$ in Series with

a Voltage Source of $\frac{v_c(0^-)}{s}$ Volts



CIRCUIT ELEMENTS IN S-DOMAIN


Model for C in s-Domain

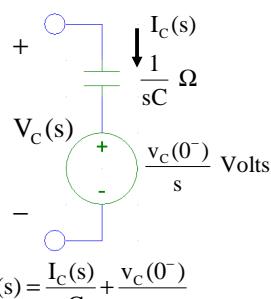

$$V_c(s) = \frac{I_c(s)}{sC} + \frac{v_c(0^-)}{s}$$



CIRCUIT ELEMENTS IN S-DOMAIN

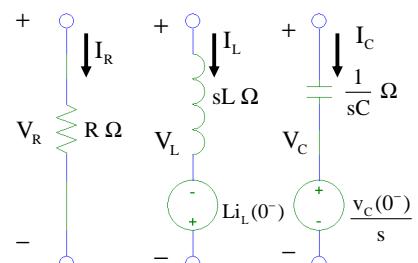

CIRCUIT ELEMENTS IN S-DOMAIN

For No Initial Stored Energy:

$$v_c(0^-) = i_L(0^-) = 0$$


Inductor has "Impedance" $Z_L = sL \Omega$

Capacitor has "Impedance" $Z_C = \frac{1}{sC} \Omega$

Resistor ALWAYS has "Impedance" $Z_R = R \Omega$



WITH NO INITIAL STORED ENERGY

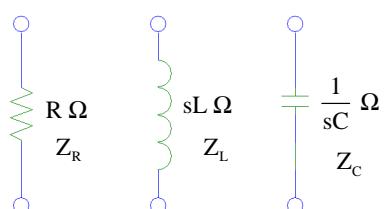

S-DOMAIN CIRCUIT ANALYSIS

- Input = $L\{x(t)\} = X(s)$
- Replace all $i(t), v(t) \rightarrow I(s), V(s)$
- Use s-Domain Models for R, L, C
- Use all techniques developed for Resistive Circuits to find Output in s-Domain = $Y(s)$
- Take Inverse Laplace Transform of $Y(s)$ to find Output $y(t)$
- We'll Practice with Activities 21-1 (today), & 22-1(Thursday)

