

ELECTRIC CIRCUITS ECSE-2010

Lecture 17 Review



REVIEW: LECTURE 9

- First order RC and RL circuits
- Already a solved problem!
- Get RC and RL into the form of the solved problem
 - Find Thevenin Equivalent circuit
 - Find τ
- Find coefficients
 - Need $t \rightarrow \infty$ and initial condition $t=0+$

sawyer@rpi.edu

www.rpi.edu/~sawyer



DYNAMIC CIRCUITS

$$y(t) = y_H + y_P$$

Homogeneous Response + Particular Response

$$y(t) = y_N + y_F$$

Natural Response + Forced Response

$$y_N = y_H; \quad y_F = y_P$$

$$y(t) = y_{ZI} + y_{ZS}$$

Zero-Input Response + Zero-State Response



RC CIRCUITS

Solution to Any Current or Voltage in Any Circuit Containing 1 C plus R's, Independent Sources and Dependent Sources, with a Switched DC Input:

$$y(t) = y_{SS} + (y_0 - y_{SS})e^{-(t-t_0)/\tau} \quad \text{for } t \geq t_0$$

$$\tau = R_{eq} C$$

Can Find y_0 , y_{SS} , τ
Directly From Circuit

R_{eq} = Equivalent Resistance Seen at Terminals of C



RL CIRCUITS

Solution to Any Current or Voltage in Any Circuit Containing 1 L plus R's, Independent Sources and Dependent Sources, with a Switched DC Input:

$$y(t) = y_{SS} + (y_0 - y_{SS})e^{-(t-t_0)/\tau} \quad \text{for } t \geq t_0$$

$$\tau = \frac{L}{R_{eq}}$$

Can Find y_0 , y_{SS} , τ
Directly From Circuit

R_{eq} = Equivalent Resistance Seen at Terminals of L



REVIEW: LECTURE 10


- Second order Series RLC and Parallel RLC
- Already solved problems!
- Get into standard form and find α , ω_0 and β (if needed)
- Compare α , ω_0 to find form of solution
- Find coefficients
- Need $t \rightarrow \infty$ and initial conditions both $V_C(0+)$ and $dV_C(0+)/dt$ for example

sawyer@rpi.edu

www.rpi.edu/~sawyer



SERIES RLC CIRCUITS

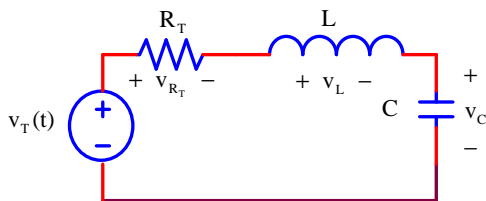

$$LC \frac{d^2 v_C}{dt^2} + R_T C \frac{dv_C}{dt} + v_C = v_T$$

$$\frac{d^2 v_C}{dt^2} + \frac{R_T}{L} \frac{dv_C}{dt} + \frac{1}{LC} v_C = \frac{1}{LC} v_T$$



SERIES RLC CIRCUITS


$$\frac{d^2 v_C}{dt^2} + \frac{R_T}{L} \frac{dv_C}{dt} + \frac{1}{LC} v_C = \frac{1}{LC} v_T$$

$$\left[\frac{1}{LC} \right] = \frac{1}{(\text{seconds})^2} = \omega_0^2 \quad \left[\frac{R_T}{L} \right] = \frac{1}{\text{seconds}} = 2\alpha$$

$$\frac{d^2 v_C}{dt^2} + 2\alpha \frac{dv_C}{dt} + \omega_0^2 v_C = \omega_0^2 v_T$$



SERIES RLC CIRCUITS

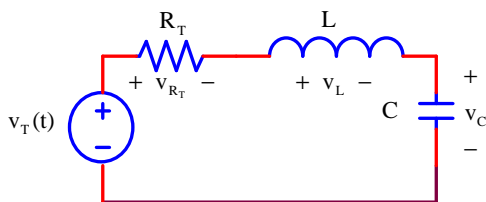

$$\frac{d^2 v_C}{dt^2} + 2\alpha \frac{dv_C}{dt} + \omega_0^2 v_C = \omega_0^2 v_T \quad \text{Need Initial Conditions}$$

$$v_C(0^+) \text{ and } \frac{dv_C}{dt}(0^+) \quad \frac{dv_C}{dt}(0^+) = \frac{1}{C} i_L(0^+)$$



SERIES RLC CIRCUITS

$$\frac{d^2 v_{CN}}{dt^2} + 2\alpha \frac{dv_{CN}}{dt} + \omega_0^2 v_{CN} = 0$$

$$\text{Assume } v_{CN}(t) = K e^{st}$$

$$s^2 + 2\alpha s + \omega_0^2 = 0$$

Characteristic Equation

$$\text{Roots are } s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$v_{CN}(t) = K_1 e^{s_1 t} + K_2 e^{s_2 t}$$



SERIES RLC CIRCUITS

$$s^2 + 2\alpha s + \omega_0^2 = 0$$

$$\text{Roots are } s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

3 Possible Cases:

Case 1: $\alpha^2 > \omega_0^2$: 2 Real, Unequal Roots

Case 2: $\alpha^2 = \omega_0^2$: 2 Real, Equal Roots

Case 3: $\alpha^2 < \omega_0^2$: 2 Complex Conjugate Roots



SERIES RLC CIRCUITS

Case 1: $\alpha^2 > \omega_0^2$: 2 Real, Unequal Roots

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \quad \alpha = \frac{R_T}{2L}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} \quad \omega_0^2 = \frac{1}{LC}$$

$$v_{CN} = K_1 e^{s_1 t} + K_2 e^{s_2 t}$$

2 Decaying Exponentials

Circuit is Overdamped



SERIES RLC CIRCUITS

Case 2: $\alpha^2 = \omega_0^2$: 2 Real, Equal Roots

$$s_1 = -\alpha \quad \alpha = \frac{R_T}{2L} \quad \omega_0^2 = \frac{1}{LC}$$

$$s_2 = -\alpha$$

$$v_{CN} = K_1 e^{-\alpha t} + K_2 t e^{-\alpha t}$$

Decaying Exponential + Exponentially Damped Ramp

Circuit is Critically Damped



SERIES RLC CIRCUITS

Case 3: $\alpha^2 < \omega_0^2$: 2 Complex Conjugate Roots

$$s_1 = -\alpha + j\sqrt{\omega_0^2 - \alpha^2} = -\alpha + j\beta$$

$$s_2 = -\alpha - j\sqrt{\omega_0^2 - \alpha^2} = -\alpha - j\beta$$

$$v_{CN} = K_1 e^{(-\alpha + j\beta)t} + K_2 e^{(-\alpha - j\beta)t}$$


$$v_{CN} = A e^{-\alpha t} \cos(\beta t + \phi)$$

Exponentially Damped Sinusoid

Circuit is Underdamped



PARALLEL RLC CIRCUITS

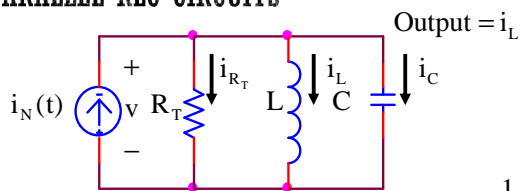

$$\frac{d^2 i_L}{dt^2} + 2\alpha \frac{di_L}{dt} + \omega_0^2 i_L = \omega_0^2 i_N \quad \alpha = \frac{1}{2R_T C}$$

Same Form of Equation as for Series RLC $\omega_0^2 = \frac{1}{LC}$

Slightly Different α

sawyer@rpi.edu

www.rpi.edu/~sawyer



PARALLEL RLC CIRCUITS

Parallel RLC Circuits

LHS of Differential Equation is Same for Any Output

Natural Response for Any Output

$$\frac{d^2 y_N}{dt^2} + 2\alpha \frac{dy_N}{dt} + \omega_0^2 y_N = 0$$

Same as for Series RLC Circuits

sawyer@rpi.edu

www.rpi.edu/~sawyer



PARALLEL RLC CIRCUITS

Natural Response

$$\frac{d^2 y_N}{dt^2} + 2\alpha \frac{dy_N}{dt} + \omega_0^2 y_N = 0$$

Characteristic Equation

$$s^2 + 2\alpha s + \omega_0^2 = 0$$

Same Roots as for Series RLC

Overdamping, Critical Damping, Underdamping

sawyer@rpi.edu

www.rpi.edu/~sawyer



REVIEW: LECTURE 12 AND 13

- Laplace transforms
- Finding poles and zeros
- Partial Fraction Expansion
 - Simple real poles
 - Complex conjugate poles
 - Double poles
- Relationship to differential equations
- S-domain impedances (zero and non-zero initial conditions)

sawyer@rpi.edu

www.rpi.edu/~sawyer



LAPLACE TRANSFORMS

Signal	$f(t)$	$F(s)$
Impulse	$\delta(t)$	1
Step	$u(t)$	$\frac{1}{s}$
Constant	$Au(t)$	$\frac{A}{s}$
Ramp	$tu(t)$	$\frac{1}{s^2}$

sawyes@rpi.edu

www.rpi.edu/~sawyes



LAPLACE TRANSFORMS

Signal	$f(t)$	$F(s)$
Exponential	$e^{-\alpha t}u(t)$	$\frac{1}{s + \alpha}$
Damped Ramp	$[te^{-\alpha t}]u(t)$	$\frac{1}{(s + \alpha)^2}$
Cosine Wave	$[\cos \beta t]u(t)$	$\frac{s}{s^2 + \beta^2}$
Damped Cosine	$[e^{-\alpha t} \cos \beta t]u(t)$	$\frac{s + \alpha}{(s + \alpha)^2 + \beta^2}$

sawyes@rpi.edu

www.rpi.edu/~sawyes



LAPLACE TRANSFORMS

Time Domain	s-Domain
$AF_1(t) + BF_2(t)$	$AF_1(s) + BF_2(s)$
$\int_0^t f(\tau) d\tau$	$\frac{F(s)}{s}$
$\frac{df(t)}{dt}$	$sF(s) - f(0^-)$
$e^{-\alpha t}f(t)$	$F(s + \alpha)$
$t f(t)$	$-dF(s)/ds$
$f(t-a)u(t-a)$	$e^{-as}F(s)$

sawyes@rpi.edu

www.rpi.edu/~sawyes



POLES AND ZEROS

$$F(s) = \frac{b_m s^m + \dots + b_1 s + b_0}{a_n s^n + \dots + a_1 s + a_0}$$

Factor $F(s)$:

$$F(s) = K \frac{(s - z_1)(s - z_2) \dots (s - z_m)}{(s - p_1)(s - p_2) \dots (s - p_n)}$$

$$K = \frac{b_m}{a_n} = \text{Scale Factor}$$

sawyes@rpi.edu

www.rpi.edu/~sawyes



POLES AND ZEROS

$$F(s) = K \frac{(s - z_1)(s - z_2) \dots (s - z_m)}{(s - p_1)(s - p_2) \dots (s - p_n)}$$

At $s = z_i \Rightarrow F(s) \rightarrow 0 \Rightarrow$ Zeros of $F(s)$

At $s = p_j \Rightarrow F(s) \rightarrow \infty \Rightarrow$ Poles of $F(s)$

Poles and Zeros are "Critical Frequencies" of $F(s)$


Useful to Plot "Pole-Zero Diagram" in s-plane

sawyes@rpi.edu

www.rpi.edu/~sawyes



POLE-ZERO DIAGRAMS

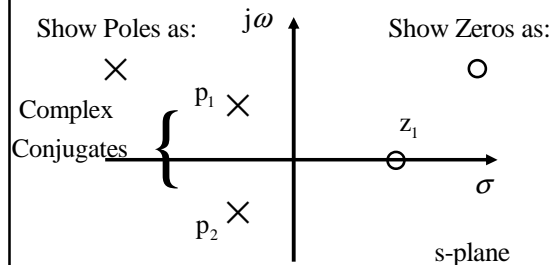

sawyes@rpi.edu

www.rpi.edu/~sawyes



PARTIAL FRACTION EXPANSION

There are only 3 Types of Poles:

Simple, Real Poles: $(s-4)$, $\Rightarrow p_1 = 4$

Real, Equal Poles: $(s+3)^2$, $\Rightarrow p_1 = p_2 = -3$

Complex Conjugate Poles: $(s^2 + 8s + 25)$
 $\Rightarrow p_1, p_2 = -4 \pm j3$



PARTIAL FRACTION EXPANSION

For $m < n$:

- Simple Real Poles

In General:

$$\text{Expand: } F(s) = \frac{A_1}{s-p_1} + \frac{A_2}{s-p_2} + \frac{A_3}{s-p_3} + \dots$$

$$A_n = [(s-p_n)F(s)]|_{s=p_n}; \quad \text{Cover-Up Rule}$$

$$\Rightarrow f(t) = A_1 e^{p_1 t} + A_2 e^{p_2 t} + A_3 e^{p_3 t} + \dots \quad t \geq 0$$



PARTIAL FRACTION EXPANSION

- Complex Conjugate Poles

In General:

$$\text{Expand } F(s) = \frac{A_1}{s-p_1} + \dots + \frac{A}{s+\alpha-j\beta} + \frac{A^*}{s+\alpha+j\beta}$$

Find A_1 and $A = |A|/\phi$ from Cover-Up Rule

$$\Rightarrow f(t) = A_1 e^{p_1 t} + \dots + 2|A|e^{-\alpha t} \cos(\beta t + \phi) \quad t \geq 0$$

Simple Poles Complex Poles



PARTIAL FRACTION EXPANSION

- Real, Equal Poles – Double Pole:

$$\text{Expand } F(s) = \frac{A_1}{s-p_1} + \dots + \left[\frac{A_{n1}}{s-p_n} + \frac{A_{n2}}{(s-p_n)^2} \right]$$

$$A_{n2} = [(s-p_n)^2 F(s)]|_{s=p_n}; \quad \text{Cover-Up Rule}$$

Usually Find A_{n1} from evaluating $F(0)$ or $F(1)$


$$\Rightarrow f(t) = (A_1 e^{p_1 t} + \dots + A_{n1} e^{p_n t} + A_{n2} t e^{p_n t}) \quad t \geq 0$$

Simple Poles Repeated Poles



IMPEDANCE

Zero initial conditions

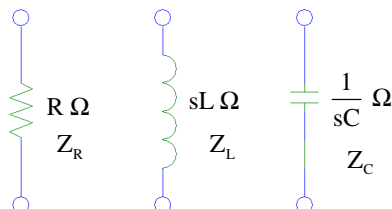


$$Z = \text{Impedance} = \frac{V(s)}{I(s)}$$

sawyes@rpi.edu

www.rpi.edu/~sawyes



NON-ZERO INITIAL CONDITIONS

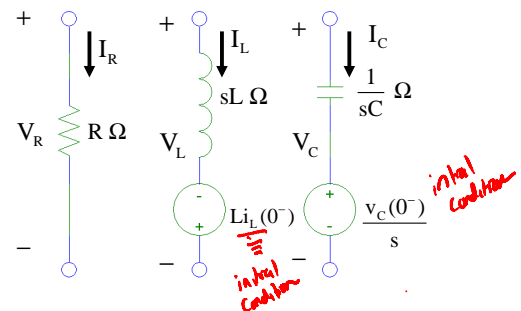

REVIEW: LECTURE 14 CIRCUIT ANALYSIS


- Unit 1 + Unit 2 in one problem

sawyes@rpi.edu

www.rpi.edu/~sawyes



GENERAL PROCESS

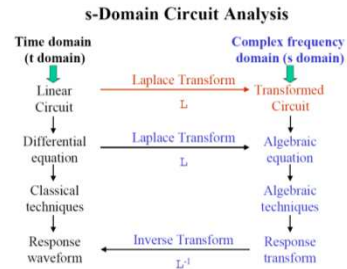

sawyes@rpi.edu

www.rpi.edu/~sawyes



CIRCUITS WITH LAPLACE

- Find Initial Conditions
- Determine Laplace Equivalent circuit
- Use Unit 1 concepts (node/mesh/voltage dividers etc.) to find an expression for the parameter of interest (impedances)
 - "Clean up" expression to have $\frac{N(s)}{D(s)}$
- Find poles (zeros, Unit 3)
- Partial fraction expansion
 - Cover up rule for coefficients or $F(0)$, $F(1)$
- Inverse Laplace gives time domain response



EXAM DETAILS

All questions are similar to problems done in class, homework, or lab!

- Short answer section
 - May include any mini-analysis
- First order circuit (Diff. Eq.)
- Second order circuit (Diff. Eq.)
- Second order circuit (Diff. Eq.)
- Second order circuit (Laplace)

sawyes@rpi.edu

www.rpi.edu/~sawyes



OTHER SHORT ANSWER QUESTIONS


- Voltage/Current continuity
- Overdamped, underdamped, critically damped analysis
- Laplace transforms
- Equivalent impedance conversion in s-domain
- Partial fraction expansion
- Pole-zero diagram

sawyes@rpi.edu

www.rpi.edu/~sawyes



VOLTAGE/CURRENT CONTINUITY

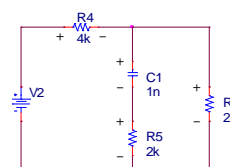

In the above circuit, the voltage is defined as follows:


$$V_1 = \begin{cases} 5V & t < 0 \\ 10V & 0 < t \end{cases} \quad \text{(the voltage source changes from 5V to 10V at } t = 0 \text{)}$$

sawyes@rpi.edu

www.rpi.edu/~sawyes




FIRST ORDER DIFFERENTIAL EQUATIONS

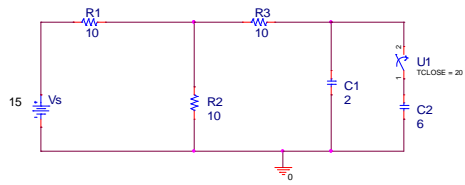

In the above circuit, the source turns on at $t = 0$ with a voltage of 15V, $V_s = 15u(t)V$. Additionally, at $t = 20s$ the switch in series with $C2$ is closed. You can (should) ignore $C2$ for part a) of this problem.

sawyes@rpi.edu

www.rpi.edu/~sawyes

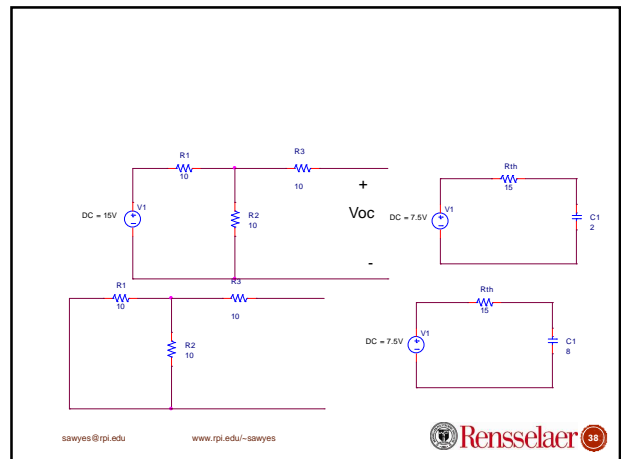


sawyes@rpi.edu

www.rpi.edu/~sawyes



SECOND ORDER DIFFERENTIAL EQUATIONS

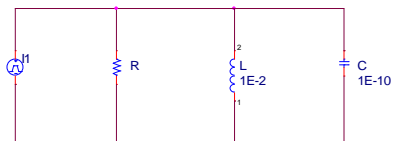


In the above circuit, the source current is 20mA for $t < 0$ and 0 for $t > 0$ (the source turns off at $t = 0$).

sawyes@rpi.edu

www.rpi.edu/~sawyes



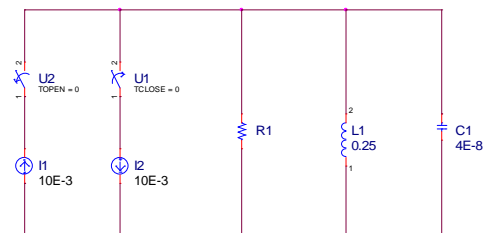SECOND ORDER LAPLACE WITH INITIAL CONDITIONS



sawyes@rpi.edu

www.rpi.edu/~sawyes

