

ELECTRIC CIRCUITS

ECSE-2010

Lecture 19.1



Rensselaer

LECTURE 19.1 AGENDA

- Kirkoff's laws for phasors
- AC steady state impedance
- Examples



PHASORS

Phasors module

Phasor = Rotating Vector in Complex Space

Phasor \underline{X} Rotates Counterclockwise at
Angular Frequency ω

Amplitude (or Magnitude) of $\underline{X} = |\underline{X}|$

Angle (or Phase) of $\underline{X} = \angle \underline{X} = \phi_X$

=> Can Express as $\underline{X} = |\underline{X}| \angle \phi_X$ => " $|\underline{X}|$ at an angle of ϕ_X "

$\underline{X} = |\underline{X}| \angle \phi_X$ = "Polar Form for \underline{X} "

K'S LAWS FOR PHASORS

- **Circuit in AC steady state:**

$$\text{Input} = x(t) = |X| \cos(\omega t + \phi_X)$$

Express $x(t)$ as a Phasor $\underline{X} = |X| / \underline{\phi_X}$

- **Can express all v's and i's in circuit as phasors:**

$$v_1(t) \rightarrow \underline{V_1}; \quad v_2(t) \rightarrow \underline{V_2}$$

$$i_1(t) \rightarrow \underline{I_1}; \quad i_2(t) \rightarrow \underline{I_2}$$

AC STEADY STATE

■ Time Domain:

- Currents, Voltages expressed as Sinusoids; $i(t)$, $v(t)$

■ Frequency Domain:

- Currents, Voltages expressed as Phasors; \underline{I} , \underline{V}

K'S LAWS FOR PHASORS

■ KCL:

- If $i_1 + i_2 = i$; $\Rightarrow \underline{I}_1 + \underline{I}_2 = \underline{I}$

■ KVL:

- If $v_1 + v_2 = v$; $\Rightarrow \underline{V}_1 + \underline{V}_2 = \underline{V}$

■ K's Laws Work for Phasors!

- Complex Addition, not Simple Addition

AC STEADY STATE

■ Phasor Diagram:

- Plot of Phasors in Complex Space
- Same as Plotting Vectors in Real Space

AC STEADY STATE IMPEDANCE


■ Capacitor:

$$i_C = C \frac{dv_C}{dt}$$

$$v_C(t) = V \cos(\omega t + \phi)$$

$$= \text{Real} \left[V e^{j(\omega t + \phi)} \right]$$
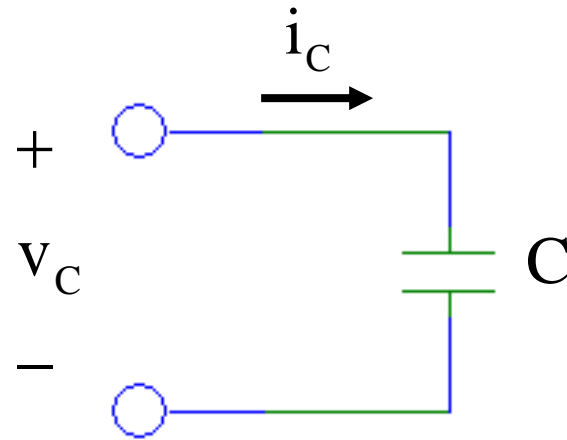
$$= \text{Real} \left[V e^{j\phi} e^{j\omega t} \right] = \text{Real} \left[\underline{V_C} e^{j\omega t} \right]$$



AC STEADY STATE IMPEDANCE


■ Inductor:

$$v_L = L \frac{di_L}{dt}$$

$$i_L(t) = I \cos(\omega t + \phi)$$

$$= \text{Real} \left[I e^{j(\omega t + \phi)} \right]$$
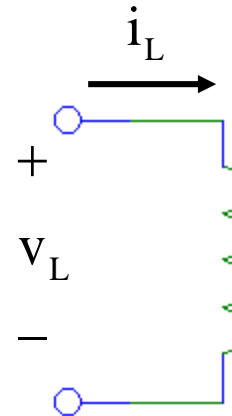
$$= \text{Real} \left[I e^{j\phi} e^{j\omega t} \right] = \text{Real} \left[\underline{I_L} e^{j\omega t} \right]$$



AC STEADY STATE IMPEDANCE

$$Z_R = R \Omega$$

$$Z_L = j\omega L \Omega$$

$$Z_C = -\frac{j}{\omega C} = \frac{1}{j\omega C} \Omega$$

AC STEADY STATE IMPEDANCE

Note:

$$\text{As } \omega \rightarrow 0; Z_L = j\omega L \rightarrow 0$$

Inductor is a Short Circuit for DC

$$\text{As } \omega \rightarrow \infty; Z_L = j\omega L \rightarrow \infty$$

Inductor is an Open Circuit for
Very High Frequencies

AC STEADY STATE IMPEDANCE

Note:

$$\text{As } \omega \rightarrow 0; Z_C = -\frac{j}{\omega C} \rightarrow \infty$$

Capacitor is an Open Circuit for DC

$$\text{As } \omega \rightarrow \infty; Z_C = -\frac{j}{\omega C} \rightarrow 0$$

Capacitor is a Short Circuit for
Very High Frequencies

AC STEADY STATE IMPEDANCE

- In General, $\underline{V} = Z \underline{I}$ in AC Steady State:
 - $Z =$ AC SS Impedance
 - Units of Ohms
 - Ohm's Law for AC Steady State
- $Y =$ AC Steady State Admittance
 - $= 1/Z$ (Units of Siemens)

AC STEADY STATE IMPADENCE

$\underline{V} = \underline{Z}\underline{I}$; Ohm's Law for AC Steady State

$Z = R(\omega) + jX(\omega) = \text{AC Steady State Impedance}$

$R(\omega) = \text{AC Steady State Resistance}$

$X(\omega) = \text{AC Steady State Reactance}$

$Y = G(\omega) + jB(\omega) = \text{AC Steady State Admittance}$

$G(\omega) = \text{AC Steady State Conductance}$

$B(\omega) = \text{AC Steady State Susceptance}$


AC SS CIRCUIT ANALYSIS

- Time Domain \rightarrow Frequency Domain
- Express all Voltages and Currents as Phasors
 $v_1(t) \rightarrow \underline{V}_1; \quad i_1(t) \rightarrow \underline{I}_1; \quad \text{etc.}$
- Express R, L and C with AC Steady State Impedances

$$Z_R = R \, \Omega; \quad Z_L = j\omega L \, \Omega; \quad Z_C = \frac{-j}{\omega C} \, \Omega$$

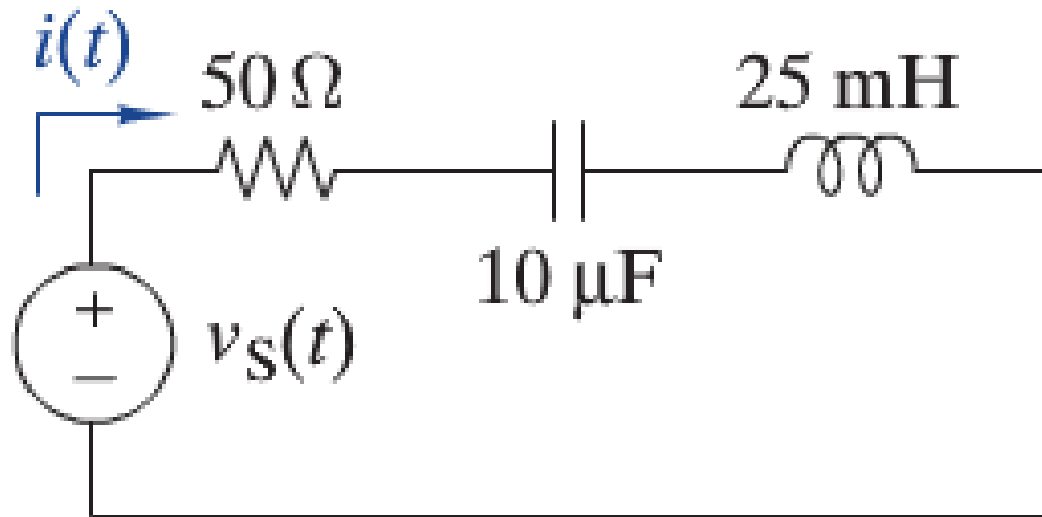EXAMPLE 1A

The circuit in Figure 8-15(a) is operating in the sinusoidal steady state with $v_s(t) = 35 \cos 100t$ V



(a)

EXAMPLE 1A

The circuit in Figure 8-15(a) is operating in the sinusoidal steady state with $v_s(t) = 35 \cos 100t$ V

- (a) Transform the circuit into the phasor domain
- (b) Solve the phasor current I
- (c) Solve for the phasor voltage across each element
- (d) Find the waveforms corresponding to the phasors found in (b) and (c)

EXAMPLE 1B

The circuit in Figure 8-15(a) is operating in the sinusoidal steady state with $v_s(t) = 100 \cos 2000t - 45^\circ \text{ V}$

- (a) Transform the circuit into the phasor domain
- (b) Solve the phasor current I
- (c) Solve for the phasor voltage across each element
- (d) Find the waveforms corresponding to the phasors found in (b) and (c)
- (e) Draw a phasor diagram of all three voltages and the current