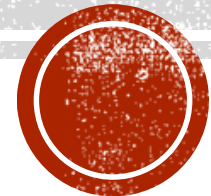


# **ELECTRIC CIRCUITS**

## **ECSE-2010**

Lecture 21.1



**Rensselaer**

# LECTURE 21.1

- AC Power
  - Average Power
  - Complex Power
  - Real Power
  - Reactive Power
  - Apparent Power
- Power Factor

# AC POWER

- **AC Steady State Circuit Analysis:**
  - Find  $\underline{V}$ ,  $\underline{I}$   $\Rightarrow$  Write down  $v(t)$ ,  $i(t)$
- **Will Now Focus on AC Power:**
  - **RMS Values**
  - **Average Power**
  - **Reactive Power**
  - **Complex Power**
  - **Power Factor**

# RMS VALUES

Consider  $x(t) = |X| \cos \omega t$       Periodic Function

$$x_{\text{ave}} = \frac{1}{T} \int_0^T |X| \cos \omega t \, dt = 0$$

$$(x^2)_{\text{ave}} = \frac{1}{T} \int_0^T |X|^2 \cos^2 \omega t \, dt = \frac{|X|^2}{2}$$

$$\text{Define } X_{\text{RMS}} = \sqrt{(x^2)_{\text{ave}}}$$

$$\text{For Sinusoids: } X_{\text{RMS}} = \frac{|X|}{\sqrt{2}} = .707 |X|$$

# RMS VALUES

AC Voltage,  $v(t) = |V| \cos(\omega t + \phi)$

$$\Rightarrow V_{\text{RMS}} = \frac{|V|}{\sqrt{2}} \text{ Volts (RMS)}$$

AC Current,  $i(t) = |I| \cos(\omega t + \psi)$

$$\Rightarrow I_{\text{RMS}} = \frac{|I|}{\sqrt{2}} \text{ Amps (RMS)}$$

# RMS VALUES

- **RMS Value is a Scalar:**
  - **Not a Phasor!**
- **Convenient Way to Describe Current and Voltage in AC Steady State:**

# RMS VALUES

- **Convenient Way to Calculate Power in AC Steady State:**
- **All Residential AC Electricity is Described in Terms of RMS Values:**
- **120 V = 120 Volts, RMS**

$$|V| = \sqrt{2}V_{\text{RMS}} \approx 170 \text{ Volts (0 to Peak)}$$

# REACTIVE POWER

Recall:

$$p(t) = |I|^2 \frac{|Z|}{2} (\cos \theta + \cos(2\omega t - \theta))$$

$$|Z| = \frac{V_m}{I_m} = \frac{V_{\text{RMS}}}{I_{\text{RMS}}}; \quad I_{\text{RMS}} = \frac{I_m}{\sqrt{2}}$$

$$\Rightarrow p(t) = V_{\text{RMS}} I_{\text{RMS}} (\cos \theta + \cos(2\omega t - \theta))$$



# REACTIVE POWER

Use a different Trigonometric Identity:

$$\cos(2\omega t - \theta) = \cos 2\omega t \cos \theta + \sin 2\omega t \sin \theta$$

$$\Rightarrow p(t) = V_{\text{RMS}} I_{\text{RMS}} (\cos \theta + \cos (2\omega t - \theta))$$

$$= V_{\text{RMS}} I_{\text{RMS}} \cos \theta (1 + \cos 2\omega t) + V_{\text{RMS}} I_{\text{RMS}} \sin \theta \sin 2\omega t$$

$$P = \frac{1}{T} \int_0^T p(t) dt = V_{\text{RMS}} I_{\text{RMS}} \cos \theta + 0 + 0$$

$\Rightarrow$  Same result as before

# REACTIVE POWER

Define  $P = \text{"Real Power"} = V_{\text{RMS}} I_{\text{RMS}} \cos \theta$

$P$  is Measured in Watts

Define  $Q = \text{"Reactive Power"} = V_{\text{RMS}} I_{\text{RMS}} \sin \theta$

$Q$  is Measured in VAR's

(Volt-Amperes-Reactive)

# REACTIVE POWER

- **Q is a Measure of the Rate of Change of Energy Stored in the Reactive Elements (L, C):**
  - ❑ **Power companies must worry about Q since they supplied this energy**
  - ❑ **Supplied Q over their Lines => Real Cost**
  - ❑ **Power companies want customers to have Low Q**

# REACTIVE POWER

- **Q is a Measure of the Rate of Change of Energy Stored in the Reactive Elements (L, C):**
  - ❑ **Big issue for a large user - like Rensselaer**
  - ❑ **Fans all use Motors - Motors are Inductive**
  - ❑ **Large users are charged for Q, not just P**

# REACTIVE POWER

Impedance Triangle:  $Z = |Z| \angle \theta$

$$R(\omega) = |Z| \cos \theta ; X(\omega) = |Z| \sin \theta$$

$$\begin{aligned} \Rightarrow \text{Real Power} = P &= V_{\text{RMS}} I_{\text{RMS}} \cos \theta \\ &= I_{\text{RMS}}^2 R(\omega) \quad [\text{Watts}] \end{aligned}$$

$$\begin{aligned} \Rightarrow \text{Reactive Power} = Q &= V_{\text{RMS}} I_{\text{RMS}} \sin \theta \\ &= I_{\text{RMS}}^2 X(\omega) \quad [\text{VAR's}] \end{aligned}$$

# REACTIVE POWER

$$P = I_{\text{RMS}}^2 |Z| \cos \theta$$

$$= I_{\text{RMS}}^2 R(\omega)$$

$$= V_{\text{RMS}} I_{\text{RMS}} \cos \theta$$

{ Equivalent ways of  
expressing Real Power

[Watts]

$$Q = I_{\text{RMS}}^2 |Z| \sin \theta$$

$$= I_{\text{RMS}}^2 X(\omega)$$

$$= V_{\text{RMS}} I_{\text{RMS}} \sin \theta$$

{ Equivalent ways of  
expressing Reactive Power

[VAR's]



# REACTIVE POWER

- **Notes on Reactive Power:**
  - **Real Power =  $P$  is always  $\geq 0$**
  - **Reactive Power =  $Q$  can be  $\geq 0$  or  $\leq 0$**
  - **For Inductive Load,  $X > 0 \Rightarrow Q > 0$**
  - **For Capacitive Load,  $X < 0 \Rightarrow Q < 0$**

# COMPLEX POWER

Define "Complex Power" =  $\underline{S} = P + jQ$

$\underline{S}$  is a Complex Number, but not a Phasor

$\underline{S}$  is a Convenient Way to Keep Track of P and Q

$$\text{Real}\{\underline{S}\} = P = V_{\text{RMS}} I_{\text{RMS}} \cos \theta \Rightarrow \text{Watts}$$

$$\text{Imag}\{\underline{S}\} = Q = V_{\text{RMS}} I_{\text{RMS}} \sin \theta \Rightarrow \text{VAR's}$$



# COMPLEX POWER

## ■ Significance of $\underline{S}$ = Complex Power:

- For Several Loads  $\Rightarrow \underline{S}_{\text{Total}} = \underline{S}_1 + \underline{S}_2 + \underline{S}_3 + \dots$
- $\underline{S}_{\text{Total}} = (P_1 + P_2 + \dots) + j (Q_1 + Q_2 + \dots)$
- Regardless of how loads are connected! Just Add P's and Q's


# APPARENT POWER

$$\text{Magnitude of } \underline{S} = |S| = \sqrt{P^2 + Q^2} = V_{\text{RMS}} I_{\text{RMS}}$$


$$|S| = \text{"Apparent Power"} \Rightarrow [\text{Volt-Amperes}]$$

$$|S| = \text{Product of } V_{\text{RMS}} \times I_{\text{RMS}} \text{ at Terminals}$$

# POWER TRIANGLE

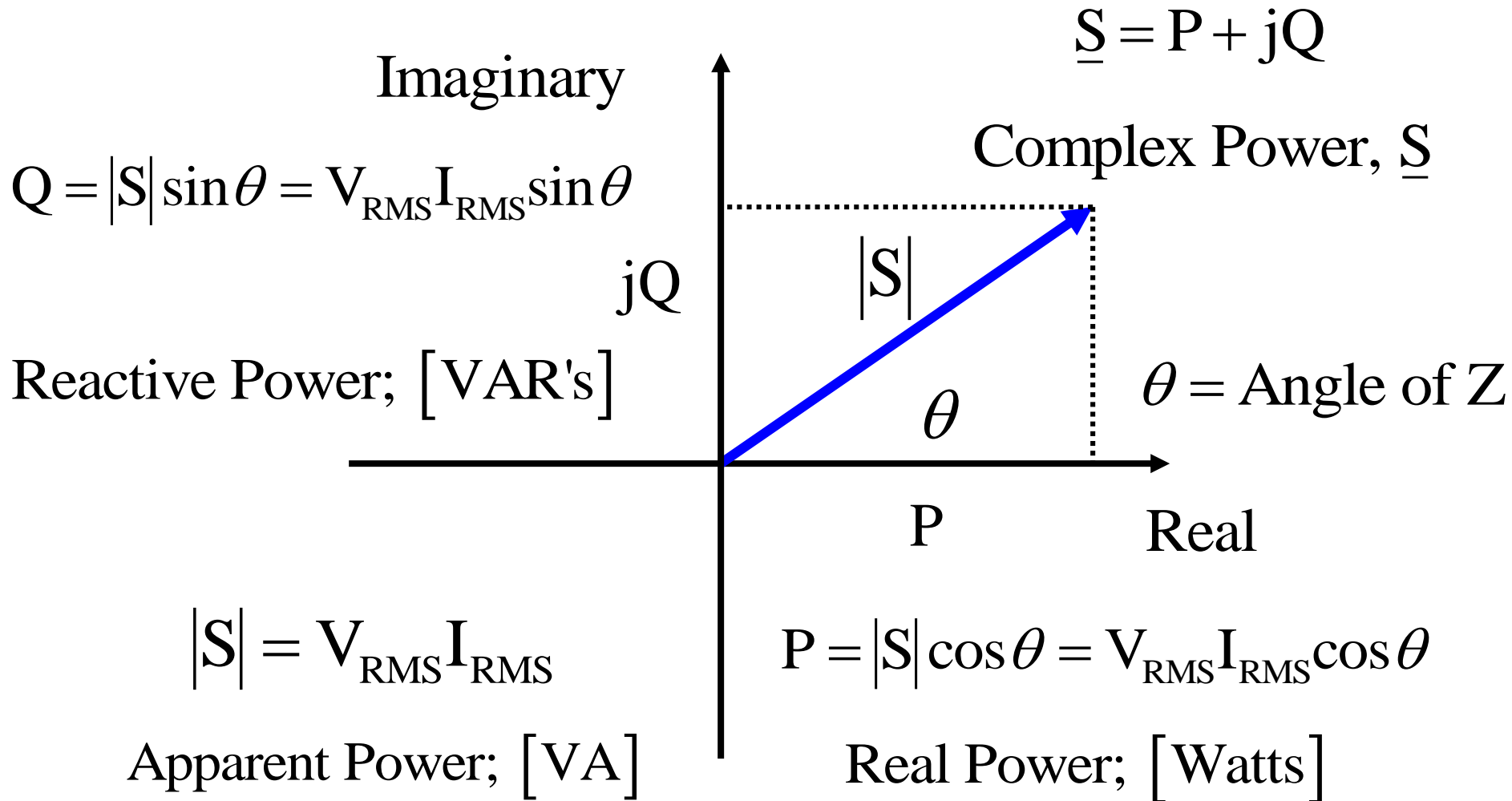

# POWER FACTOR

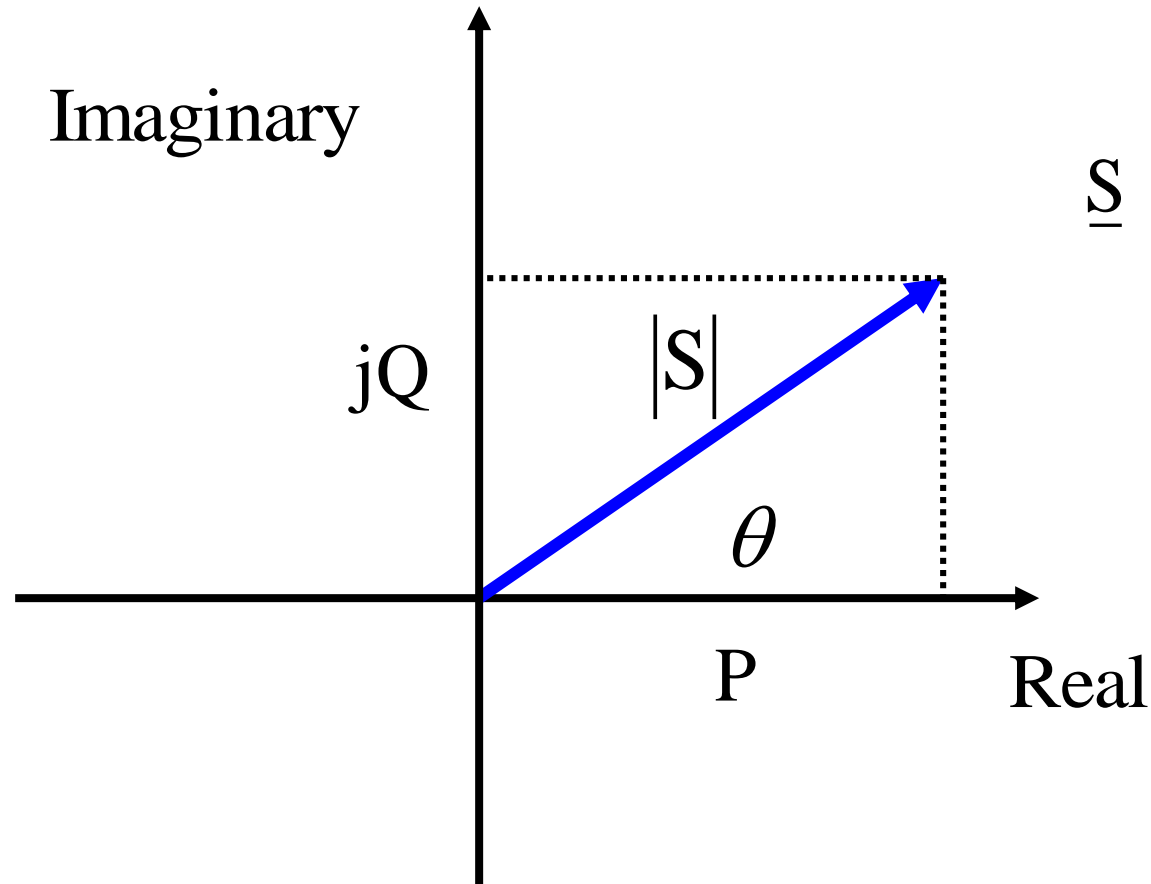

$$\cos \theta = \frac{P}{|S|} = \frac{\text{Real Power}}{\text{Apparent Power}} = \text{Power Factor} = \text{pf}$$



# POWER FACTOR

For Inductive Loads,  $\theta > 0$ ;  $\cos \theta > 0$

For Capacitive Loads,  $\theta < 0$ ;  $\cos \theta > 0$

Need a Way to Distinguish

$$\underline{I} = \frac{\underline{V}}{\underline{Z}} = \frac{|V| \angle \phi}{|Z| \angle \theta} = \frac{|V|}{|Z|} \angle \phi - \theta$$

If  $\theta > 0; \Rightarrow$  Lagging Power Factor ( $\underline{I}$  lags  $\underline{V}$ )

If  $\theta < 0; \Rightarrow$  Leading Power Factor ( $\underline{I}$  leads  $\underline{V}$ )

# POWER FACTOR

Power Factor:

Define  $\text{pf} = \cos \theta$ ;  $0 \leq \text{pf} \leq 1$

Must distinguish between  $\theta \geq 0$ ,  $\theta \leq 0$ :

$\theta \geq 0$ ;  $X \geq 0$ ;  $Q \geq 0$ ;  $\underline{I}$  lags  $\underline{V}$ ; lagging pf

$\theta \leq 0$ ;  $X \leq 0$ ;  $Q \leq 0$ ;  $\underline{I}$  leads  $\underline{V}$ ; leading pf

e.g: pf = .8 lagging  $\Rightarrow$  Inductive Load

pf = .8 leading  $\Rightarrow$  Capacitive Load