

ELECTRIC CIRCUITS

ECSE-2010

Lecture 24 continued



LECTURE 19.1 AGENDA


- First order low pass filter
- First order high pass filter

sawyes@rpi.edu

www.rpi.edu/~sawyes



FIRST ORDER FILTERS

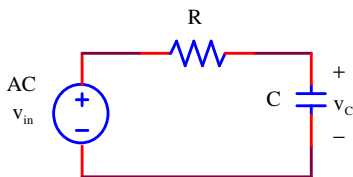


As $\omega \rightarrow 0$ (DC): $Z_C \rightarrow \infty$; $v_C = v_{in}$

As $\omega \rightarrow \infty$: $Z_C \rightarrow 0$; $v_C = 0$



FIRST ORDER FILTERS

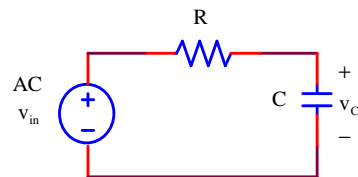

Let's look at this in the s-Domain

$$\text{Find } H(s) = \left. \frac{V_C(s)}{V_{in}(s)} \right|_{\text{No Initial Stored Energy}}$$



FIRST ORDER FILTERS

$$\underline{H(s)} = \frac{V_c(s)}{V(s)} = \frac{1/RC}{s + 1/RC} = \frac{1/\tau}{s + 1/\tau} = \frac{\omega_c}{s + \omega_c}$$

$$H(j\omega) = \frac{\omega_c}{\omega_c + j\omega} = |H(j\omega)| \angle \theta$$

$$|H(j\omega)| = \frac{\omega_c}{\sqrt{\omega^2 + \omega_c^2}} = \text{Gain} = \frac{1}{\sqrt{1 + \frac{\omega^2}{\omega_c^2}}}$$

$$\theta = -\tan^{-1} \frac{\omega}{\omega_c} = \text{Phase Shift}$$



1st ORDER LOW PASS FILTER

$$|H(j\omega)| = \frac{\omega_c}{\sqrt{\omega^2 + \omega_c^2}} = \text{Gain}$$

varying

At $\omega = 10\omega_c$, Gain $\approx \frac{1}{10}$; $20\log_{10}(\text{Gain}) \approx -20 \text{ dB}$

At $\omega = 100\omega_c$, Gain $\approx \frac{1}{100}$, $20\log_{10}(\text{Gain}) \approx -40 \text{ dB}$

At $\omega = 1000\omega_c$, Gain $\approx \frac{1}{1000}$, $20\log_{10}(\text{Gain}) \approx -60 \text{ dB}$


Gain decreases at a Slope = -20 dB/decade



1st ORDER LOW PASS FILTER


$$20\log_{10}|H| \text{ Gain in dB} \quad |H(j\omega)| = \frac{\omega_c}{\sqrt{\omega^2 + \omega_c^2}} = \text{Gain}$$

-3dB

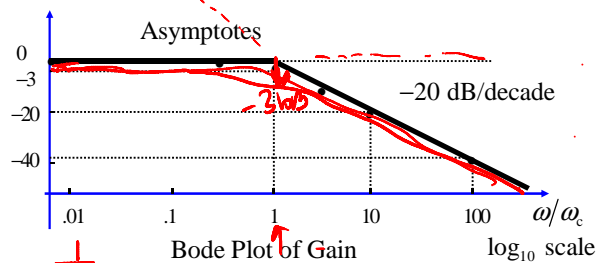

1st ORDER LOW PASS FILTER

$$20\log_{10}|H| \text{ Gain in dB} \quad |H(j\omega)| = \frac{\omega_c}{\sqrt{\omega^2 + \omega_c^2}} = \text{Gain}$$

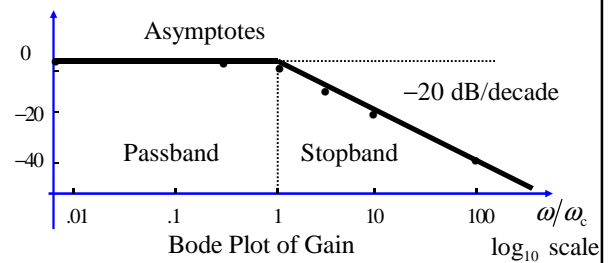

1st ORDER LOW PASS FILTER

$$\theta = -\tan^{-1} \frac{\omega}{\omega_c} = \text{Phase Shift}$$

For "low frequencies" ($\omega \ll \omega_c$): $\theta \rightarrow 0$

For "high frequencies" ($\omega \gg \omega_c$): $\theta \rightarrow -90^\circ$

For $\omega = \omega_c$: $\theta = -45^\circ$


Most of the change in θ occurs for $.1 \leq \frac{\omega}{\omega_c} \leq 10$

Corner Frequencies at $\frac{\omega}{\omega_c} = .1, 10$




1st ORDER LOW PASS FILTER
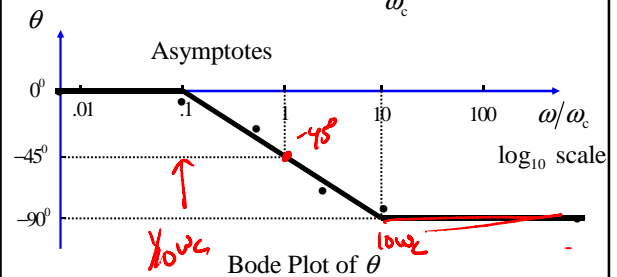
$$\theta = -\tan^{-1} \frac{\omega}{\omega_c} = \text{Phase Shift}$$



1st ORDER LOW PASS FILTER

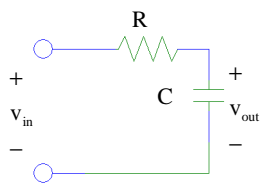


$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{1/RC}{s + 1/RC} = \frac{\omega_c}{s + \omega_c} \Rightarrow \text{Low Pass Filter}$$


Low Frequencies "Pass"; High Frequencies "Stopped"



BETTER 1st ORDER LOW PASS

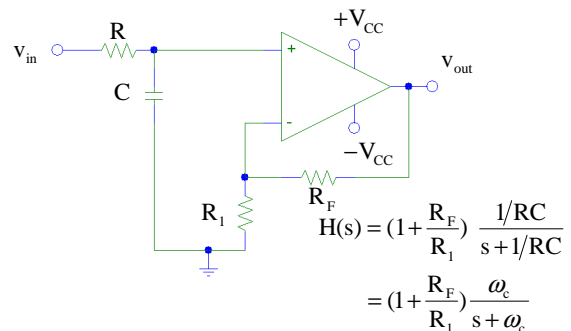

1st ORDER HIGH PASS FILTER

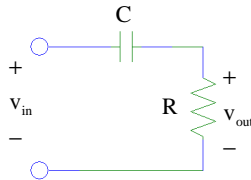

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{s}{s + 1/RC} = \frac{s}{s + \omega_c} \Rightarrow \text{High Pass Filter}$$

High Frequencies "Pass"; Low Frequencies "Stopped"



1st ORDER HIGH PASS FILTER

$$|H(j\omega)| = \frac{\omega}{\sqrt{\omega^2 + \omega_c^2}} = \text{Gain}$$

As $\omega \rightarrow 0$, Gain $\rightarrow 0$, $20\log_{10}(\text{Gain}) \rightarrow -\infty$

$$\text{At } \omega = .01\omega_c, \text{ Gain} = \frac{.01\omega_c}{\sqrt{(.01)^2 + \omega_c^2}} \approx .01$$

$$20\log_{10}(\text{Gain}) = -40 \text{ dB}$$



1st ORDER HIGH PASS FILTER

$$|H(j\omega)| = \frac{\omega}{\sqrt{\omega^2 + \omega_c^2}} = \text{Gain}$$

At $\omega = .01\omega_c$, Gain $\approx .01$; $20\log_{10}(\text{Gain}) \approx -40 \text{ dB}$

At $\omega = .1\omega_c$, Gain $\approx .1$, $20\log_{10}(\text{Gain}) \approx -20 \text{ dB}$

Gain increases at a Slope = +20 dB/decade


At $\omega = \omega_c$, Gain = $\frac{1}{\sqrt{2}}$, $20\log_{10}(\text{Gain}) = -3 \text{ dB}$




1st ORDER HIGH PASS FILTER

$$20\log_{10}|H| \quad |H(j\omega)| = \frac{\omega}{\sqrt{\omega^2 + \omega_c^2}} = \text{Gain}$$

Gain in dB

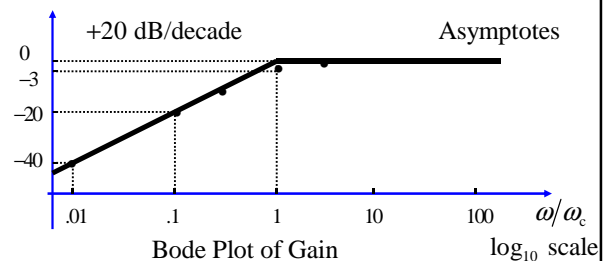

1st ORDER HIGH PASS FILTER

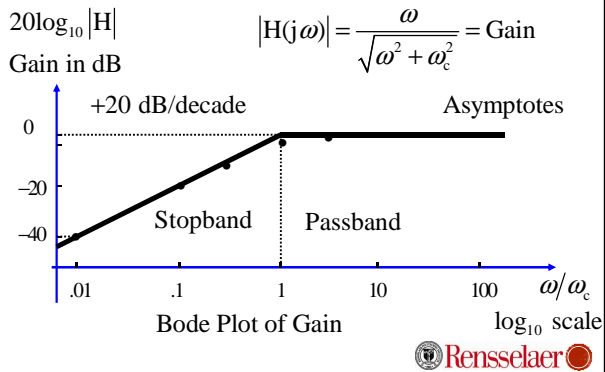

1st ORDER HIGH PASS FILTER

$$\theta = 90^\circ - \tan^{-1} \frac{\omega}{\omega_c} = \text{Phase Shift}$$

For "low frequencies" ($\omega \ll \omega_c$): $\theta \rightarrow 90^\circ$

For "high frequencies" ($\omega \gg \omega_c$): $\theta \rightarrow 0^\circ$


For $\omega = \omega_c$: $\theta = +45^\circ$

Most of the change in θ occurs for $.1 \leq \frac{\omega}{\omega_c} \leq 10$


Corner Frequencies at $\frac{\omega}{\omega_c} = .1, 10$



1st ORDER HIGH PASS FILTER

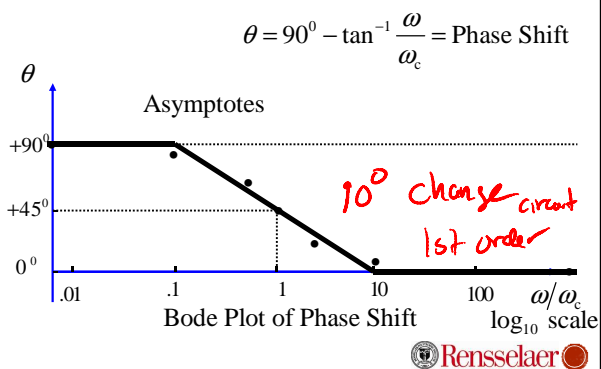

BETTER 1st ORDER HIGH PASS

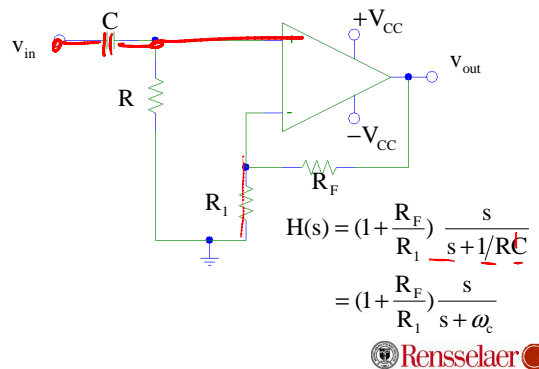

USING STRAIGHT LINE APPROXIMATIONS MAGNITUDE BODE PLOTS

1. Find poles, zeros
2. In each region between sequential poles/zeros, can use $H(j\omega)$ or $H(s)$
 - a) Draw line in first region based on three possibilities based on frequency range
 - b) Repeat for every region
3. Add corrections at poles/zeros
 - a) n *pole n (-3db) correction at that pole
 - b) n *zero n (+3db) correction at that zero

sawyes@rpi.edu

www.rpi.edu/~sawyes



USING STRAIGHT LINE APPROXIMATIONS MAGNITUDE BODE PLOTS

We have three possibilities

Note: Can ALSO analyze using $H(s)$ instead of $H(j\omega)$

$$H(j\omega) \propto \omega^n \quad +n \cdot 20 \frac{\text{db}}{\text{dec}} \quad \text{slope}$$

$$H(j\omega) \propto \text{constant}, K \quad \text{constant} \quad 20 \log |K|$$

$$H(j\omega) \propto \frac{1}{\omega^n} \quad -n \cdot 20 \frac{\text{db}}{\text{dec}} \quad \text{slope}$$

sawyes@rpi.edu

www.rpi.edu/~sawyes



USING STRAIGHT LINE APPROXIMATIONS PHASE BODE PLOTS

1. Crossing a n *pole is a change of phase of $-n \cdot 90$ deg (absolute change)
 - a) Changing over approximately two decades
 - b) Specifically, 0.1 and 10 times ω_c
2. Crossing a n *zero is a change of phase $+n \cdot 90$ deg (absolute change)
 - a) Changing over approximately two decades
 - b) Specifically, 0.1 and 10 times ω_c

sawyes@rpi.edu

www.rpi.edu/~sawyes



USING STRAIGHT LINE APPROXIMATIONS PHASE BODE PLOTS

1. Crossing a n *pole is a change of phase of $-n \cdot 90$ deg (absolute change)
 - a) Changing over approximately two decades
 - b) Specifically, 0.1 and 10 times ω_c
2. Crossing a n *zero is a change of phase $+n \cdot 90$ deg (absolute change)
 - a) Changing over approximately two decades
 - b) Specifically, 0.1 and 10 times ω_c

SLA have slopes of $\pm n \cdot 45$ deg per decade slope (+ is a zero, - is a pole)

sawyes@rpi.edu

www.rpi.edu/~sawyes



ELECTRIC CIRCUITS ECSE-2010

Lecture 19.2



LECTURE 19.2 AGENDA

- Cascaded filters/Parallel filters
- First order Bandpass filter
- First order Bandstop (Notch filter)

sawyer@rpi.edu

www.rpi.edu/~sawyer



LOW PASS + HIGH PASS

$$H(s) = K \left(\frac{s}{s + \omega_{CH}} \right) \left(\frac{\omega_{CL}}{s + \omega_{CL}} \right)$$

$$|H(j\omega)| = |K| \left(\frac{\omega}{\sqrt{\omega^2 + \omega_{CH}^2}} \right) \left(\frac{\omega_{CL}}{\sqrt{\omega^2 + \omega_{CL}^2}} \right)$$


High Pass Low Pass

Let's Design Such that $\omega_{CL} > \omega_{CH}$

$$\Rightarrow R_H C_H > R_L C_L$$



BANDPASS FILTER

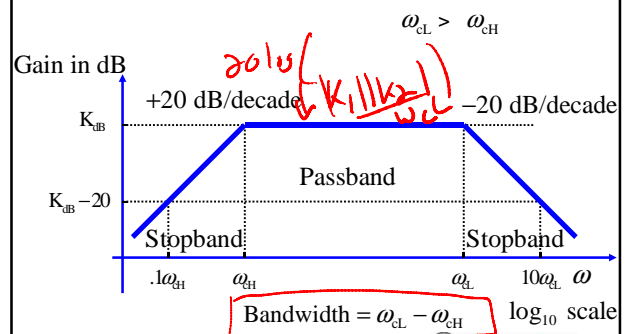

LOW PASS + HIGH PASS

$$H(s) = H_L(s) + H_H(s) = \left(1 + \frac{R_A}{R_B}\right) \left(\frac{\omega_{cl}}{s + \omega_{cl}} + \frac{s}{s + \omega_{ch}} \right)$$

For Low Frequencies \Rightarrow Looks Like a 1st Order Low Pass

For High Frequencies \Rightarrow Looks Like a 1st Order High Pass


Let's Design Such that $\omega_{ch} > \omega_{cl}$

$$\Rightarrow R_L C_L > R_H C_H$$




BANDGAP OR NOTCH FILTER

$$H(s) = H_1(s) + H_2(s)$$

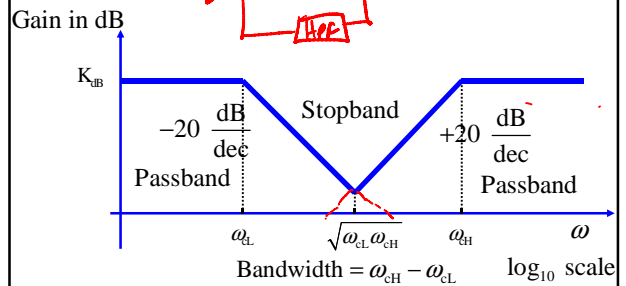

a) $H(s) = \frac{1000}{(s+1000)}$

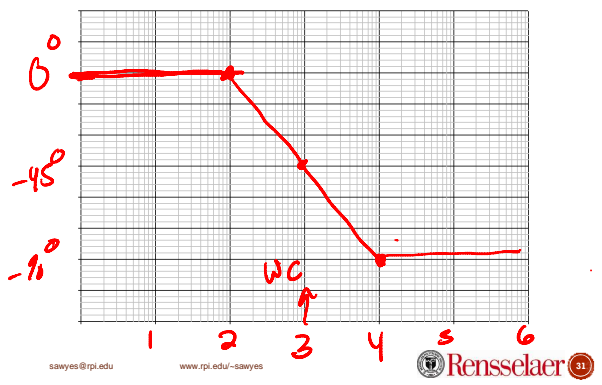


sawyer@rpi.edu

www.rpi.edu/~sawyer



a) $H(s) = \frac{1000}{(s+1000)}$





$$\omega_c = 10^3$$




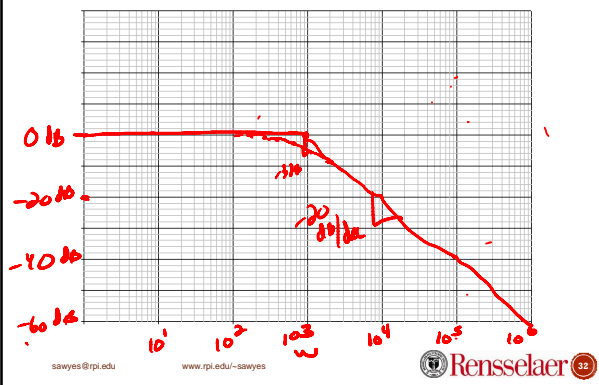


sawyer@rpi.edu


www.rpi.edu/~sawyer



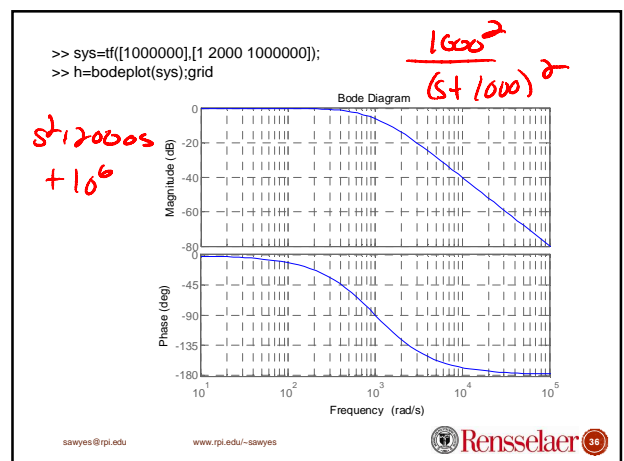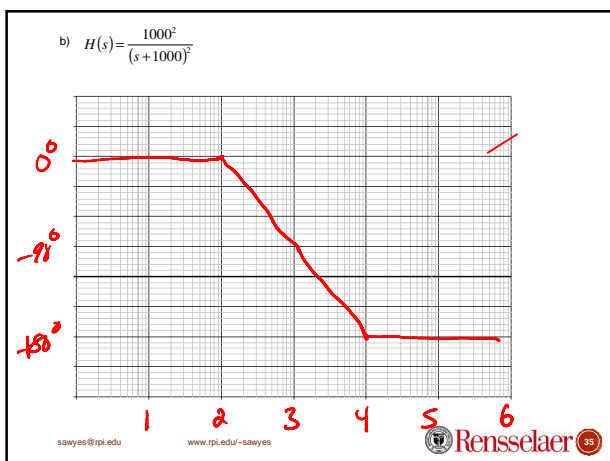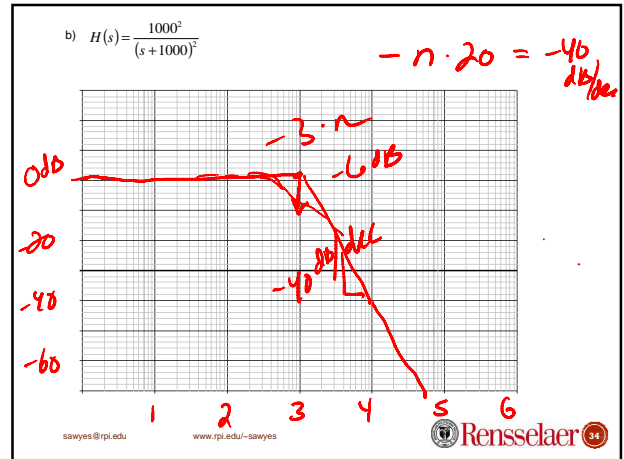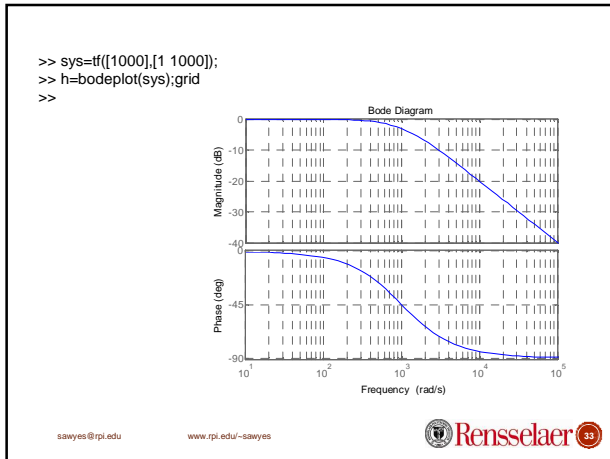

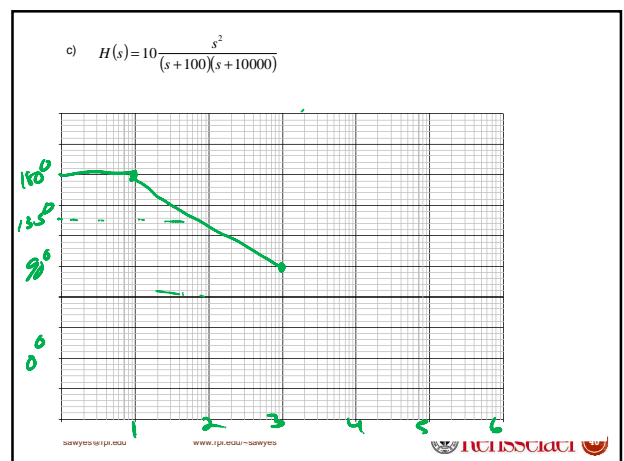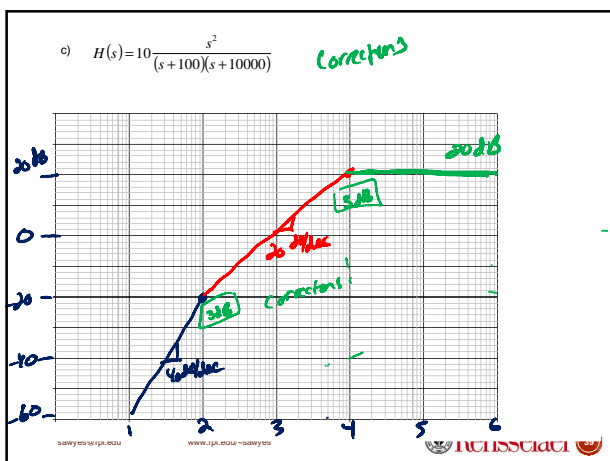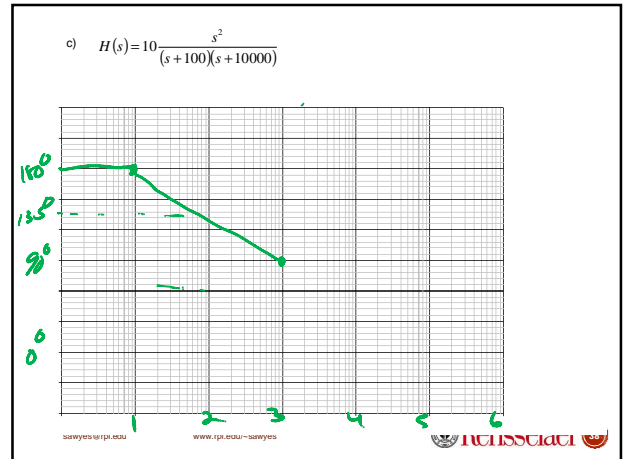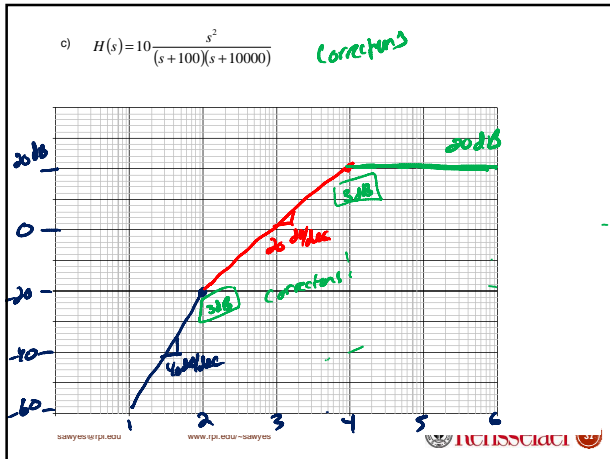
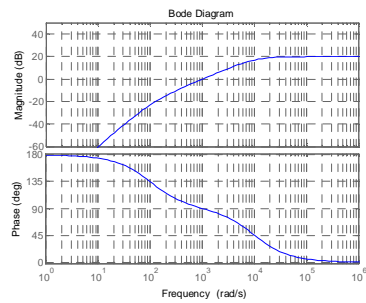
```
>> sys=tf([10 0 0],[1 10100 1000000]);
>> h=bodeplot(sys);grid
>> setoptions(h,'MagLowerLimMode','manual','MagLowerLim',-60)
```




sawyes@rpi.edu

www.rpi.edu/~sawyes




2) Bode plot-multiple stages

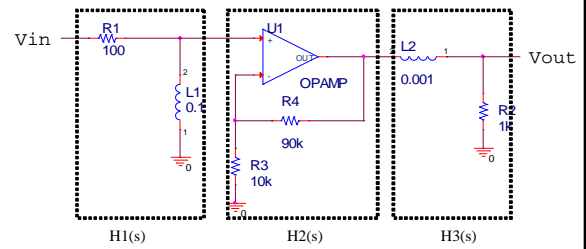


sawyes@rpi.edu

www.rpi.edu/~sawyes

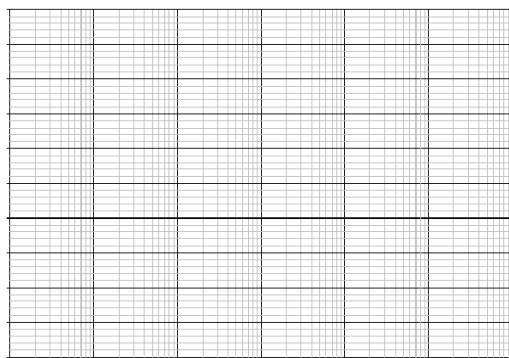

sawyes@rpi.edu

www.rpi.edu/~sawyes

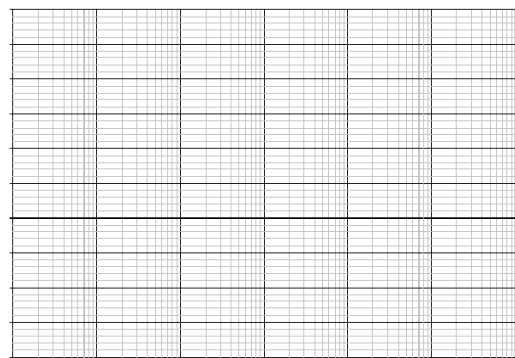


sawyes@rpi.edu

www.rpi.edu/~sawyes


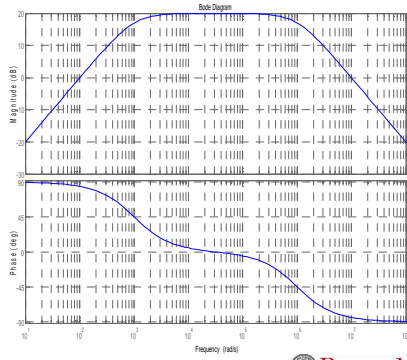
```
>> sys=tf([10000000 0],[1 1001000 100000000]);
>> h=bodeplot(sys);grid
```



sawyes@rpi.edu

www.rpi.edu/~sawyes

