

ELECTRIC CIRCUITS ECSE-2010

Lecture 27




LECTURE 22.1

- Filter design principles
- Example



PASSIVE VS. ACTIVE FILTER

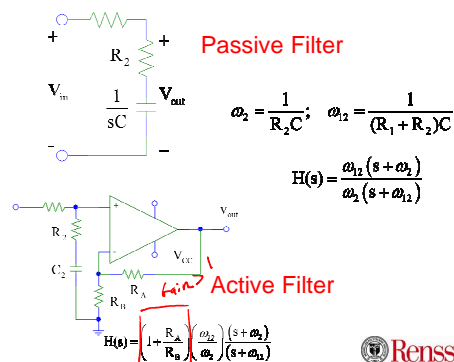

PASSIVE VS. ACTIVE FILTER

- Active Filter Better
 - Provide frequency selectivity comparable to passive RLC plus gains greater than one
 - They have Op Amp outputs so chain rule applies in cascade design
 - They do not require inductors, which are large and lossy and expensive at low freq.



CHAIN RULE

→ stage

- $H(s) = H_1(s) \times H_2(s) \times H_3(s) \times \dots \times H_n(s)$
- Stages can be either first or second order
- Design an active filter by controlling the poles introduced by each stage of a cascade connection
 - Denominator controls location of poles and critical frequencies
 - Numerator controls zeros and type of filter



SECOND ORDER CIRCUITS

- Critically damping is equivalent to cascaded first order circuits (-6 dB corrections at one frequency) *double poles*
- Overdamping is equivalent to cascaded first order circuits (Two -3dB corrections at two different frequencies)
- *** Underdamping can achieve a flat(ter) *** passband with the same stopband *damps*



EXAMPLE

- Low pass filter, $\omega_c = 10^8$
- Stopband rolloff 60 dB
- Cutoff frequency $H(j\omega)$ is -9dB relative to passband

