
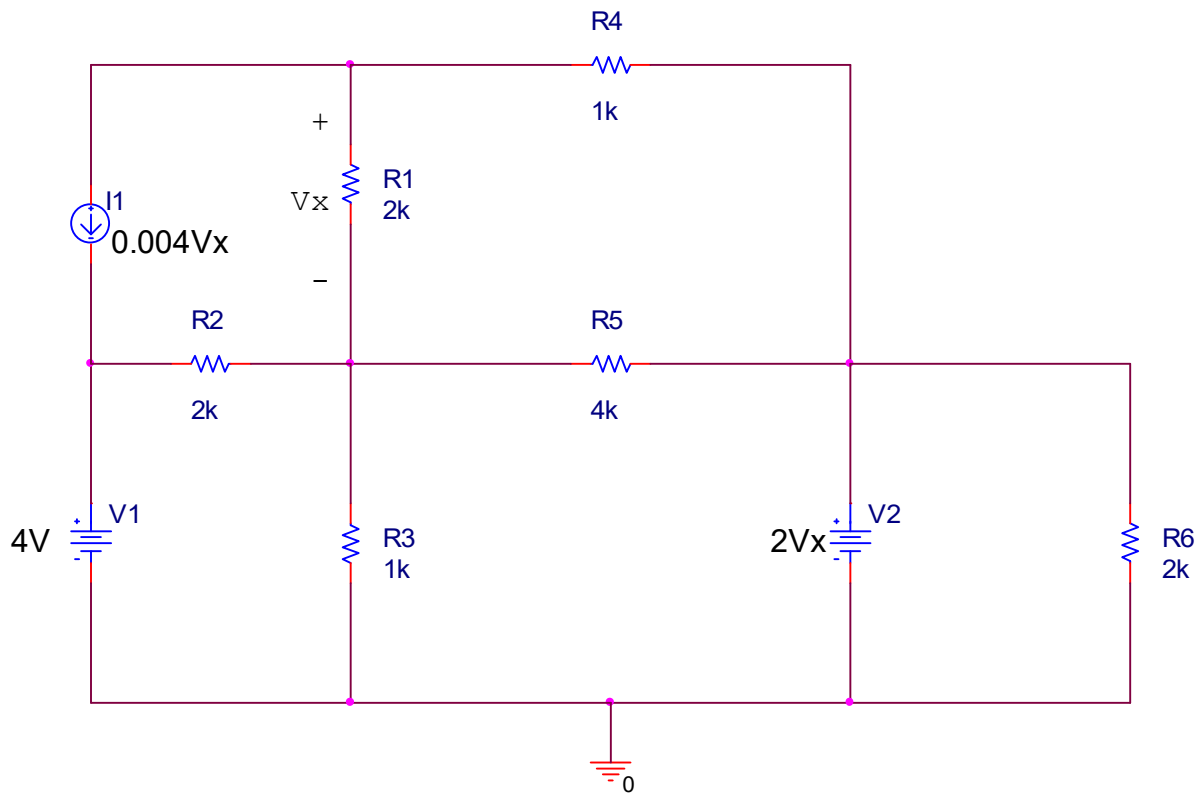


1) Dependent Voltage Sources

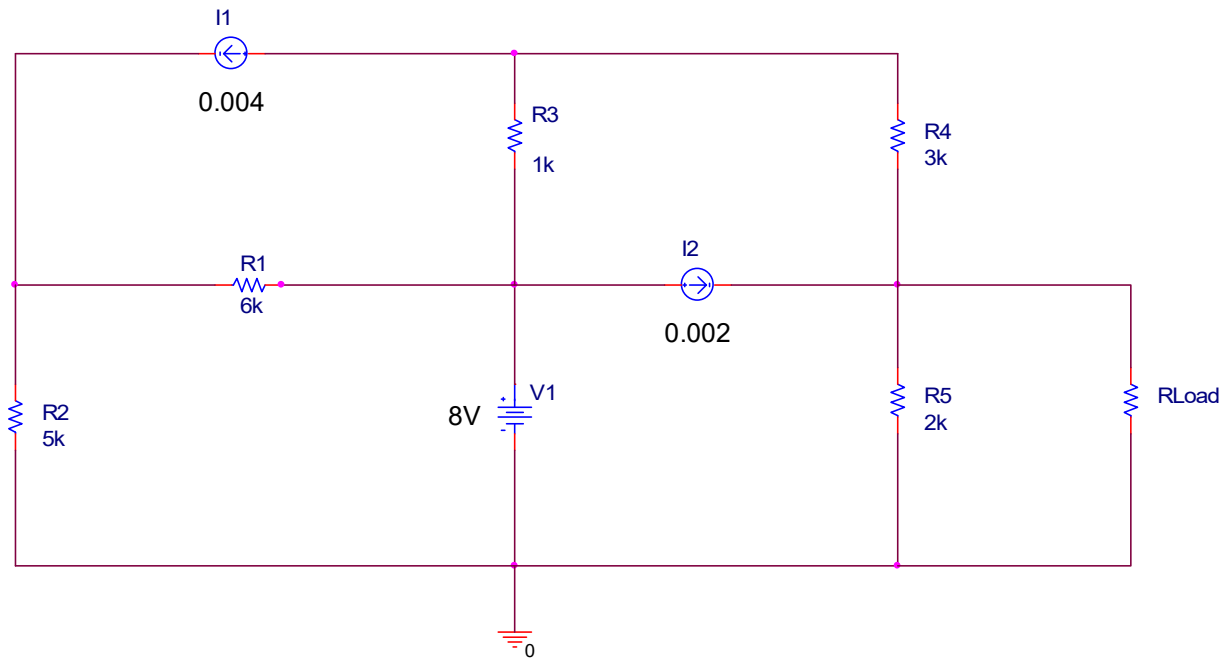


In the circuit above, set up the linear system to analyze the circuit using both mesh and node analysis. You only need to solve for V_x using one of the methods. Be sure to include the following:

- Label the nodes you would use to perform node analysis.
- Clearly write linear system of equations for nodal analysis.
- Clearly write linear system of equation for mesh analysis.
- Find V_x using either method.


2) Thevenin/Norton Voltage

On the above circuit, using any method, find the a) thevenin voltage, b) thevenin resistance, and c) norton current. Draw the schematics of the norton and thevenin circuits for full credit. Confirm your values by any method.

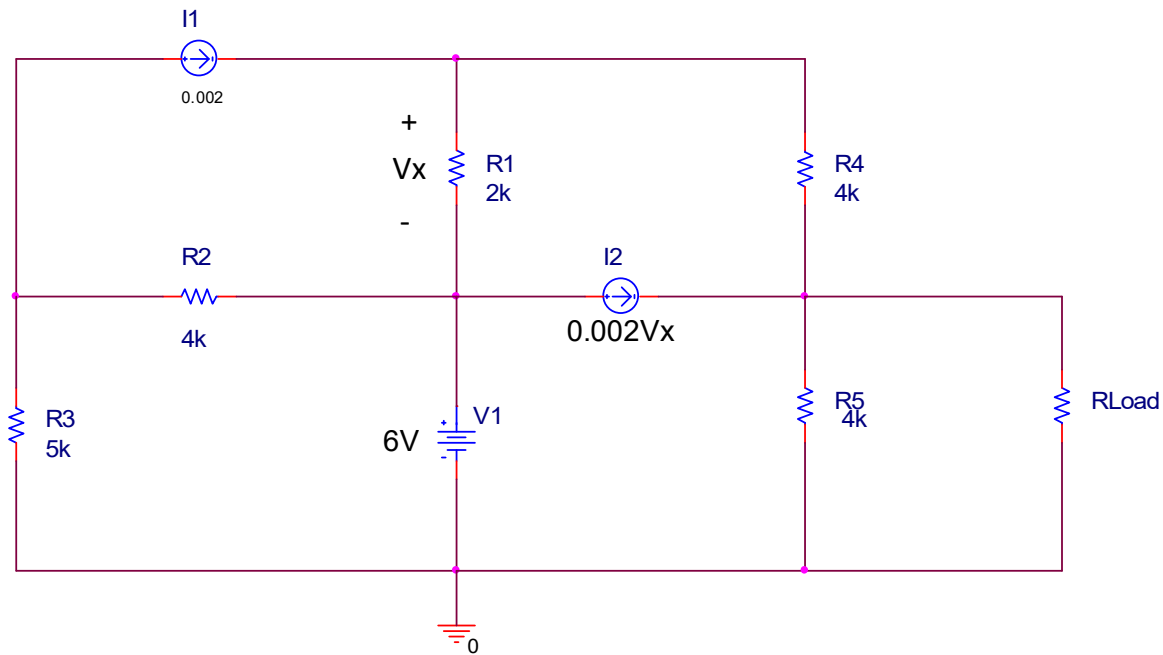3) Thevenin/Norton Voltage

a) Determine V_{TH} using any analysis method, I_N using any analysis method, and R_{TH} using the test method for the above circuit. Verify your answers.

4) Amplifier Circuits

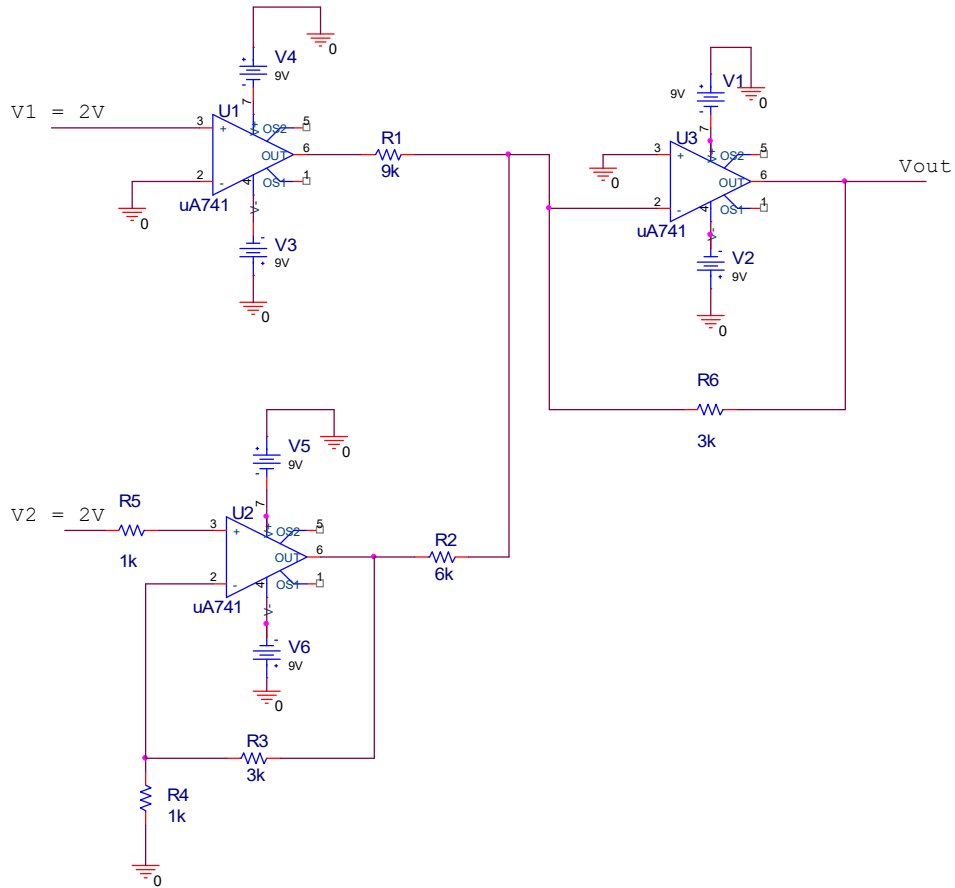

a) Find the output voltage, V_{out} . The voltages to power the op-amps are $9V$ and $-9V$.

5) Amplifier Circuits - Designing problem

- a) Design a two stage amplifier such that the output of the first stage is $V_1 = 5V_{in}$ and the output of the second stage is $V_2 = -V_1$.

