



1.1: For the above circuit, determine the equivalent capacitance between A and B

Note: capacitors in series add like resistors in parallel

Long way: C23 := $\frac{C_2(C_3)}{C_2 + C_3}$ C23 = 3×10^{-9} F C23 = 3×10^{-9} F C234 := $\frac{C23 \cdot C_4}{C23 + C_4}$ C234 = 1.5×10^{-9} F C2345 := C234 + C_5 C2345 = 8×10^{-9} F CTotal := $\frac{C2345 \cdot C_1}{C2345 + C_1}$

1.2:



For the above circuit, determine the equivalent inductance between A and B

 $L_1 := 20\mu H$ $L_2 := 5\mu H$ $L_3 := 10\mu H$ $L_4 := 15\mu H$ $L_5 := 20\mu H$

Note: Inductors in parallel add like resistors in parallel....

Long way: L45 := $\frac{L_4 \cdot L_5}{L_4 + L_5}$ L45 = 8.571 × 10⁻⁶ H Short wav: Tot_L := $\left[\left(\frac{L_4 \cdot L_5}{L_4 + L_5} + L_3 \right)^{-1} + \frac{1}{L_2} \right]^{-1} + L_1$

 $L345 := L45 + L_3$

 $L345 = 1.857 \times 10^{-5} H$

$$L2345 := \frac{L_2 \cdot L345}{L_2 + L345}$$

 $L2345 = 3.939 \times 10^{-6} H$

 $L_{T} := L2345 + L_{1}$

 $L_T = 23.939 \cdot \mu H$

If students use sL, which is more accurate, or this answer mark correct.

2) Amplifier circuits



Electric Cir2uftsFor the RL amplifier circuit, determine the feature from the state of the state

Apply KCL at the negiative input node

$$I_{1} + I_{2} + I_{3} = 0$$

$$I_{1} = \frac{1}{L} \cdot \int V_{.L} dt = \frac{1}{L} \cdot \int (0 - Vin) dt = \frac{-1}{L} \cdot \int V_{in} dt$$

$$I_{1} = \frac{1}{L} \cdot \int V_{.L} dt = \frac{1}{L} \cdot \int (0 - Vin) dt = \frac{-1}{L} \cdot \int V_{in} dt$$

$$I_{2} = \frac{0 - Vout}{R} = \frac{-Vout}{R}$$

$$I_{2} = \frac{0 - Vout}{R} = \frac{-Vout}{R}$$

$$I_{2} = \frac{1}{R} \cdot \int V_{.L} dt = \frac{1}{R} \cdot \int V_{in} dt$$

$$I_{2} = \frac{1}{R} \cdot \int V_{.L} dt = \frac{1}{R} \cdot \int V_{in} dt$$

$$I_{2} = \frac{1}{R} \cdot \int V_{.L} dt = \frac{1}{R} \cdot \int V_{in} dt$$

$$I_{3} = \frac{1}{R} \cdot \int V_{in} dt$$

$$I_{4} = \frac{1}{R} \cdot \int V_{in} dt$$

$$I_{5} = \frac{1}{R} \cdot \int V_{in} dt$$

$$I_{5} = \frac{1}{R} \cdot \int V_{in} dt$$

$$I_{6} = \frac{1}{R} \cdot \int V_{in} dt$$

$$I_{7} = \frac{1}{R} \cdot \int V_{in} dt$$

$$I_$$

13 is zero since there is now current draw in an ideal op amp.



2.2: What type of op amp is this?

It is an integrator (the signal is also inverted, it is ok if students mention this).



2.3: In the above circuit V1=V2=1sin(2π f t) where the frequency is 1 kHz. Determine Vout.

Opamp U1 is a differentiator circuit

$$Vout_{U1} = -RC \cdot \frac{dV_{in}}{dt}$$

$$Vout_{U1} = -(2 \cdot 10^3) \cdot (1.59 \cdot 10^{-7}) \cdot (2000\pi) \cdot \cos(2000\pi t) = -2 \cdot \cos(2000\pi t)$$
[V]

Opamp U2 is a differentiator circuit

$$Vout_{U2} = \frac{-L}{R} \cdot \frac{dV_{in}}{dt}$$
$$Vout_{U2} = \frac{-1.27}{2 \cdot 10^3} \cdot [(2000\pi) \cdot \cos(2000\pi t)] = -4\cos(2000\pi t)$$
[V]

Opamp U3 is a difference amplifier

Note: R4/R2=R6/R5 so the equation can be simplified

$$Vout_{U3} = \frac{R_5}{R_2} \cdot [-4 \cdot \cos(2000\pi t) - (-2 \cdot \cos(2000\pi t))]$$
$$Vout_{U3} = 2 \cdot -2 \cdot \cos(2000\pi t) = -4 \cdot \cos(2000\pi t)$$
[V]

3) Voltage/Current continuity



In the above circuit, the voltage is defined as follows:

$$V1 = \begin{cases} 5V & t < 0 \\ 10V & 0 < t \end{cases}$$
 (the voltage source turns on at t = 0)

3.1: Determine a mathematical expression for the source.

5 + 5u(t)When t is zero u(t) = 0 therefor $5 + 5^*0 = 5$ When t goes to infinity u(t) is 1 therefore $5+5^*1= 10$

A piecewise solution with the step function can also be counted on this homework.

3.2: At t =0- (just before the voltage changes), for the polarities indicated, determine the voltage across each component and the current through each component.

At t=0-, the souce is 5V. Since the intial conditions are V1=5V and dc stead state, the inductor is a

Electric fiontiand the capacitor is an open circuit.

Prof. Shayla Sawyer



Chieffield with 1010 grief to the route in the
--

Component	Voltage	Current
R1	2 V	1mA
R2	3V	1mA
C1	3V	0
L1	0	1 mA

3.3: At t=0⁺ (just after the voltage changes), determine the voltage across each component and the current through each component for the polarities indicated in the circuit.

Because of continuity IL(0-)=IL(0+) like a current source VC(0-) = VC(0+) like a voltage source



Must use Unit 1 circuit analysis Methodel V_{R1b} := 10V - 3V

For IC1 use KCL

$$V_{R1b} = 7V \qquad ImA + \left(\frac{3V - 10V}{2 \cdot 10^{3}\Omega}\right) + I_{C1} = 0 \qquad ImA + \left(\frac{3V - 10V}{2 \cdot 10^{3}\Omega}\right) = -2.5 \cdot mA$$
$$I_{R1b} := \frac{V_{R1b}}{2 \cdot 10^{3}\Omega} = 3.5 \times 10^{-3} A$$
$$I_{C1} := 2.5 mA$$

For VI1 use KVL

CHECK

 $I_{R2b} := 1mA$

 $V_{R2b} = 3V$

 $V_{R2b} := 3 \cdot 10^3 \Omega \cdot 1 mA$

$$V_{I1} = 0$$

 $-3 + 3 + V_{I1} = 0$

Chedre dharyshs gives the following results		
Component	Voltage	Current
R1	7V	3.5mA
R2	3 V	1mA
C1	3 V (continuity)	2.5mA (KCL)
L1	OV (KVL)	1mA (continuity)

Circuit analysis gives the following results

4) First order circuits



4.1: Determine the voltage as a function of time for the source voltage V1 = 10 u(t).

This is the familiar RC circuit with a step function source, which has a solution for t>0 of the form

$$V_{c}(t) = A_{1} \cdot \exp\left(\frac{-t}{RC}\right) + A_{2} = A_{1} \cdot \exp\left(\frac{-t}{1 \cdot 10^{-5}}\right) + A_{1} \cdot \exp\left(\frac{-t}{1 \cdot 10^{-5}}\right)$$

RC time constant

$$V_{c}(t) = A_{1} \cdot \exp\left(\frac{-t}{RC}\right) + A_{2} = A_{1} \cdot \exp\left(\frac{-t}{1 \cdot 10^{-5}}\right) + A_{2}$$

 $10.10^{3} \cdot 1.10^{-9} = 1 \times 10^{-5}$

The initial condition at t = 0 is Vc(t) = 0 = A1+A2The steady state condition as t approaches ∞ (capacitor acts an a open circuit) is Vc= 10 = 0 + A2

The two conditions lead to A1 = -10 and A2 = 10

$$V_{c}(t) = -10 \cdot \exp\left(\frac{-t}{1 \cdot 10^{-5}}\right) + 10$$
 [V]

Electric Circuits

$$V1 = \begin{cases} 0 & t < 0 \\ 10 & 0 < t < 0.001 \\ 0 & 0.001 < t \end{cases}$$

For 0<t<0.001 the solution for part a is the same expression

$$V_{c1}(t) = -10 \cdot \exp\left(\frac{-t}{1 \cdot 10^{-5}}\right) + 10$$

For 0.001<t, the solution takes the form

$$V_{c2}(t) = A_3 \cdot exp\left[\frac{-(t - 0.001)}{1 \cdot 10^{-5}}\right] + A4$$
 [V]

For 0.001<t The DC steady state is zero since the source is off, 0 = 0 + A4, giving A4 = 0

For 0.001<t, when t = 0.001 we have continuity (and the circuit is in steady since since 0.001 > RC).



5. First order switching circuit



In the above circuit, the voltage source turns on at t = 0. Switch U1 closes at t = 0.1 ms. Switch U2 closes and switch U3 opens at t = 0.3 ms (effectively putting resistor R3 in series with C3 at t = 0.3 ms).

5.1: Determine the voltage across R3 as a function of time for t > 0.

Three regions of interest t < 0.1ms

```
0.1ms < t < 0.3ms
0.3ms < t
```

For t<0.1ms, the circuit is a voltage divier with R1, R2 and R3

$$V_{R3} = V_1 \cdot \frac{R_3}{R1 + R_2 + R_3} = 10 \cdot \frac{4k}{10K} = 4V$$

For 0.1ms<t<0.3 ms, the circuit is an RC circuit. Use a Thevenin transformation

$$V_{TH} = 4V$$
 $R_{TH} = 2.4k\Omega$

The voltage across R3 is equal to the voltage acorss the capacitor. Including time delay

$$V_{R3}(t) = V_{c}(t) = -A_{1} \cdot exp \left[\frac{-(t - 0.0001)}{2.4 \cdot 10^{-6}} \right] + A_{2}$$

The initial condition at t = 0.1 ms is Vc(t) = 0 = A1 + A2

The steady state condition at t approaches ∞ is Vc(t) = 4 = 0+A2

Therefore A1 = -4 and A2 = 4

For 0.3ms<t, the capacitor reaches steady state voltage well before 0.3 ms. Essentially, the capacitor is an open circuit. Adding a resistor in seires with the capacitor at this point will not introduce change in the circuit Therefore...

Electric Circuits

$\label{eq:prof.Shayla Sawyer} \begin{array}{l} \mbox{Prof. Shayla Sawyer} \\ t < 0.1 m \mbox{S} \end{array}$

$$V_{R3}(t) =$$
 $-3 \exp \left[\frac{-(t - 0.001)}{2.4 \cdot 10^{-6}} \right] + 4$ $0.1 \, \text{ms} < t < 0.3 \, \text{ms}$

4

4

0.3ms < t