

1) Laplace transforms/Transfer functions

Use Laplace transform tables!!!!

1.1: Find the Laplace transform of


$$f(t) = (\cos(2t) + e^{-4t}) \cdot u(t) \quad (\text{simplify into one ratio})$$

1.2: Find the poles and zeros of the following functions. Indicate any repeated poles and complex conjugate poles. Expand the transforms using partial fraction expansion.

$$1. \quad F(s) = \frac{20}{(s+3) \cdot (s^2 + 8s + 25)}$$

$$2. \quad F(s) = \frac{2s^2 + 18s + 12}{s^4 + 9s^3 + 34s^2 + 90s + 100}$$

2) Circuits and Differential Equations

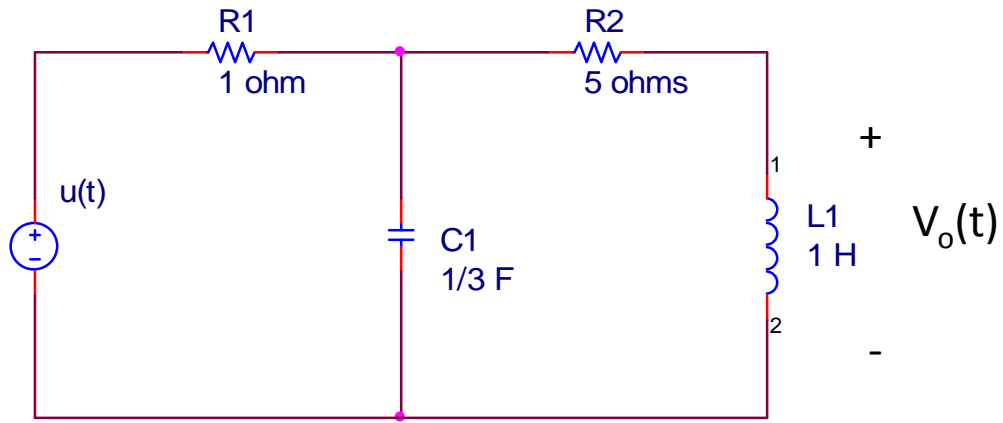


2.1: Draw the s-domain equivalent circuit. Assume all initial conditions are zero and the source is an arbitrary source.

2.2 Using impedances, determine the expression for $V_o(t)$. Consider using mesh analysis then make one ratio.

2.3 Find $V_o(t)$ which is the $V_L(t)$ for $t > 0$ using $V_s = 1 \text{ u}(t)$.

3) RLC and initial conditions

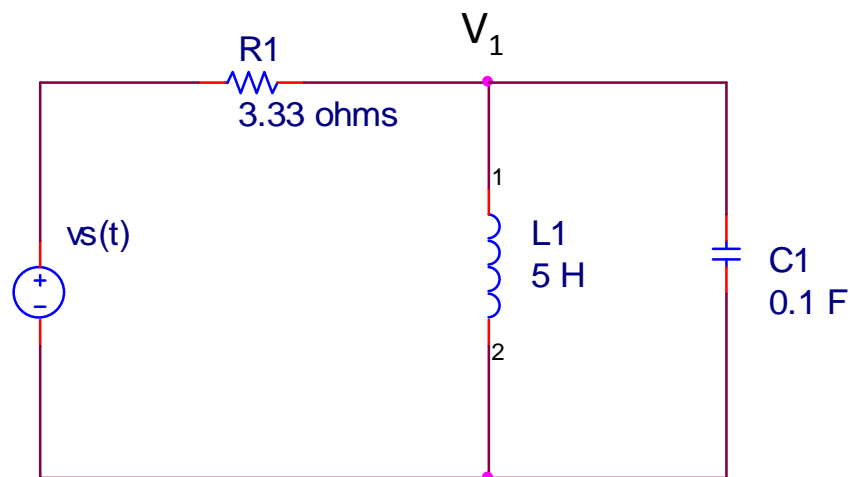


$$v_S(t) = 10u(t)$$

AND assume that -1A flows through the inductor and +5V is across the capacitor at $t=0$i.e. $v_C(0)=5$ and $i_L(0)=-1$

3.1: Draw the s-domain equivalent with initial conditions.

3.2: Find the value of the voltage across the capacitor, $v_c(t)$, using nodal analysis (at node V1) and laplace.

4) RLC parallel circuits

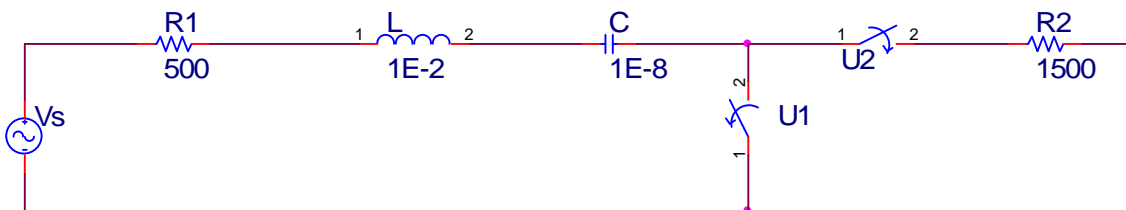

In the above circuit, the source turns on at $t=0$ with a voltage of 10V. Additionally, switch U1 is closed and switch U2 is open. At $15\text{E}-6$ s switch U1 opens and switch U2 closes. The source also turns off at $15\text{E}-6$ s.

4.1: Use Laplace analysis to determine the voltage across the capacitor as a function of time for $0 < t < 15\text{E}-6$ (s)

4.2: Use Laplace analysis to determine the voltage across the capacitor as a function of time for $t > 15\text{E}-6$ s