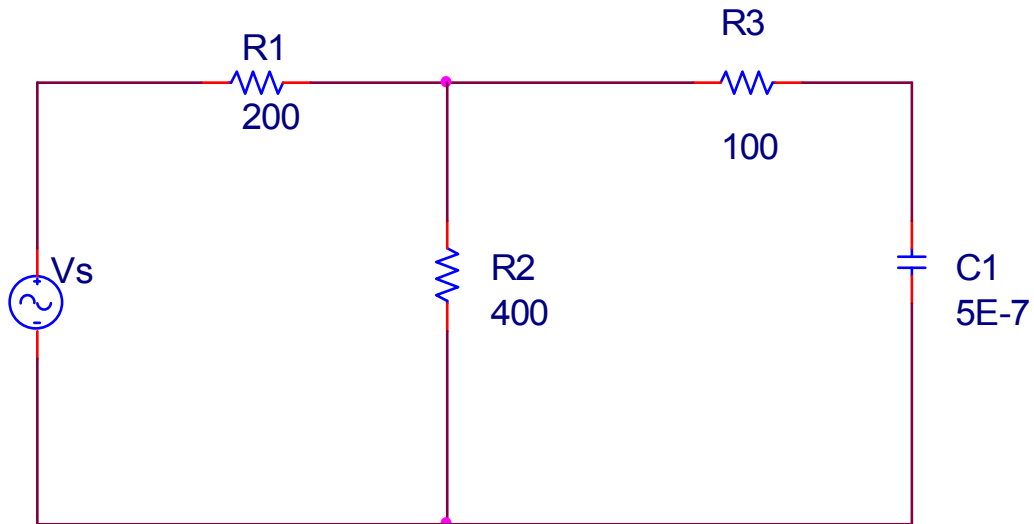


1) Equivalent circuits



1.1: For  $I = 8\angle 45^\circ \text{mA}$  in phasor form with a 1.59kHz frequency, determine the voltage  $V1$  in the time domain form.

2) First order circuits



The source is a 10V sinusoidal signal with a frequency of 636.6Hz and has zero phase.

2.1: Determine the phasor expression for the voltage source.

2.2: Determine the equivalent impedance seen by the source.

2.3: Determine the phasor expression for the current through the source.


2.4: Determine the phasor expression for the voltage across  $C_1$ .

2.5: Determine the time domain expression for the voltage across  $C_1$ .

2.6: Determine the transfer function,  $H(s) = V_{C1}(s) / V_s(s)$ , for the above RC circuit.

2.7: Verify your solution to part d. using the transfer function (remember  $s = j\omega$  in AC steady state).

3) Phasors- RLC

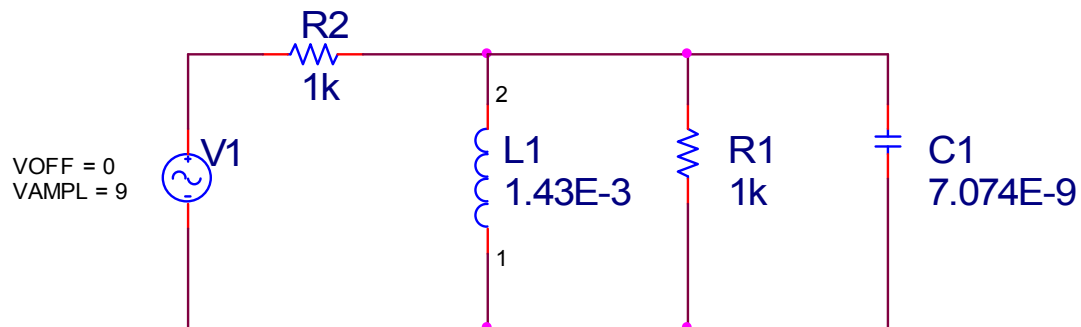


3.1: Using phasor analysis, determine the voltage across the capacitor when the source is 50kHz.

3.2: Using phasor analysis, determine the voltage across the capacitor when the source is 50 Hz.  
(reminder: -90degrees is -j) **Partial answer check:  $Z_{RLC} = 0.45j$**

3.3: Using phasor analysis, determine the voltage across the capacitor when the source is 50MHz  
(50E6Hz).(reminder: 90degrees is j)
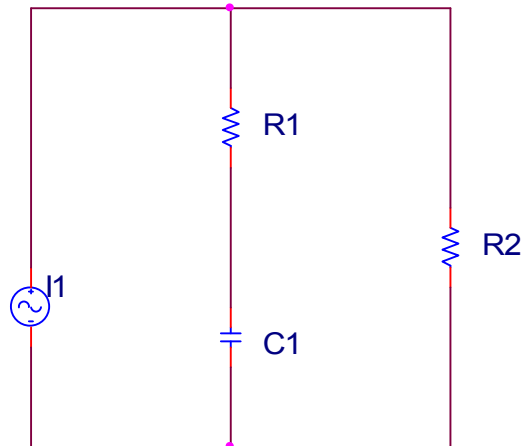
#### 4) Transfer functions


Determine the transfer functions in the following circuit. Determine the behavior of the transfer function as  $\omega \rightarrow 0$  and  $\omega \rightarrow \infty$



4.1: Voltage across C1 relative to the source voltage  $H(s) = \frac{V_{C1}(s)}{I_1(s)}$   
Using the current divider formula (then ohms law)

4.2: Determine the magnitude of the transfer function as frequency approaches zero,  $|H(s \rightarrow 0)|$

4.3: Determine the magnitude of the transfer function as frequency approaches infinity,  $|H(s \rightarrow \infty)|$

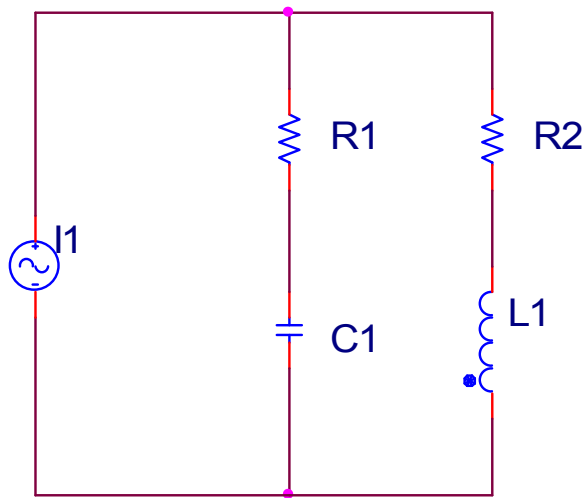

4.4: Voltage across  $L_1$  relative to the source current  $H(s) = \frac{V_{L1}(s)}{I_1(s)}$

4.5: Determine the magnitude of the transfer function as frequency approaches zero,  $|H(s \rightarrow 0)|$

4.6: Determine the magnitude of the transfer function as frequency approaches infinity,  $|H(s \rightarrow \infty)|$