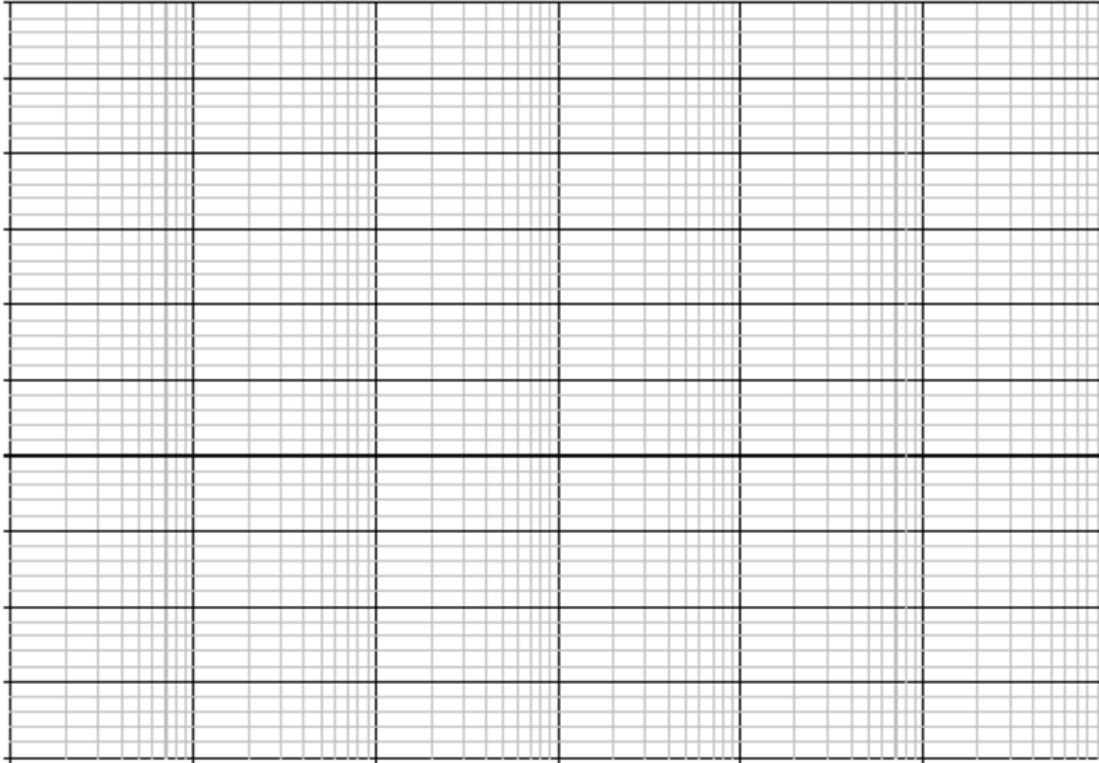


Problem 1) Sketching Bode Plots


Sketch the 'ideal' Bode plots of the magnitude (dB) and phase for the following transfer functions.

1.1
$$H(s) = -10 \cdot \frac{s}{s + 1 \cdot 10^4}$$

Magnitude Bode Plot




Phase Bode Plot

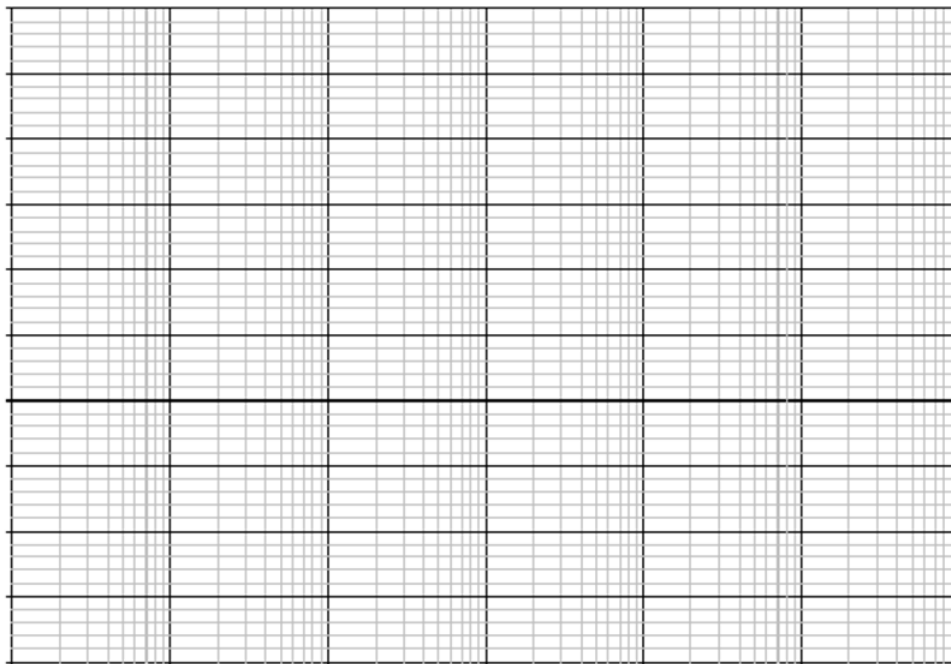


1.2.
$$H(s) = \frac{(s + 5000)}{(s + 10)(s + 1E6)}$$

Magnitude Bode Plot

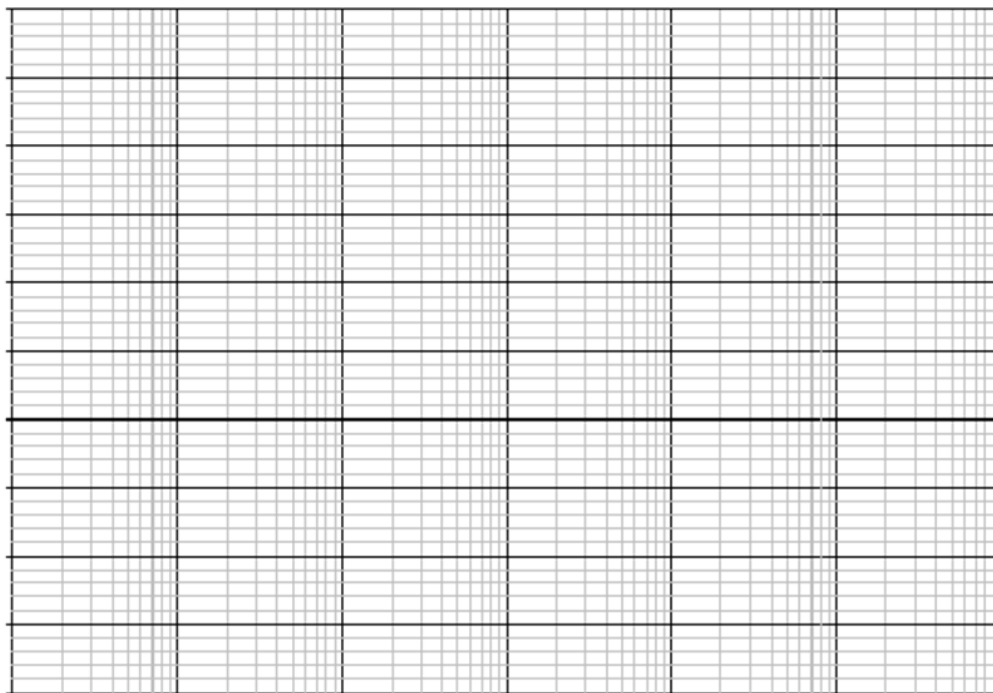


Phase Bode Plot

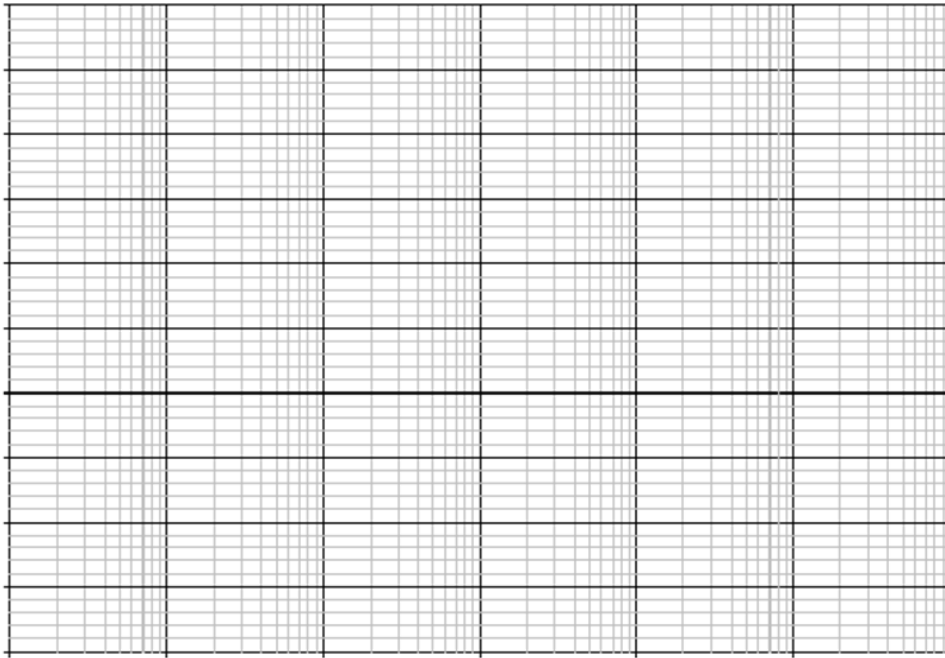

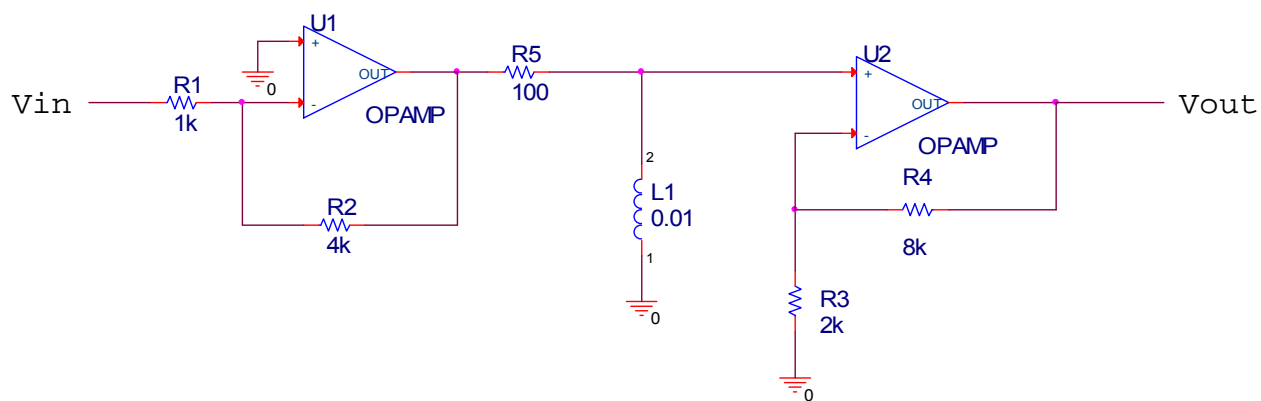Problem 2) Transfer functions, Bode plots, first order circuits

Determine the transfer functions in the following circuits




2.1 Draw the above circuit as a three stage network (put boxes around the stages for example and label $H_n(2)$ $n=1,2,3,\dots$ etc). Indicate the transfer function for each stage.

2.2. Determine the transfer functions, $H(s)$ $V_{out}(s)/V_{in}(s)$, for the circuit.



2.3. What is the gain of the circuit?

2.4. What is the cutoff frequency?

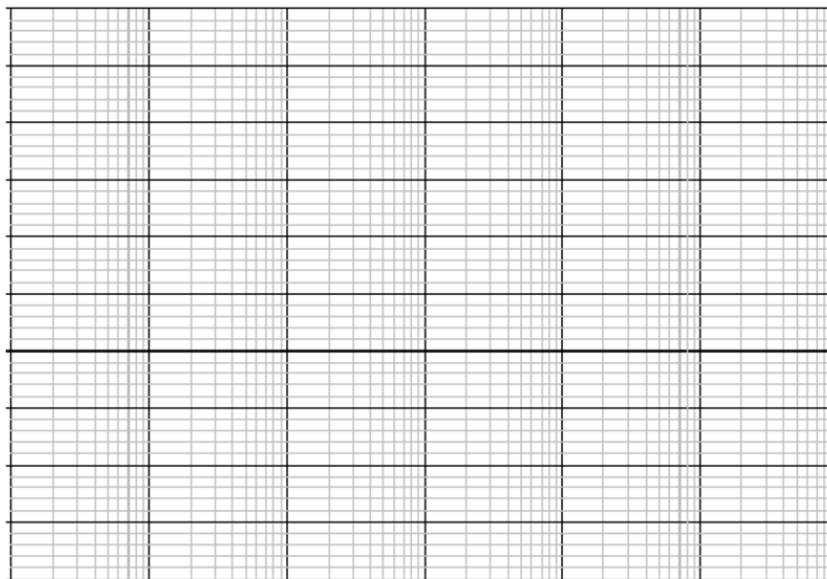2.5. Sketch an approximate Bode (dB-log) plot of the magnitude.



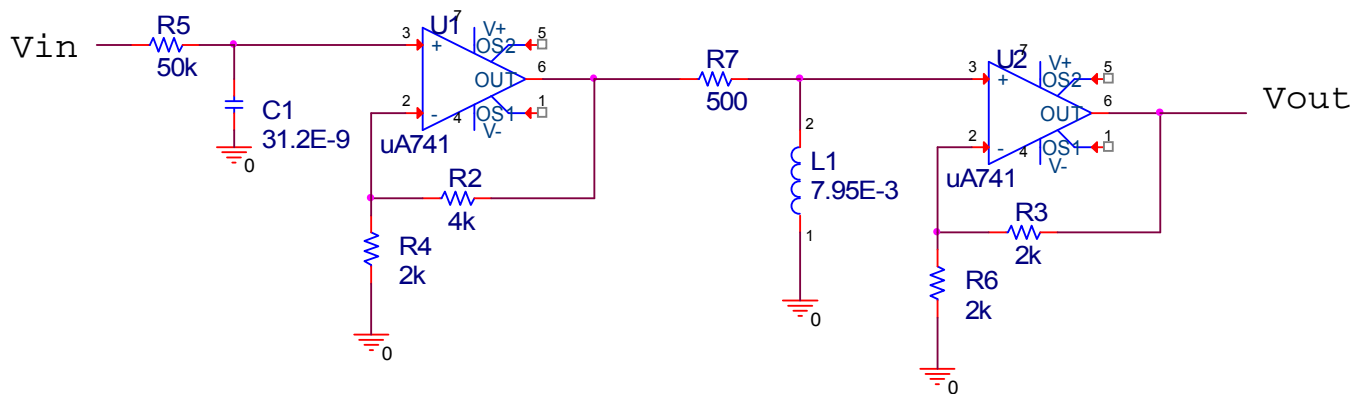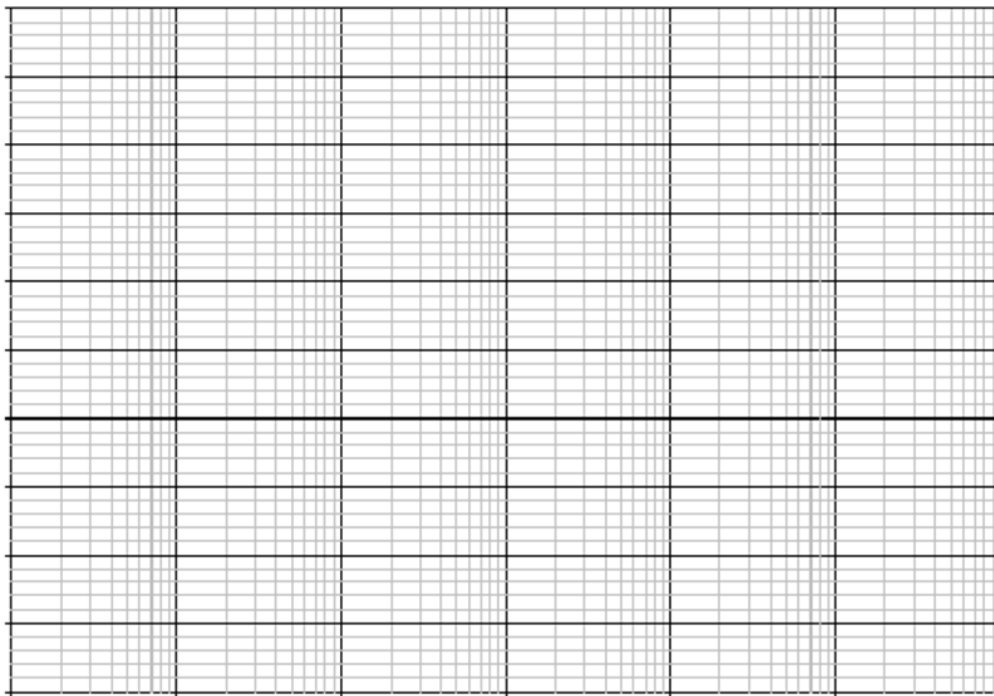
2.7. Sketch an approximate Bode (phase-log) plot of the phase.




2.8. Draw the above circuit as a three stage network (put boxes around the stages for example and label $H_n(2)$ $n=1,2,3,\dots$ etc). Indicate the transfer function for each stage.

2.9. What is the transfer function of the circuit?

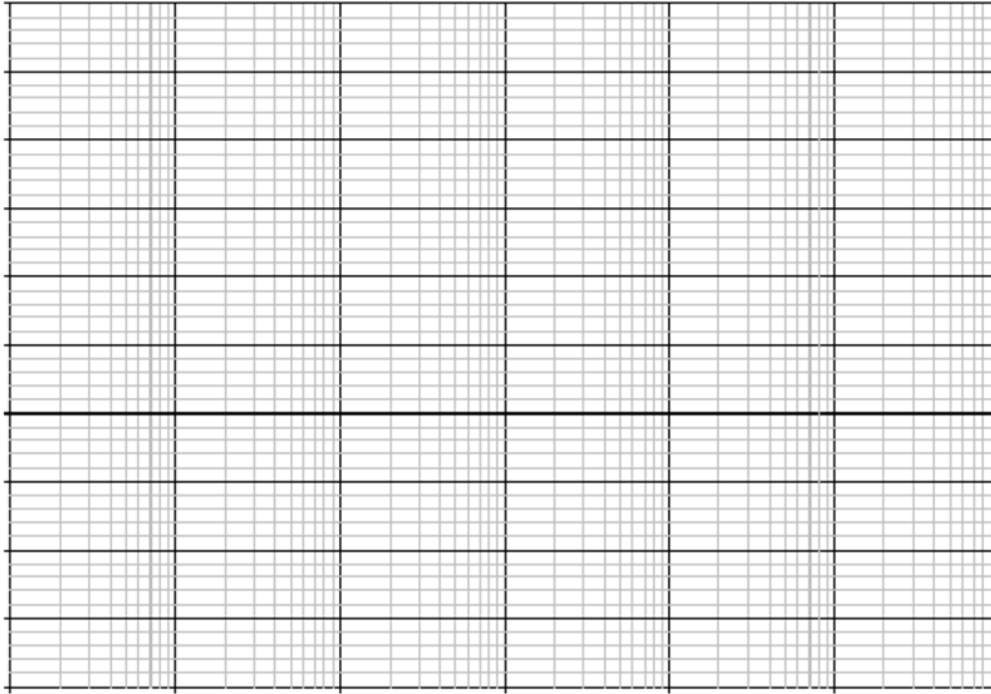
2.10. Sketch an approximate Bode (db-log) of the magnitude.



2.11. Sketch an approximate Bode (phase-log) plot of the phase.

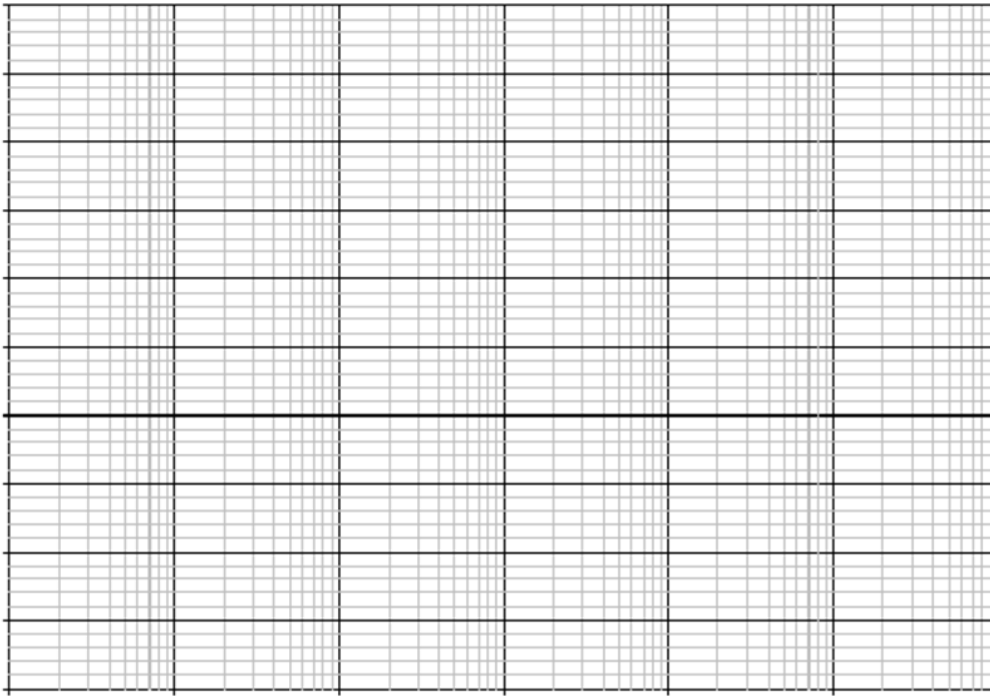

Problem 3) 2nd Order Filter Circuits

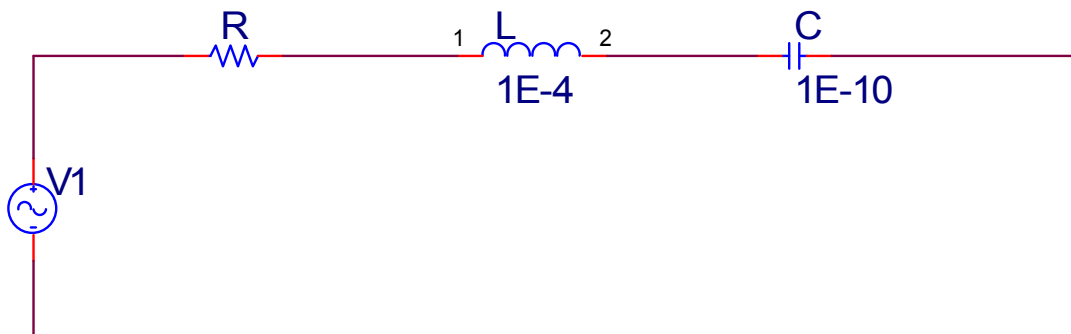


3.1. What is the resonant frequency of the circuit?


3.2. When $R = 100.01 \text{ k}\Omega$,

3.2.1. What is the damping ratio, ζ ?

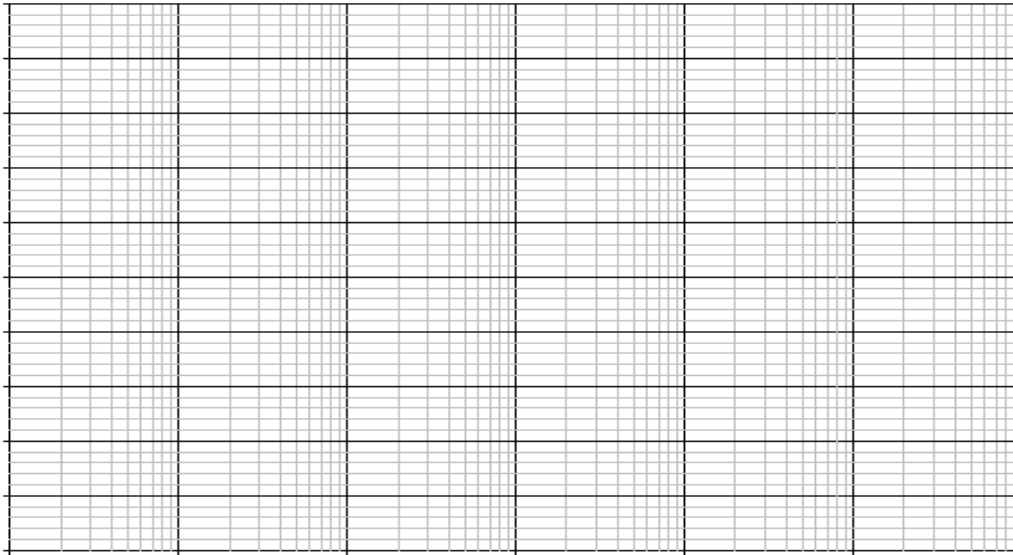3.2.2. Sketch the Bode plot of the magnitude (dB-log) when V_{out} is the voltage across the inductor, $H(s) = V_L(s)/V_1(s)$



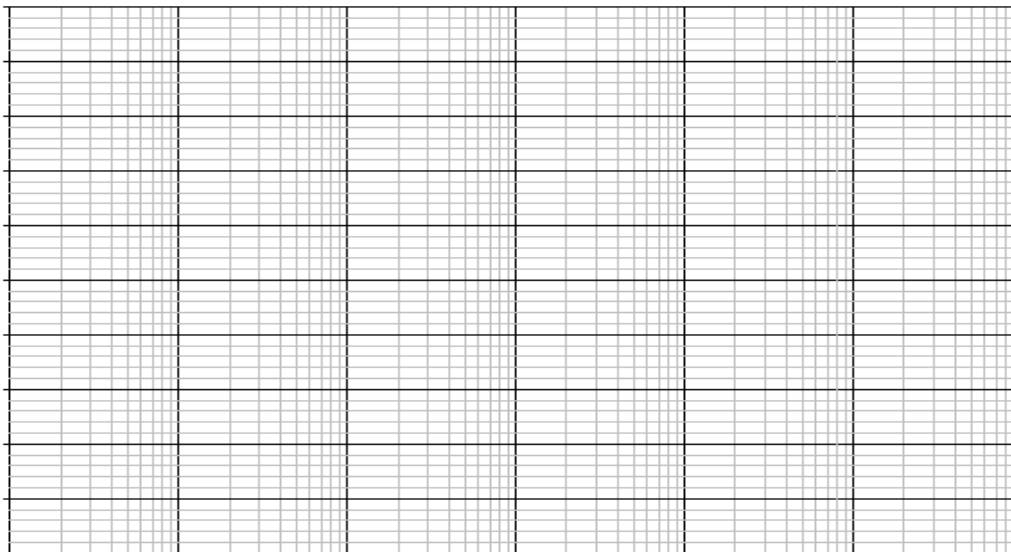
3.2.3. Sketch the Bode plot of the magnitude (dB-log) when V_{out} is the voltage across the resistor, $H(s) = V_R(s)/V_1(s)$.




3.3. When $R = 2000\Omega$,

3.3.1. What is the damping ratio, ζ ?

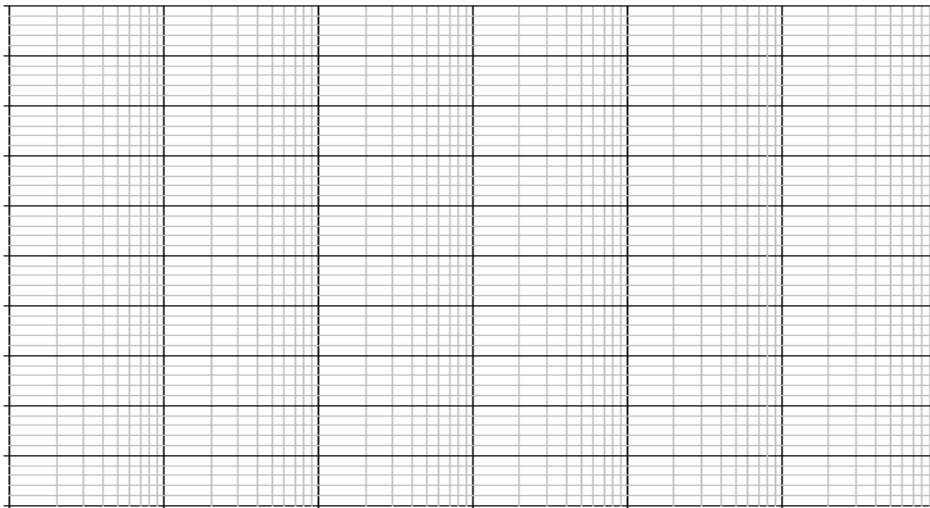3.3.2. Sketch the Bode plot of the magnitude (dB-log) when V_{out} is the voltage across the inductor, $H(s) = V_L(s)/V_1(s)$




3.3.3. Sketch the Bode plot of the magnitude (dB-log) when V_{out} is the voltage across the resistor, $H(s) = V_R(s)/V_1(s)$

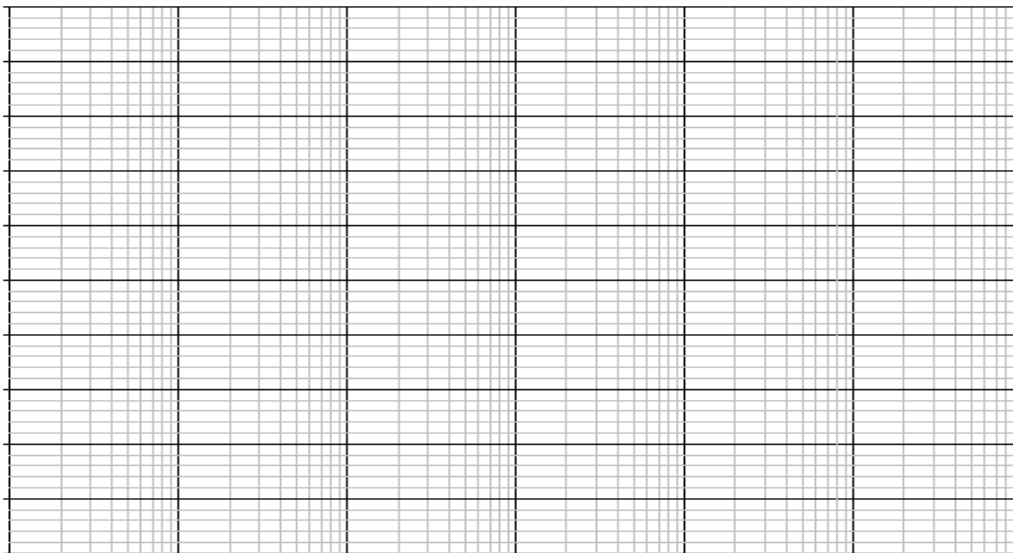

Problem 4) Design Problems

For the problem design specifications, determine a transfer function that meets the requirements. The answers may not be unique. You should provide a plot that verifies that your transfer function meets the specifications.

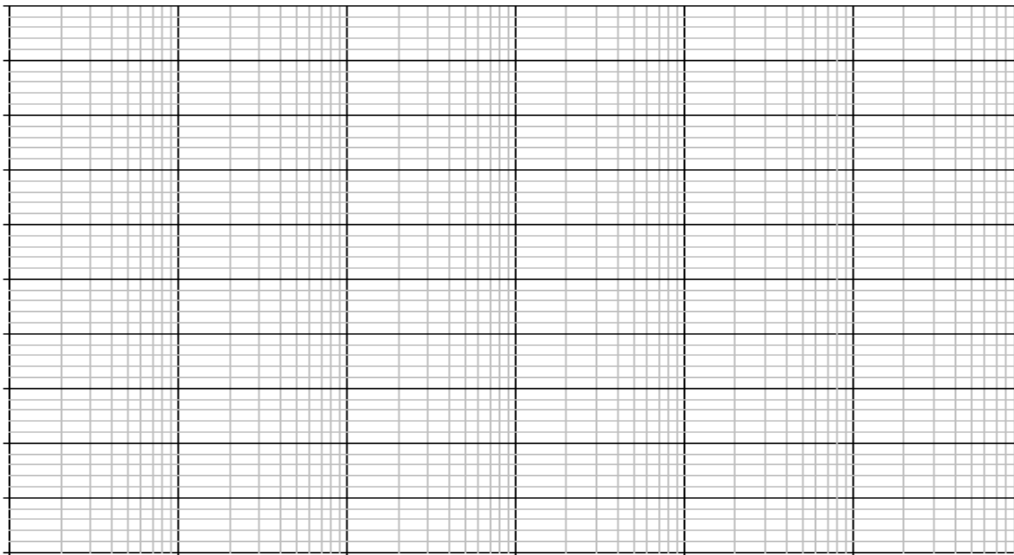1. Design 1
 - a. Bandpass filter with a passband of 100 [rad/s] to 100E3 [rad/s]
 - b. In the passband, the gain should be $0 < \text{gain} < 10\text{dB}$
 - c. The rolloff (slope) in the stopbands should have a magnitude of 40dB/decade



2. Design 2

- a. Narrow bandpass filter centered at $f = 960\text{MHz}$
- b. The gain at the center of the passband should be 20dB
- c. The 17dB points should be $\sim 940\text{MHz}$ at $\sim 980\text{MHz}$

